


EECS 210 W97 Section#2

Final Exam Solutions

(20 points)
Problem # 1

Winick

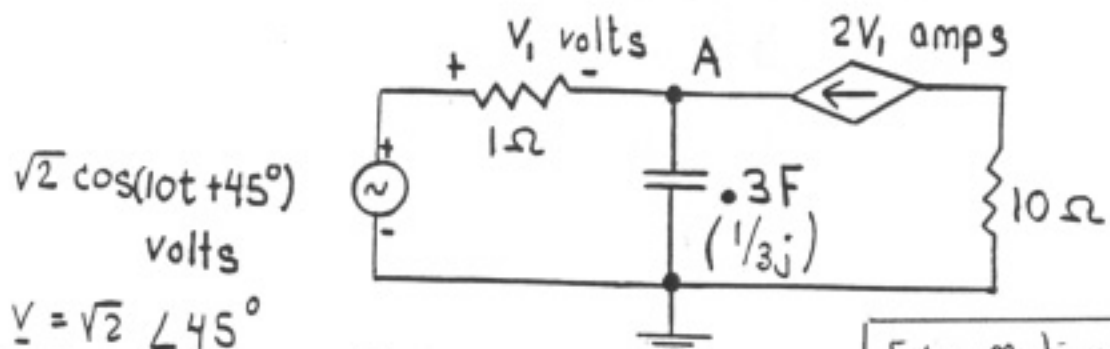Consider the circuit shown below which contains a voltage controlled current source.



$\therefore \underline{V} = \sqrt{2} \angle 45^\circ$
Find the voltage at node A.

$$V_A(t) = \boxed{\cos(10t) \text{ volts}}$$

$$\frac{\underline{V} - \underline{V}_A}{1} + (0 - \underline{V}_A)j3 + 2(\underline{V} - \underline{V}_A) = 0$$

$$\therefore \underline{V}_A = \frac{\underline{V}}{1+j} = \frac{\underline{V}}{\sqrt{2}} \angle -45^\circ$$

$$= 1 \angle 0^\circ$$

Exam Median = 69%


Exam Mean = 64.7%

Score	No. of Students
0-10	3
11-20	3
21-30	3
31-40	11
41-50	10
51-60	9
61-70	10
71-80	11
81-90	16
91-100	18
total = 94	

(20 points)

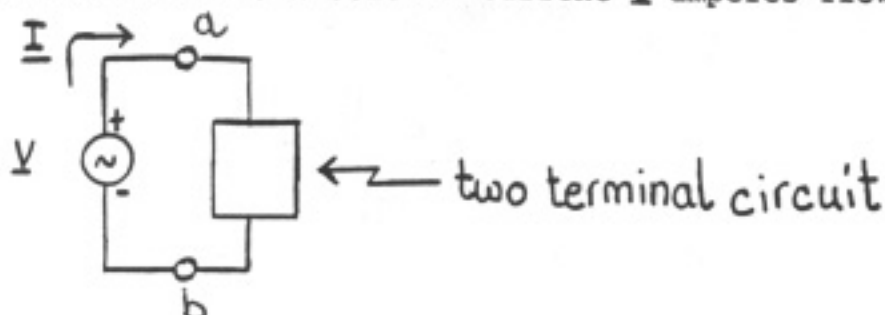Problem # 2

When an arbitrary voltage V volts (at $\omega=100$ rad/s) is applied to the two terminal circuit shown below a current I amperes flows.



It is experimentally found that the relationship between V and I is given by


$$V = (5 + j5) + I(10 + j5)$$

Draw an equivalent two terminal circuit which contains only one independent voltage source (V_g), one resistor (R) and one inductor (L). Specify the values of V_g , R and L .

$$\therefore V_{oc} = (5 + j5)$$

$$I_{sc} = \frac{-(5 + j5)}{10 + j5}$$
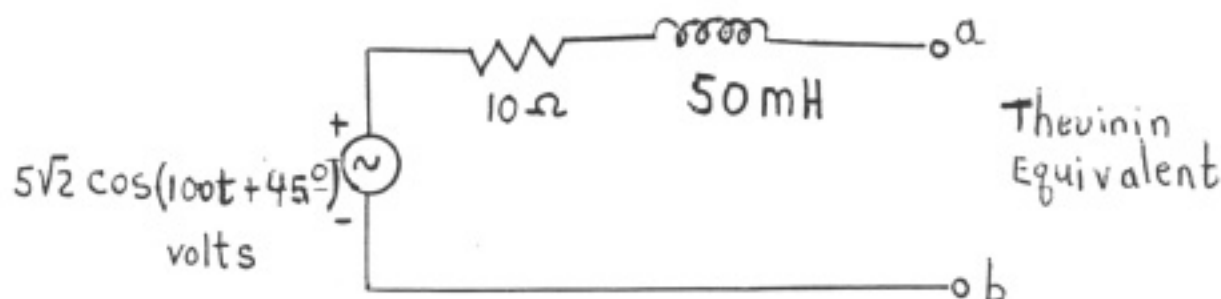
$$Z_T = \frac{-V_{oc}}{I_{sc}} = 10 + j5$$



(20 points)
Problem # 3

The frequency transfer function, $H(\omega)$, of a filter is given by the Bode plots shown on the next page.

- 2 pts. (a) What kind of filter is this?

bandstop or notch

- 9 pts. (b) If the signal
 $x(t) = 0.1 \cos(100t + 5^\circ) + 0.1 \cos(3100t + 53^\circ) + 0.1585 \cos(8 \times 10^5 t + 47^\circ)$
 is input to this filter, then estimate the filter output $y(t)$ using the Bode plot.

$$y(t) = \cos(100t) + \cos(3100t) - \sin(8 \times 10^5 t)$$


$$|H(100)| = 20 \text{ dB } (10), \quad \angle H(100) = \sim -5^\circ (5.08^\circ)$$

$$|H(3100)| = 10 \text{ dB } (3.16), \quad \angle H(3100) = -53^\circ (-53.29^\circ)$$

$$|H(8 \times 10^5)| = 16 \text{ dB } (6.31), \quad \angle H(8 \times 10^5) = 43^\circ (43.57^\circ)$$



- 9 pts. (c) Find the system transfer function, $H(s)$, from the asymptotic Bode plot.

$H(s) =$

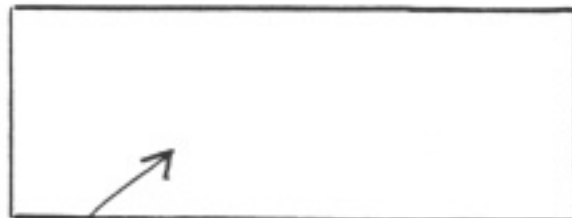


$$10 \frac{(1 + s/10^4)(1 + s/10^5)}{(1 + s/10^3)(1 + s/10^6)}$$

Bode Plots for Problem # 3

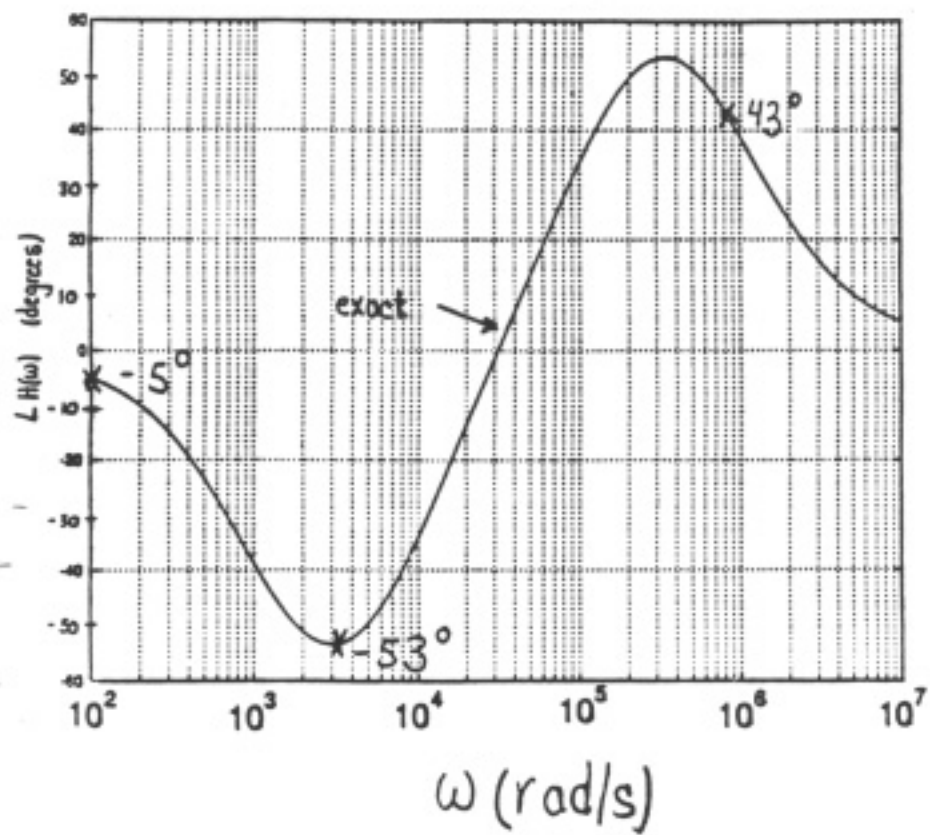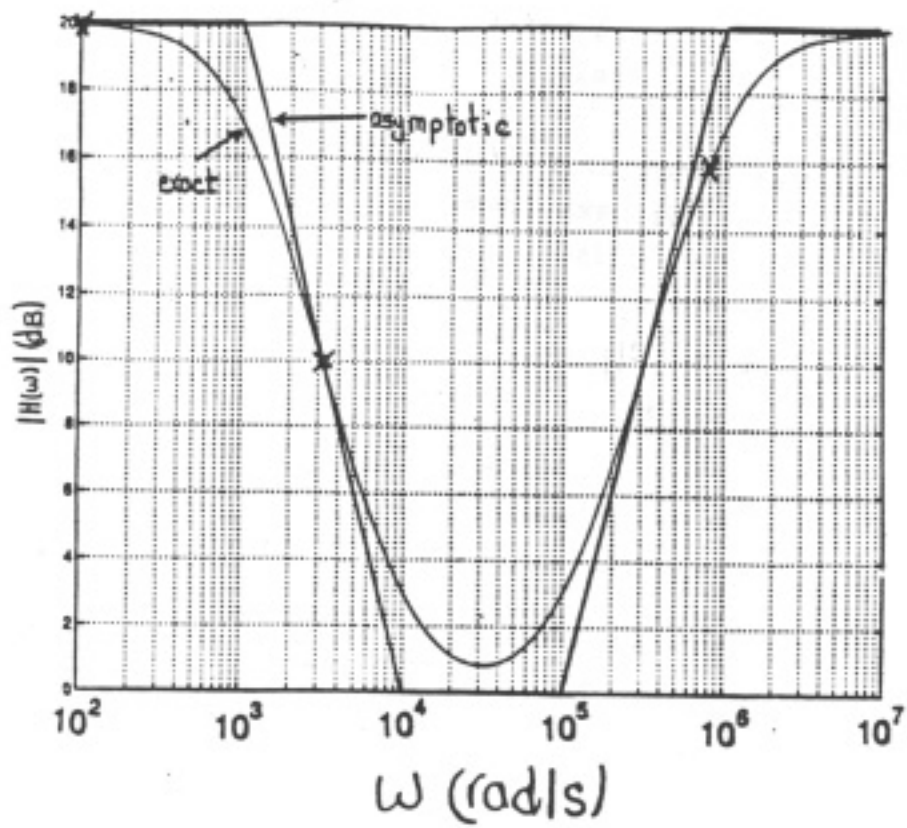

(20 points)
Problem # 4

Consider the Op-Amp circuit shown below.

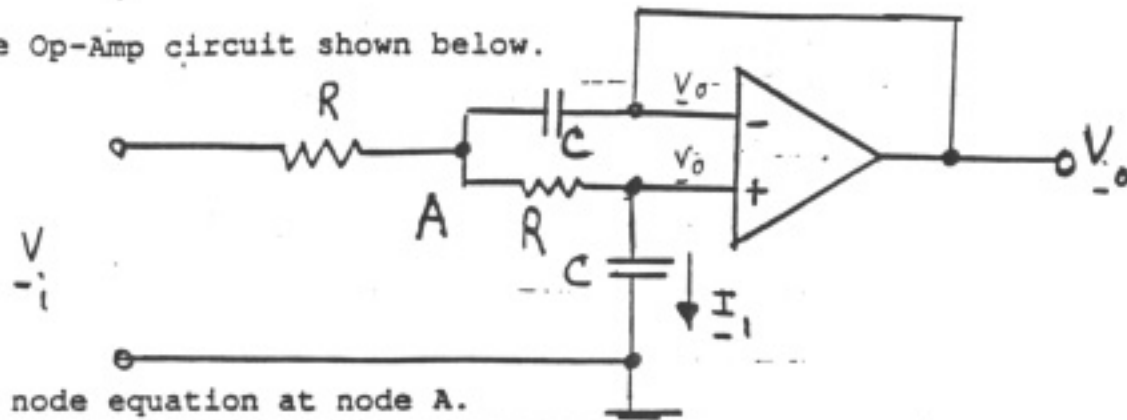

(a) Write a node equation at node A.

$$\frac{V_A - V_i}{R} + (V_A - V_o) sC + \frac{(V_A - V_o)}{R} = 0 \quad (1)$$

$$\text{or } (2 + RCs)V_A = V_i + (1 + RCs)V_o \quad (2)$$

(b) Express the node voltage at node A in terms of V_o by first computing I_1 .

$$I_1 = V_o sC \quad (3)$$

$$V_A - V_o = R I_1 = V_o RCs \quad (4)$$

$$\therefore V_A = (1 + RCs)V_o \quad (5)$$

(c) Combine your results of parts (a) and (b) above to show that the system transfer function is given by

$$H(s) = \frac{1}{as^2 + bs + 1} = \frac{1}{(1 + RCs)^2}$$

Find the values of a and b in terms of R and C.

$$a = (RC)^2$$

$$b = 2RC$$

5pts total (d) For $R=1\Omega$ and $C=1F$, $H(s)$ is given by

$$H(s) = \frac{1}{(1+s)^2}$$

→ 4 pts.

Sketch the asymptotic Bode plot (magnitude only) of this $H(s)$ on page 12. What type of filter is this?

Low Pass

← 1 pt.

5pts (e) When $R=1\Omega$ and $C=1F$, the 3 dB cut-off frequency ω_c (i.e., $|H(\omega_c)|=0.707|H(0)|$) is 0.644 rad/s. Frequency and impedance scaling are used to transform this circuit into a new low-pass filter with $C=10\text{ nF}$ and 3 dB cut-off frequency 6440 rad/s. Find the new value for R .

$R =$

10k Ω

$$K_f = 6440 / 0.644 = 10^4$$

$$C^{new} = C^{old} / K_f K_m \Rightarrow K_m = 10^4$$


\uparrow 10nF \uparrow 1F \uparrow 10⁴

$$R^{new} = K_m R_{old} \Rightarrow R^{new} = 10k\Omega$$

Work Area For Problem # 4


(continued on page 13)

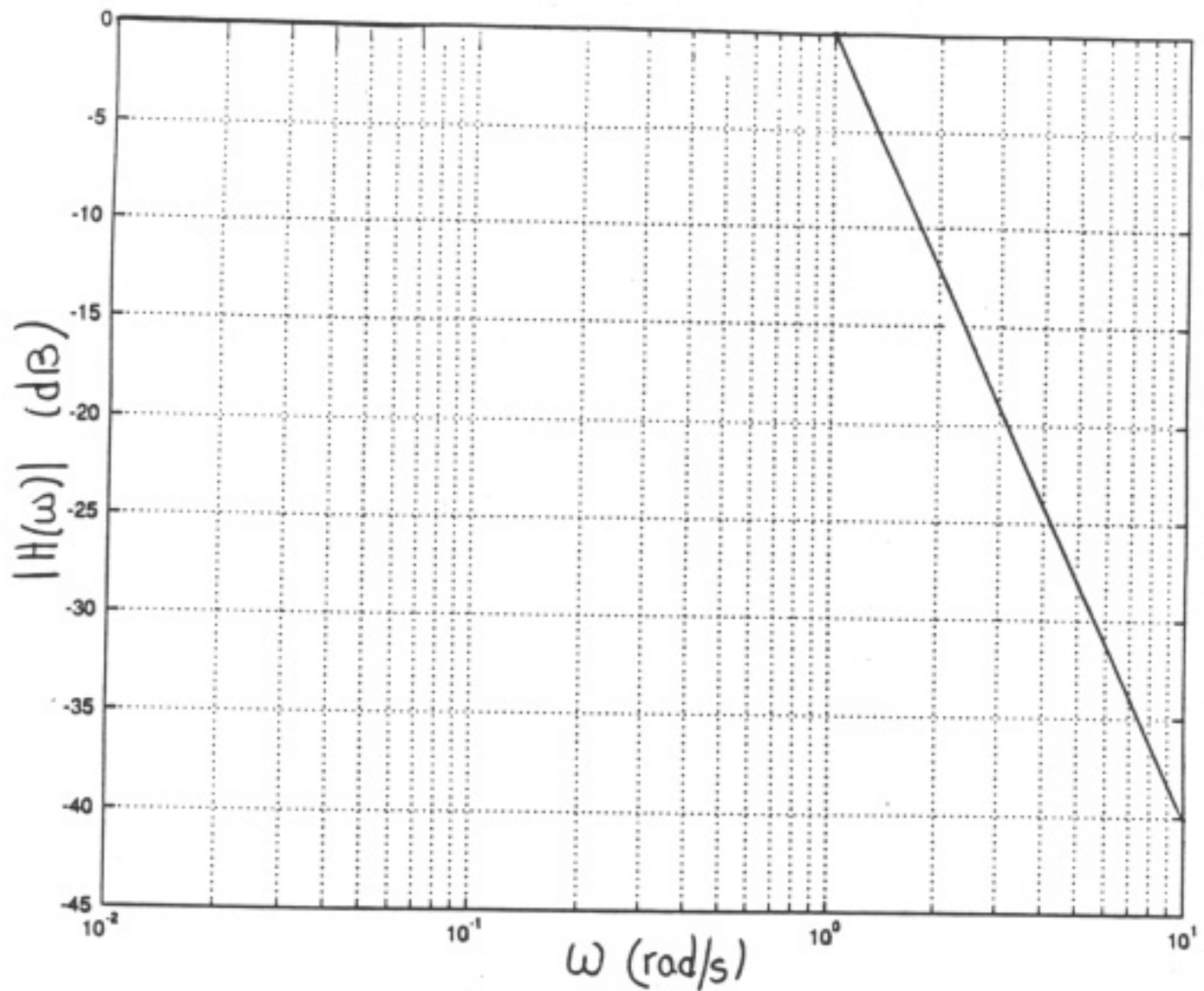Asymptotic Bode Plot (Magnitude) for Problem #4



(20 points)
Problem # 5

Consider the circuit shown below.

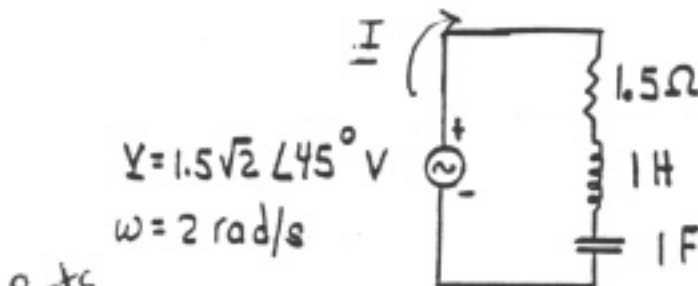

8 pts

(a). Compute the power factor seen by the source. Specify whether it is leading or lagging.

$$pf = \boxed{.707 \text{ lagging}}$$

$$Z = 1.5 + j2 - .5j = 1.5(1 + j)$$

$$\angle pf = \tan^{-1} \frac{-1.5}{1.5} = -45^\circ$$

$$\therefore pf = .707 \text{ lagging}$$

4 pts

(b). Find the (i) apparent power, (ii) complex power, and (iii) real power delivered by the source. Don't forget to include the units.

$$\underline{I} = \underline{V} / \underline{Z} = 1.5\sqrt{2} \angle 45^\circ / 1.5\sqrt{2} \angle 45^\circ = 1 \angle 0^\circ \text{ A}$$

$$\text{apparent power} = \frac{1}{2} |\underline{I}| |\underline{V}| = \frac{1}{2} (1)(1.5\sqrt{2}) = \underline{1.5/\sqrt{2} \text{ VA}}$$

$$\text{complex power} = \underline{S} = \frac{1}{2} \underline{V} \underline{I}^* = \frac{1}{2} (1.5\sqrt{2} \angle 45^\circ) 1 = .75\sqrt{2} \angle 45^\circ = \underline{.75(1+j) \text{ VA}}$$

$$\text{real power} = \underline{.75 \text{ W}}$$

8 pts

(c). A second load is connected in parallel with the series RLC combination. This load dissipates 1.25 W and has a power factor of 0.9806 lagging. Compute the power factor seen by the source with these two loads connected in parallel. Specify whether it is leading or lagging.

$$pf = \boxed{}$$

$$\underline{S}_2 = 1.25 + jQ_2$$

$$\angle pf_2 = -\cos^{-1}[.9806] = -11.304^\circ$$

$$= \tan^{-1}[-Q_2/1.25]$$

$$\underline{S}_{tot} = \underline{S}_1 + \underline{S}_2 = P_{tot} + jQ_{tot}$$

14

$$\therefore Q_2 = .25 \text{ VAR}$$

$$= (.75 + j.75) + (1.25 + j.25)$$

$$= 2 + j1 \text{ VA} \Rightarrow \angle pf_{tot} = \tan^{-1}(1/2) = -26.57^\circ$$

$$pf_{tot} = \underline{.894 \text{ lagging}}$$