

EECS 210 W97
midterm#2 (Winick)

(25 points)
Problem # 1

- 10 (a) $A \cos(10t + \theta) = 5 \cos(10t + 45^\circ) + 5 \cos(10t + 135^\circ) + 10(2)^{1/2} \sin(10t)$
Find A.


$$A = \boxed{5\sqrt{2} = 7.07}$$

convert to phasor form

& then add phasors.

Find magnitude of resultant phasor.
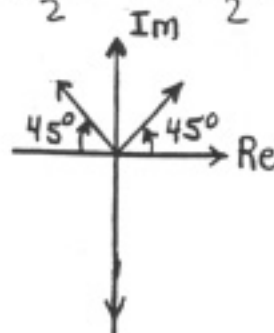
$$\begin{aligned} A \angle \theta &= 5 \angle 45^\circ + 5 \angle 135^\circ + 10\sqrt{2} \angle -90^\circ \\ &= \left(5 \frac{\sqrt{2}}{2} + j 5 \frac{\sqrt{2}}{2}\right) + \left(-5 \frac{\sqrt{2}}{2} + j 5 \frac{\sqrt{2}}{2}\right) - 10\sqrt{2} j \\ &= -5\sqrt{2} j \end{aligned}$$



10 (b)

$$x + jy = \frac{(4.33 + j 2.5)(1.414 + j 1.414)(-2.121 + j 2.121)}{(2.5 - j 4.33)(3 - j 5.196)}$$

Find x and y.

$$\begin{aligned} &= \frac{(5 \angle 30^\circ)(2 \angle 45^\circ)(3 \angle 135^\circ)}{(5 \angle 300^\circ)(6 \angle 300^\circ)} = 1 \angle -30^\circ \\ &= .866 - j .5 \end{aligned}$$

$$x = \boxed{.866}$$

$$y = \boxed{-.5}$$

Do computation
using polar
form.

- 5 (c) $x + jy = (1 + j .176325)^{30}$ Find x and y.

$$x = \boxed{0.7915}$$

$$y = \boxed{-1.371}$$

$$Z = (1 + j .176325)$$

$$= 1.01543 \angle 10^\circ$$

$$\therefore Z^{30} = (1.01543)^{30} \angle 300^\circ$$


$$= 1.583 \angle 300^\circ$$

$$= 0.7915 - j 1.371$$

(25 points)

Problem # 2

Consider the following circuit.

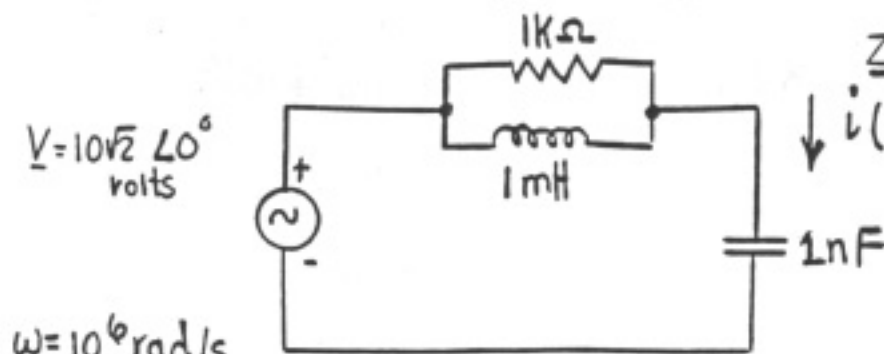

$\omega = 10^6 \text{ rad/s}$
10 (a) Find $i(t)$.

$$i(t) = \boxed{20 \cos(10^6 t + 45^\circ) \text{ mA}}$$

$$1k\Omega \parallel 1mH = 500 + j500\Omega$$

$Z = (1nF)$ series with

$$1k\Omega \parallel 1mH = -j1000 + 500 + j500 \\ 500 - j500\Omega$$

$$\underline{I} = \underline{V} / \underline{Z} = 20 \angle 45^\circ \text{ mA}$$

↑ impedance seen by source

10 (b) Find the average power supplied by the voltage source.

$$P_{av} =$$

$$\boxed{100 \text{ mW}}$$


$$P_{av} = \frac{1}{2} \text{Re}[\underline{V} \underline{I}^*]$$

$$= \frac{1}{2} (10\sqrt{2} \text{ V}) (20 \text{ mA}) \cos(-45^\circ)$$

$$= 100 \text{ mW}$$

5 (c) Sketch an equivalent circuit when $\omega \rightarrow 0$.

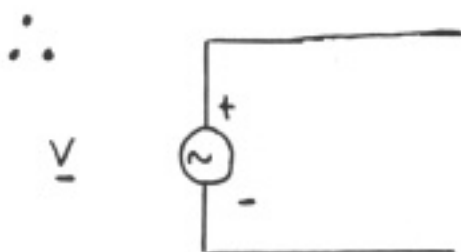
When $\omega \rightarrow 0$, capacitor is open & inductor is short



(25 points)

Problem # 3

Consider the Op-Amp circuit shown below.

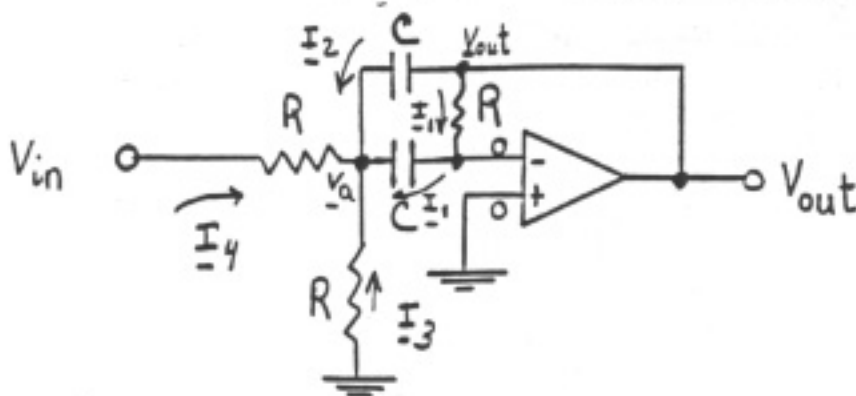

$$V_{in}(t) = \sqrt{5} \cos(10^6 t + \pi/3) \text{ V}$$

$$R = 1 \Omega$$

$$C = 1 \mu\text{F}$$

Find $v_{out}(t)$.

$$v_{out}(t) = \boxed{\cos(10^6 t + 266.565^\circ) \text{ Volts}}$$

$$I_1 = V_{out}/R = V_{out} \quad (1)$$

$$V_a = -I_1 \left(\frac{1}{j\omega C} \right) = -I_1 \left(\frac{1}{j} \right) = jI_1 \quad (2)$$

$$\therefore \boxed{V_a = jV_{out}} \quad (3)$$

$$\text{KCL @ node } a \quad I_4 + I_2 + I_1 + I_3 = 0 \quad (4)$$

$$\therefore (V_{in} - V_a)/R + (V_{out} - V_a)j\omega C + V_{out}/R - V_a/R = 0 \quad (5)$$


$$\rightarrow (V_{in} - jV_{out}) + j(V_{out} - jV_{out}) + V_{out} - jV_{out} = 0 \quad (6)$$

$$\Rightarrow V_{out} = \frac{1}{-2+j} V_{in} = \left(\frac{1}{\sqrt{5}} \angle 206.565^\circ \right) V_{in}$$

$$\therefore V_{out}(t) = \cos(10^6 t + 266.565^\circ)$$

(25 points)
Problem # 4

Consider the circuit shown below.

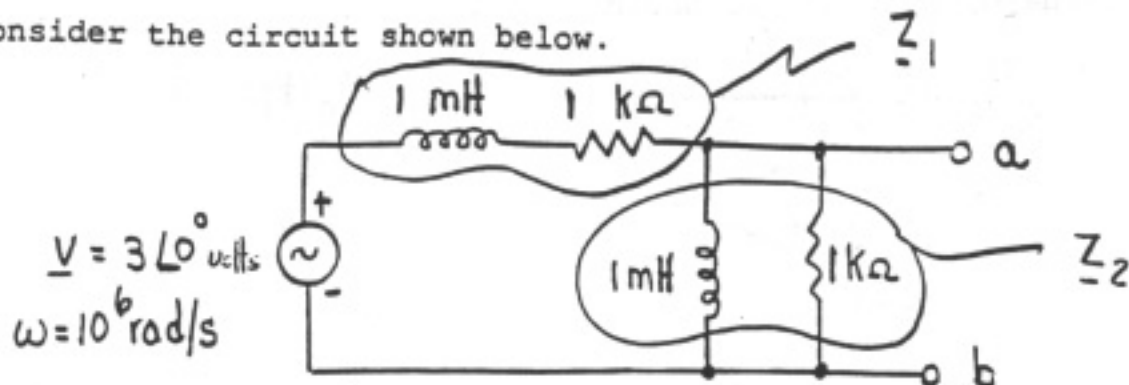

(a) Find the Thevenin equivalent voltage V_T .

$$V_T = \boxed{1 \angle 0^\circ \text{ V}}$$

$$Z_2 = 1 \text{ mH} \parallel 1 \text{ k}\Omega = 500 + j500 \Omega$$

$$Z_1 = 1 \text{ mH series } 1 \text{ k}\Omega = 1000 + j1000$$

$$\text{voltage divider} \Rightarrow V_{OC} = \frac{Z_2}{Z_1 + Z_2} V = \frac{1}{3} V = 1 \angle 0^\circ$$

(b) Find the Thevenin equivalent impedance Z_T .

$$Z_T = \boxed{\frac{1000}{3} + j\frac{1000}{3} \Omega}$$

$$Z_T = Z_2 \parallel Z_1 = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{2}{3} Z_2$$

(turn-off the independent voltage source)

⇒ i.e., short circuit it

$$= 477.3 \angle 45^\circ$$

(c) A load impedance $Z_L = 500 + j1500 \Omega$ is connected across terminals a and b. Find the power, P_L , delivered to the load.

$$P_L = \boxed{61.64 \text{ W}}$$

$$I_L = \frac{V_T}{Z_T + Z_L} = \frac{1}{833.3 + j1833.3}$$

$$P_L = \frac{1}{2} |I_L|^2 R_L = \frac{1}{2} (2.466 \times 10^{-7}) 500$$