
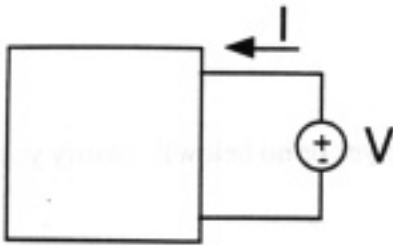


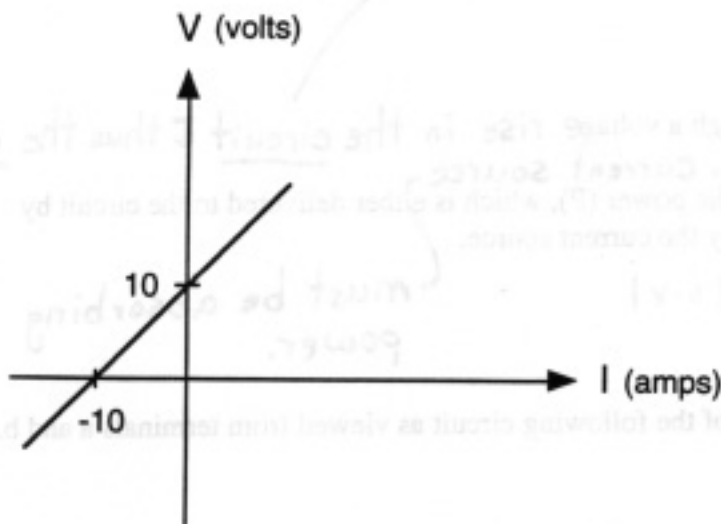1. (7 pts.) (a) Consider the following circuit connected to an external voltage source as shown.



The relationship between  $V$  and  $I$  is plotted below.



Draw the Thevenin equivalent for this circuit in the space provided below.

$$V_{oc} = 10 \text{ V and } I_{sc} = -10 \text{ A.}$$


$$\text{Thus } V_T = 10 \text{ V and } R_T = 1 \text{ } \Omega.$$

$$V_T = V_{oc}$$

$$R_T = \frac{-V_{oc}}{I_{sc}}$$

total

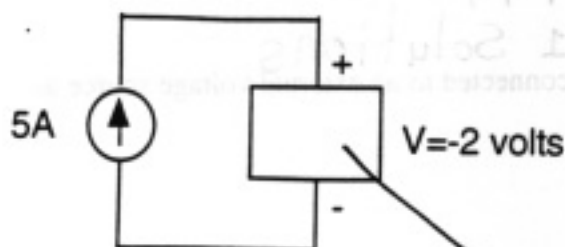- (6 pts.) 1(b) Consider the ideal current source connected to a circuit as shown below. The voltage drop across the circuit terminals is  $-2$  volts as indicated.



Is the current source delivering power to the circuit( circle yes or no below)? Justify your answer using one sentence.

(2 pts.) YES

NO

(3 pts.) Justification sentence:


Positive charge is flowing through a voltage rise in the circuit & thus the circuit is generating power.  $\therefore$  Current source must be absorbing power.

(1 pt.)  $P = 10 \text{ W}$ .

$$P = |i \cdot v|$$



must be absorbing power.

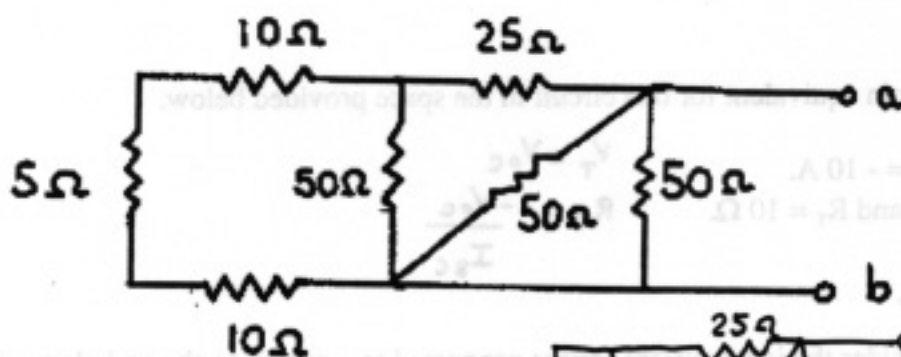(7 pts.) 1(c) Find the resistance of the following circuit as viewed from terminals a and b.



$$R = 15.625 \Omega$$
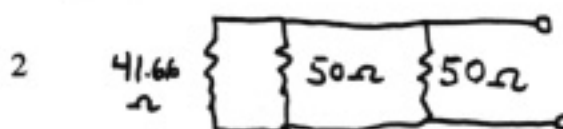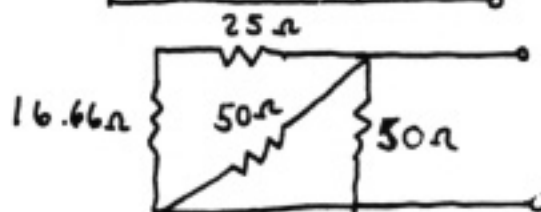
$$\frac{1}{41.66} + \frac{1}{50} + \frac{1}{50} = \frac{1}{R}$$



2. Consider a periodic sawtooth signal which has the following Fourier series representation, where  $t$  is in seconds.

$$x(t) = \sum_{n=1}^{\infty} (-1)^{n+1} \frac{\sin(n\pi t)}{n}$$

(2 pts) (a) Find its period.

$$\text{Period} = 2\pi \text{ s}$$

(2 pts) (b) Find the frequency of the sawtooth signal in Hz and rad/s.

$$\text{Frequency} = 1/(2\pi) \text{ Hz.}$$

$$1 \text{ rad/s}$$

(2 pts) (c) Find the frequency of the fourth harmonic in Hz.

$$\text{Fourth Harmonic Frequency} = 2/\pi \text{ Hz}$$

(14 pts) (d) If  $x(t)$  as given above is the input to a linear time-invariant system, the output  $y(t)$  is

$$y(t) = \cos(3t) + \sin(2t + \frac{\pi}{4})$$

Note filter only passes  
2<sup>nd</sup> & 3<sup>rd</sup> harmonic terms

Find the output  $y(t)$  of this system when the input is

$$4 \sin(t + \frac{\pi}{6}) + \cos(2t)$$


$$\therefore y(t) = 2 \cos(2t + \frac{5\pi}{4})$$

$$|H(\frac{3}{2}\pi)| = 2$$

$$\angle H(\frac{3}{2}\pi) = \frac{\pi}{4} + \pi$$

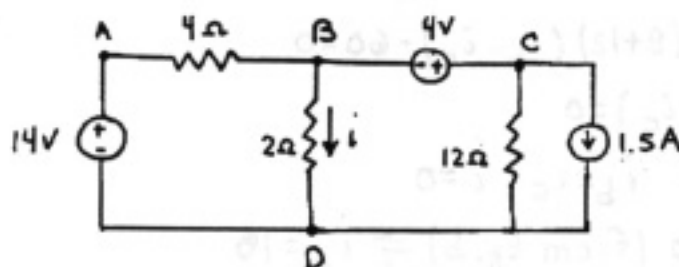3. Consider the following circuit, which is to be solved using node analysis.

(3 pts.) (a) List the essential nodes of the above circuit diagram.



Essential nodes are B, C, D.

(14 pts.) (b) Choose node D as the ground and write the required node equations in the space below.

node A:  $V_A = 14 \text{ V}$

supernode BC:  $\frac{V_A - V_B}{4} - \frac{V_B}{2} - \frac{V_C}{12} - 1.5 = 0$

supernode BC:  $V_C - V_B = 4 \text{ V}$


$\therefore 3(14 - V_B) - 6V_B - (4 + V_B) - 18 = 0 \Rightarrow V_B = 2 \text{ V}$

(3 pts.) (c) Use your node equations to find the value of  $i$ .

$i = 1 \text{ A}$

$i = V_B / 2$

4. Consider the circuit shown below.

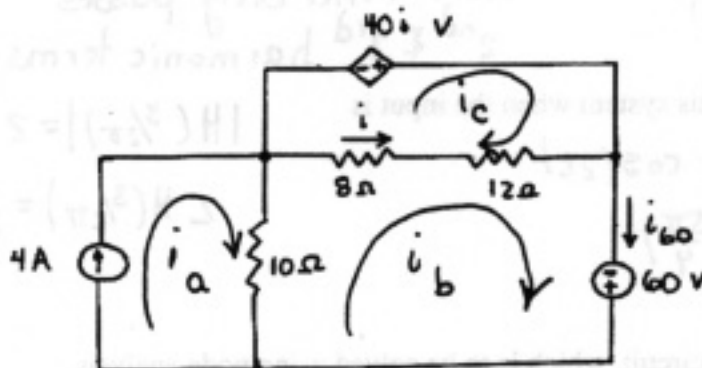

(3 pts.) (a) Draw and label the mesh currents on the above figure.

(14 Pts.) (b) Write the mesh equations in the space provided below.

Eq. a  $i_a = 4$

Eq. b  $10(i_b - i_a) + (8 + 12)(i_b - i_c) - 60 = 0$

Eq. c  $-40i - 20(i_b - i_c) = 0$


Eq. d  $i = i_b - i_c \Rightarrow i_b = i_c, i = 0$

$i_{60} = i_b, 10i_b = 100 \text{ (from Eq. b)} \Rightarrow i_b = 10$

(3 Pts.) (c) Solve the mesh equation to find the current  $i_{60}$ .

$$I_{60} = 10 \text{ A.}$$

5. Consider the following circuit.

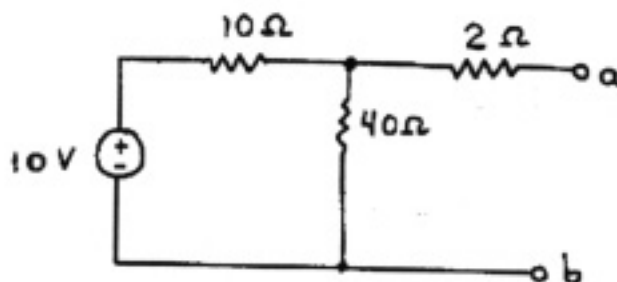


(15 pts.) Compute the Thevenin equivalent voltage and resistance.

$$V_T = 8 \text{ V.}$$

$$V_{oc} = \frac{40}{40+10} \times 10 \text{ V} = 8 \text{ V} \quad (\text{Voltage divider})$$

$$R_T = 10 \Omega.$$

$$V_T = V_{oc}$$

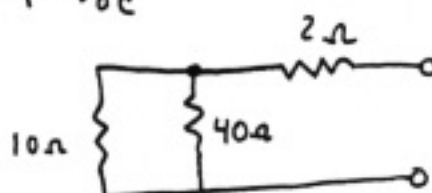

←  $R_T$

$$R_T = (10 \parallel 40) + 2 = 8 + 2 = 10 \Omega$$

(5 pts.) (b) Draw the Norton equivalent circuit in the space provided below.

$$i_{th} = V_T / R_{Th} = .8 \text{ A}$$

