
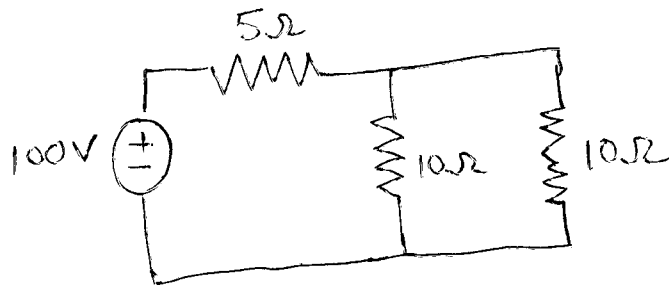


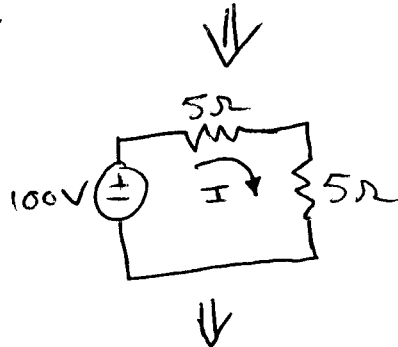1.b. (5 pts) Determine the power absorbed by the 5Ω resistor in the following circuit.



Solution




$$I = \frac{100V}{10} = 10A$$

$$P = I^2 R = (10)^2 \cdot 5 = 500W$$



$$P_2 = \underline{500W} \quad (\text{Power absorbed by } 5\Omega \text{ resistor})$$

Problem: 1 (20 pts)

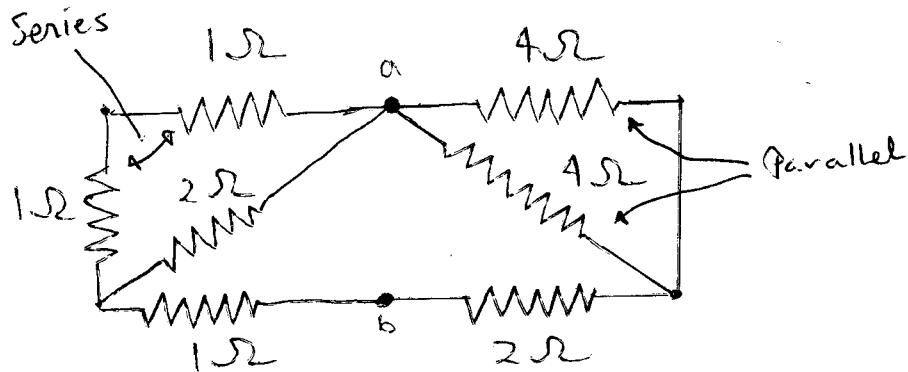- 1.a. (5 pts) Determine the equivalent resistance between terminals a and b for the following circuit.




Solution

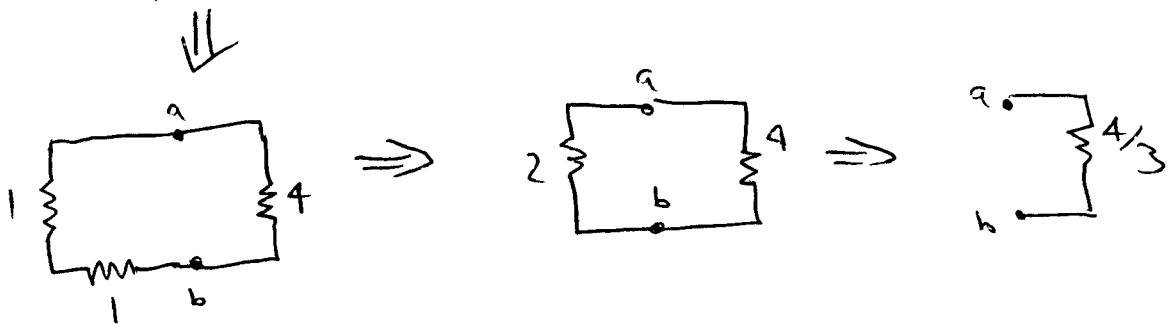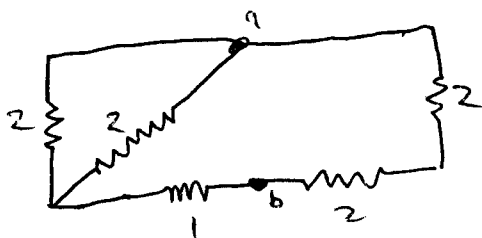


$$R_{eq} = \underline{\underline{4/3 \Omega}}$$

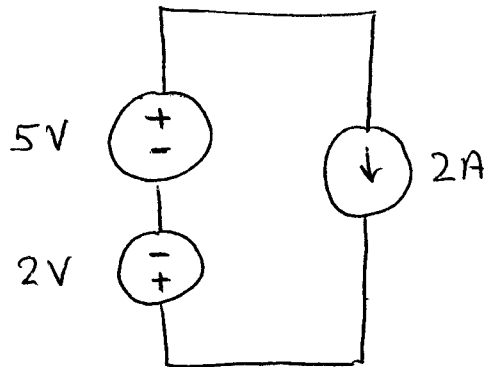1.c. (5 pts) State whether the following circuits represent valid or invalid interconnections of sources.



Circuit A

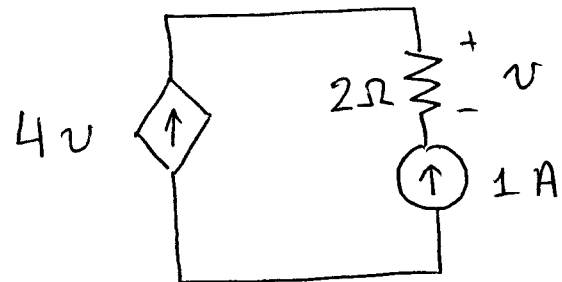

Circuit B


Solu: currents and voltages throughout circuit are consistent. Hence valid.

Solu: Dependent current source is in series with indep. current source so the currents need be the same but of opposite sign. However, using 1A source as reference, $v = -2V$ so that $4v = -8A$

Circuit A is Valid (Valid/Invalid),

Circuit B is Invalid (Valid/Invalid) $\neq -1A$

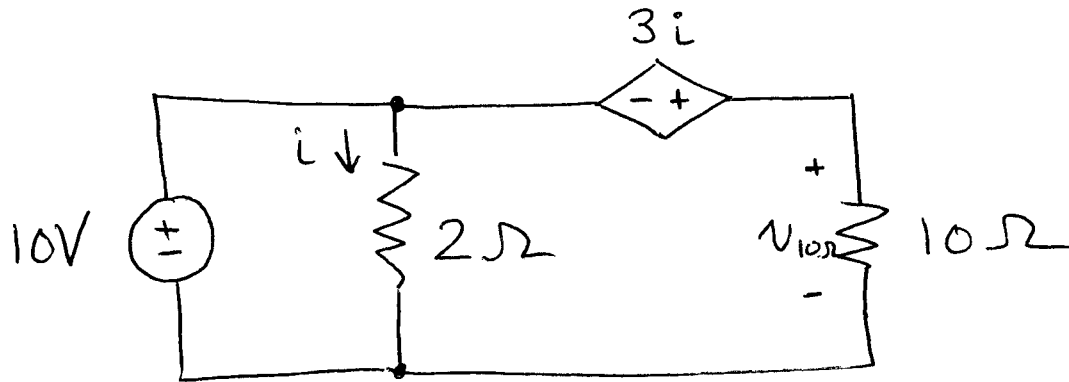1.d. (5 pts) For the circuit below, find the voltage $v_{10\Omega}$ across the 10Ω resistor.



Soln: 1) As 2Ω resistor is in parallel w/ $10V$ source

$$i = \frac{10}{2} = 5A.$$


2) Thus dependent voltage source generates $3i = 15V$
and applying KVL around outer loop:

$$-10 - 15 + v_{10\Omega} = 0 \quad \text{or} \quad v_{10\Omega} = 25V$$

$$v_{10\Omega} = \underline{25V}$$

Problem: 2 (20 pts)

Consider the following circuit:

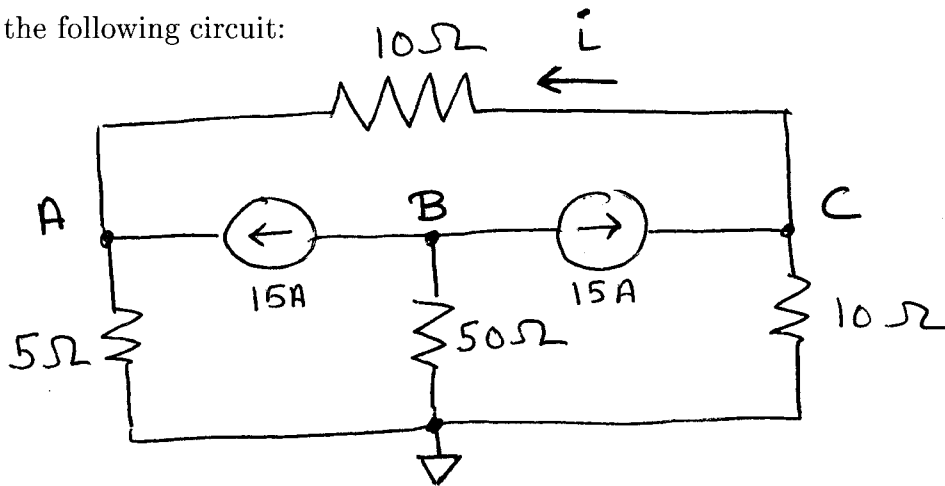

Solu:

- 2.a (5 pts): Label the essential nodes on the circuit diagram and choose a reference node.
(A, B, C as indicated plus reference node at bottom)
- 2.b (10pts) Write down the node equations and simplify.

Solu:

Apply KCL to nodes A, B, C:

$$\begin{array}{lcl}
 \text{A: } 15 - v_A/5 - \frac{v_A - v_C}{10} = 0 & \left. \begin{array}{l} \\ \\ \end{array} \right\} & \begin{array}{l} 3v_A - v_C = 150 \\ v_B = -50 \cdot 30 = -1500 \text{ V} \\ v_A - 2v_C = -150 \end{array} \\
 \text{B: } -15 - 15 - v_B/50 = 0 & & \\
 \text{C: } 15 - v_C/10 - \frac{v_C - v_A}{10} = 0 & &
 \end{array}$$

- 2.d (5 pts) Find the current i going through the 10Ω resistor on top of the circuit diagram.

Solu:

Multiply equ. A by 2 and subtract the equ. C:

$$\begin{array}{r}
 6v_A - 2v_C = 300 \\
 - \quad v_A - 2v_C = -150 \\
 \hline
 5v_A = 450
 \end{array}$$


$$\Rightarrow v_A = 90 \text{ V}, v_C = 120 \text{ V}$$

$$\text{thus: } i = \frac{v_C - v_A}{10} = 3 \text{ A}$$

$$i = \underline{\quad 3 \text{ A} \quad}$$

Problem: 3 (20 pts) Mesh analysis problem

Consider the following circuit:

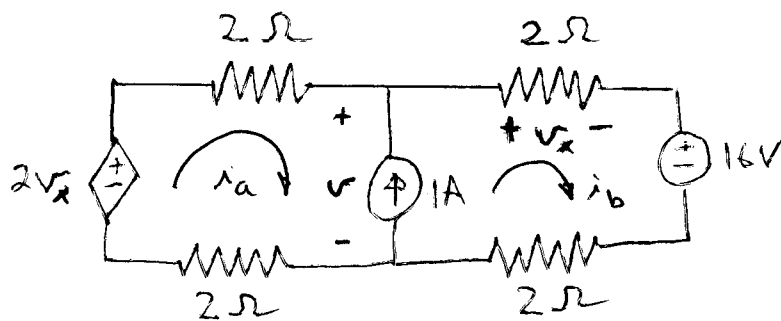

3.a (5 pts) Label the mesh currents. Are there any supermeshes?

Yes

3.b (10 pts) Write down mesh equations and simplify.

KVL around outer loop (supermesh)

$$-2v_x + 2i_a + 2i_b + 16 + 2i_b + 2i_a = 0$$

$$v_x = 2i_b$$

$$i_b - i_a = 1$$

3.c (5 pts) Solve mesh equations and find voltage v

$$-4i_b + 4i_a + 4i_b + 16 = 0$$

$$4i_a + 16 = 0 \Rightarrow i_a = -4A$$

$$i_b = i_a + 1 = -3A$$

$$v_x = 2i_b = -6V$$

$$v_x = \underline{\underline{-6V}}$$


$$v = 2i_b + 16 + 2i_b$$

$$= 4i_b + 16$$

$$= 4(-3) + 16 = 4V$$

Problem: 4 (20 pts)

Consider the following circuit:

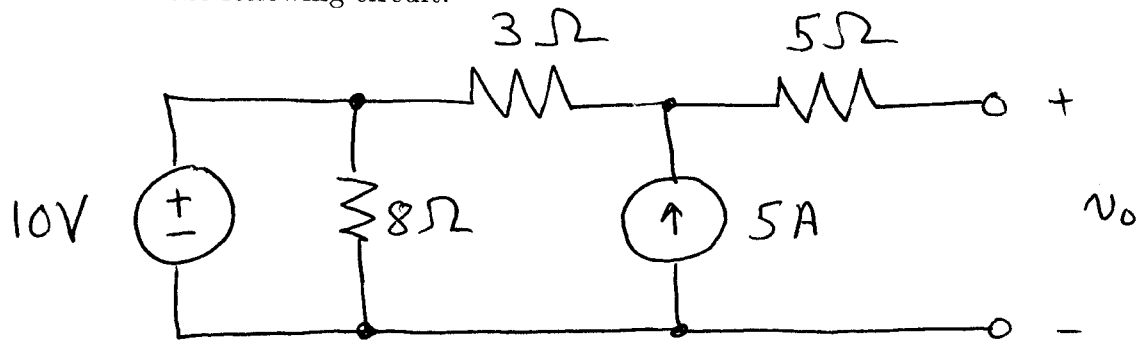


4.a (10 pts) Find the Thevenin equivalent voltage V_{th} and resistance R_{th} .

Solu.: Find $v_{open\ circuit} = v_{th}$: As zero current flows through 5Ω , v_o is the voltage drop across $5A$ source. Apply KVL around the loop containing $5A$ source, $10V$ source and 3Ω resistor to obtain (note $5A$ flows through 3Ω resistor):


$$-10 - 3(5) + v_o = 0 \Rightarrow v_o = v_{th} = 25V$$

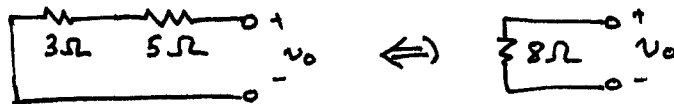To find R_{th} , turn off the sources to obtain equivalent circuit:




$$V_{th} = \underline{25V}, \quad R_{th} = \underline{8\Omega}$$

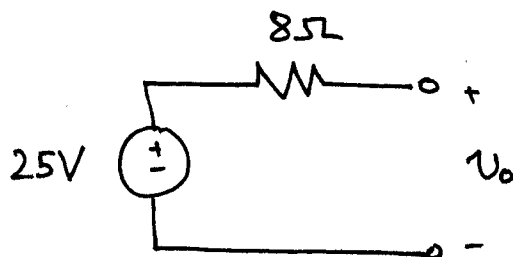4.b (10 pts) Draw the Thevenin equivalent circuit.



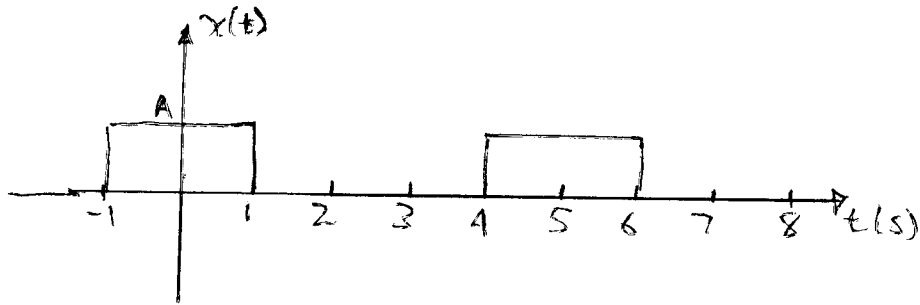Problem: 5 (20 pts) Fourier Series problem

Consider the following periodic waveform $x(t)$.



- 5.a Determine the period T , fundamental frequency f_0 and the second harmonic frequency f_2 of $x(t)$ (6 pts)



$$T = 5 \text{ s}, \quad f_0 = 1/5 \text{ Hz}, \quad f_2 = 2/5 \text{ Hz}$$

- 5.b The Fourier series representation of $x(t)$ is $x(t) = A_0 + \sum_{n=1}^{\infty} a_n \cos(2\pi n f_0 t) + b_n \sin(2\pi n f_0 t)$.

Determine whether each statement is true or false (5pts):

Statement	True	False
$b_n = 0$ for all n .	☒	☐
$b_n = 0$ only for odd n .	☐	☒
$a_n = 0$ for all n	☐	☒
$A_0 < 0$	☐	☒
The average value of $x(t)$ is $2A/5$.	☒	☐

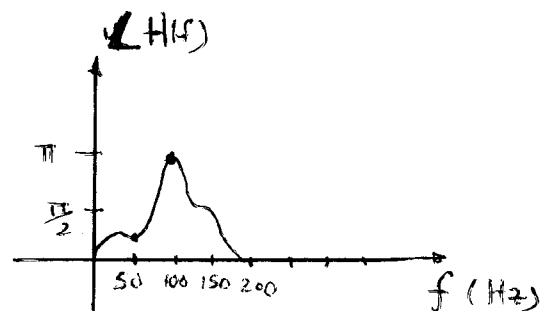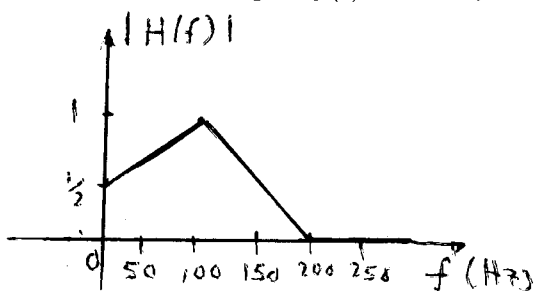- 5.c The signal $x(t) = 10 + 12 \cos(2\pi 100t) + 3 \sin(2\pi 200t)$ is the input to a linear time invariant system with transfer function (magnitude and phase) shown below. Determine the output $y(t)$ of the system (9 pts.).



$$y(t) = 5 + 12 \cos(2\pi 100t + \pi)$$