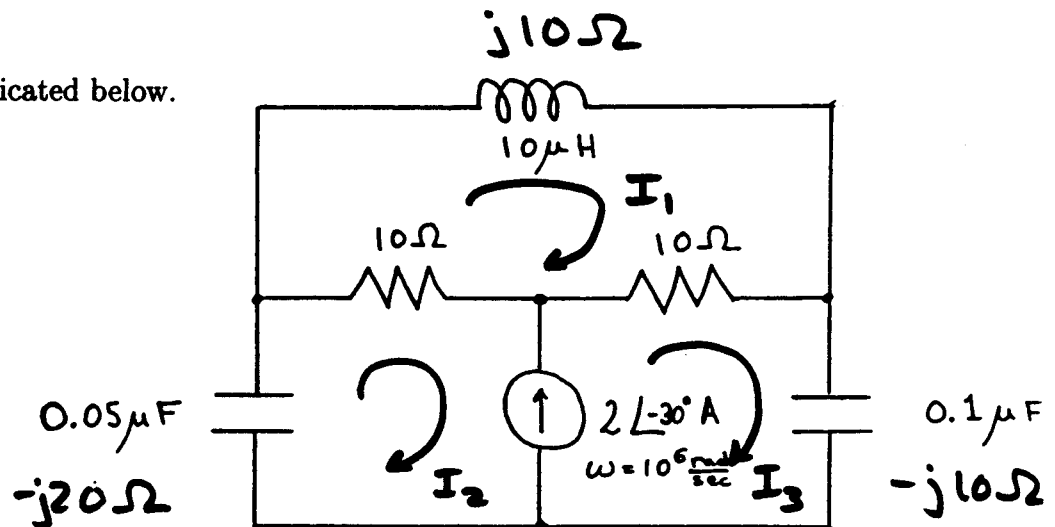


Problem 1 (16 pts):

Consider the circuit indicated below.



1.a (2 pts) Draw and label the mesh currents on the above circuit.

1.b (12 pts) Write down the mesh equations.

Mesh 1 : $10(I_1 - I_2) + j10I_1 + 10(I_1 - I_3) = 0$

Mesh Equations :

Supermesh : $-j20I_2 + 10(I_2 - I_1) + 10(I_3 - I_1) - j10I_3 = 0$

Current branch: $I_3 - I_2 = 2\angle-30^\circ$


1.c (2 pts) Express the mesh equations in matrix form.

Matrix Form :

$$\begin{bmatrix} 2+j & -1 & -1 \\ -2 & 1-2j & 1-j \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 2\angle-30^\circ \end{bmatrix}$$

Problem 2 (16 pts):

Consider the circuit indicated below.

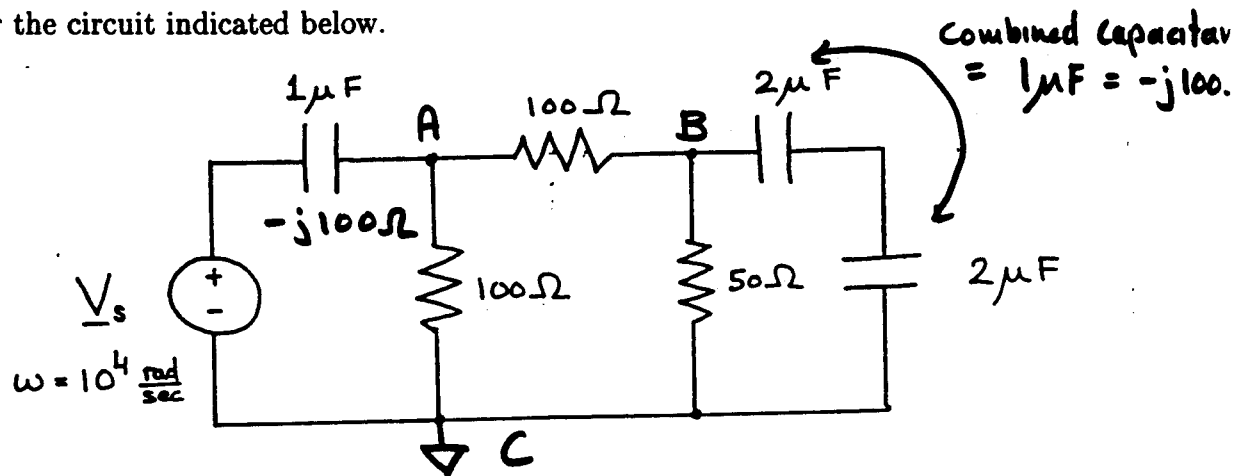

2.a (2 pts) Label the essential nodes. *Choose C as ref. node.*

2.b (12 pts) write the node equations.

Node Equations :

node A

$$(\underline{V}_A - \underline{V}_s) j \cdot 01 + \underline{V}_A \cdot 01 + (\underline{V}_A - \underline{V}_B) \cdot 01 = 0$$

node B

$$(\underline{V}_B - \underline{V}_A) \cdot 01 + \underline{V}_B \cdot 02 + \underline{V}_B j \cdot 01 = 0$$

2.c (2 pts) Express the node equations in matrix form.

Matrix Form :

$$\begin{bmatrix} 2+j & -1 \\ -1 & 3+j \end{bmatrix} \begin{bmatrix} \underline{V}_A \\ \underline{V}_B \end{bmatrix} = \begin{bmatrix} j\underline{V}_s \\ 0 \end{bmatrix}$$

Problem 3 (16 pts)


Consider the following system transfer function

$$H(s) = \frac{10^4 s}{s^2 + (10^2 + 10^3)s + 10^5}$$

- 3.a (12 pts): Sketch the asymptotic magnitude Bode plot of $|H(j\omega)|$ over the range $1 \leq \omega \leq 10^4$.

First put into standard factored form:
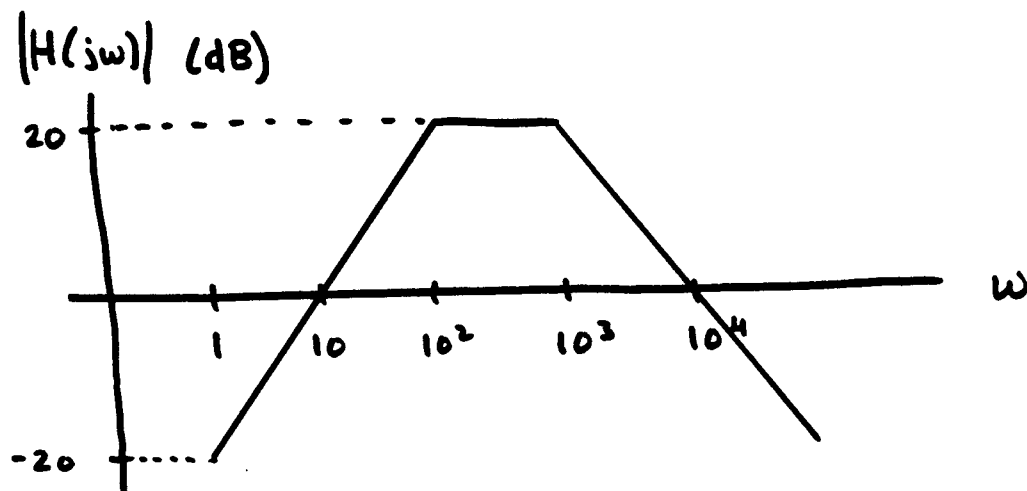
$$H(s) = \frac{10^4 s}{(s + 10^2)(s + 10^3)} = \frac{1}{10} \frac{s}{(1 + s/10^2)(1 + s/10^3)}$$




- 3.b (4pts) What kind of filter is this (Lowpass, highpass, bandpass, bandreject, none of the above).

Kind of filter :

BPF

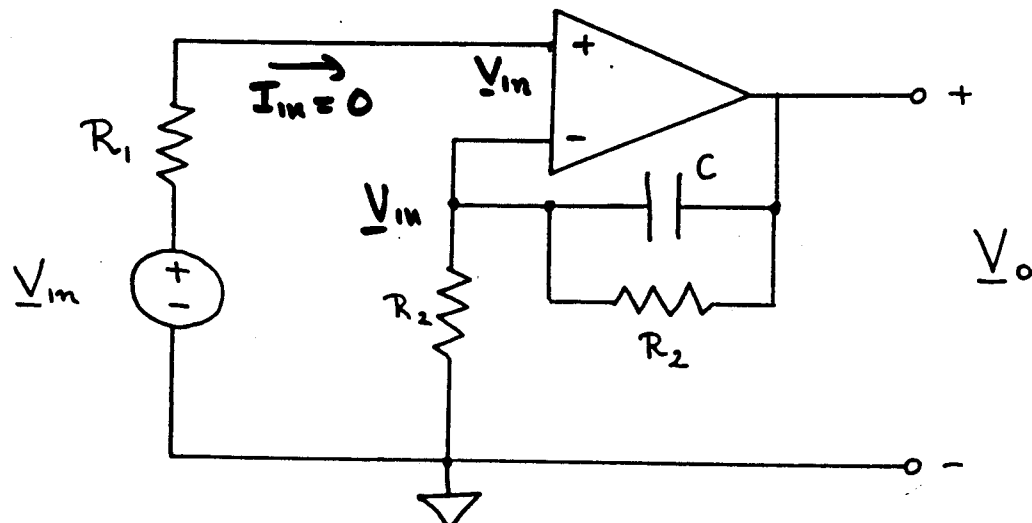Problem 4 (16 pts):

Consider the following Op-Amp circuit (Assume that Op-Amp is ideal and not in saturation):



4.a (12 pts) Use the Golden rules and circuit analysis to derive the transfer function $H(s) = \underline{V_o} / \underline{V_{in}} (s = j\omega)$.

GR#2 : "+" terminal of op amp draws 0 current $\Rightarrow \underline{V_+} = \underline{V_{in}}$

GR#1 : $\underline{V_+} = \underline{V_-} \Rightarrow \underline{V_-} = \underline{V_{in}}$

Hence, applying GR#2 again to "-" terminal of op-amp, by Voltage divider formula: $\underline{V_{in}} = \frac{R_2}{R_2 + C \parallel R_2} \underline{V_o}$

$$\Rightarrow H(s) = \frac{R_2 + C \parallel R_2}{R_2} = \frac{R_2 + R_2 / (1 + sR_2C)}{R_2} = \frac{2 + R_2Cs}{1 + R_2Cs}$$

$H(s) =$


$$\frac{2 + R_2Cs}{1 + R_2Cs}$$

4.b (4 pts) When $R_1 = 1K\Omega$, $R_2 = 100K\Omega$ and $C = 1\mu F$, the circuit's magnitude transfer function $|H(j\omega)|$ has the Bode plot shown below. If R_1 is replaced by $10K\Omega$, R_2 is replaced by $R_2 = 1M\Omega$ and C is replaced by $0.01\mu F$ what is the frequency ω_1 (in rad/sec) for which the new circuit has $|H(j\omega_1)| = 2\text{dB}$?

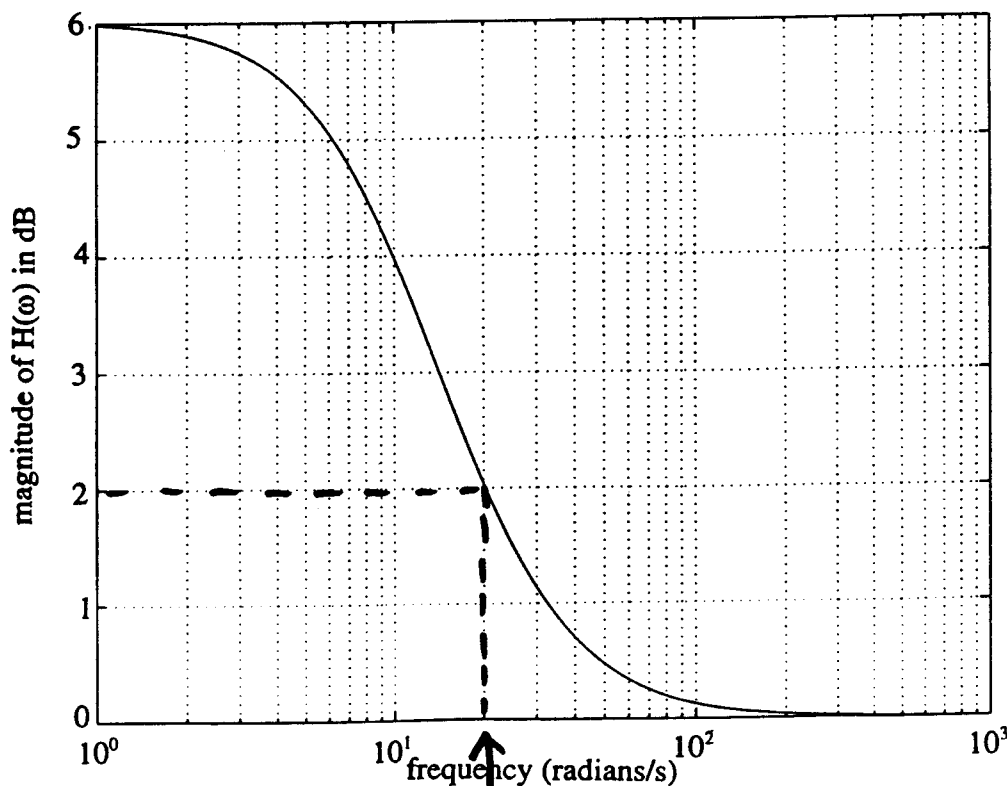1. Magnitude (impedance) scaling: $R'_1 = 10R_1$, $R'_2 = 10R_2 \Rightarrow k_m = 10$
To obtain equiv. $H(j\omega)$: $C' = \frac{1}{k_m} C = \frac{1}{10} 1\mu F = 0.1\mu F$
2. Frequency scaling: $C'' = 0.01\mu F = \frac{1}{k_f} C' \Rightarrow k_f = 10$

Thus $\omega_1^{\text{new}} \rightarrow 10\omega_1^{\text{old}}$
 $= 10(20)$
 $= 200$


$\omega_1 = \boxed{200 \frac{\text{rad}}{\text{sec}}}$



$\omega_1 = 20 \frac{\text{rad}}{\text{sec}}$

Problem: 5 (16 pts)

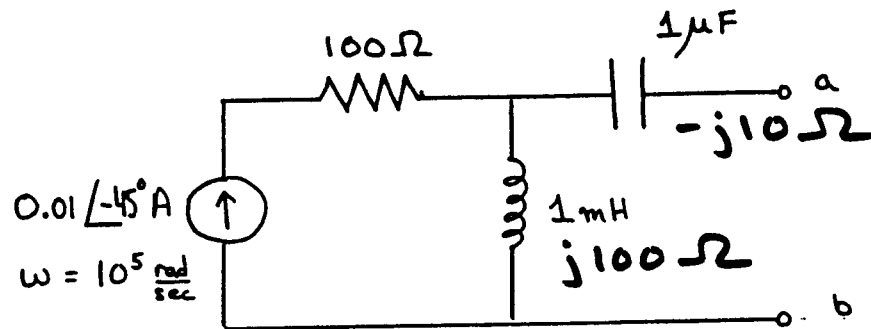5.a (8 pts) Consider the circuit below. Find the Thevenin equivalent voltage V_{th} and Thevenin equivalent impedance Z_{th} . Draw the Thevenin equivalent circuit.




$$V_{th} = V_{ab}^{oc} = (0.01 \angle -45^\circ)(j100) = 1 \angle +45^\circ$$

(Note: 0 current thru
 1μ F capacitor)


$$Z_{th} = -j10 + j100 = j90 \Omega \quad (\text{open current source removes } 100 \Omega \text{ from } Z_{th})$$

$$V_{th} = \boxed{1 \angle 45^\circ \text{ V}}, \quad Z_{th} = \boxed{j90 \Omega}$$

Equivalent circuit

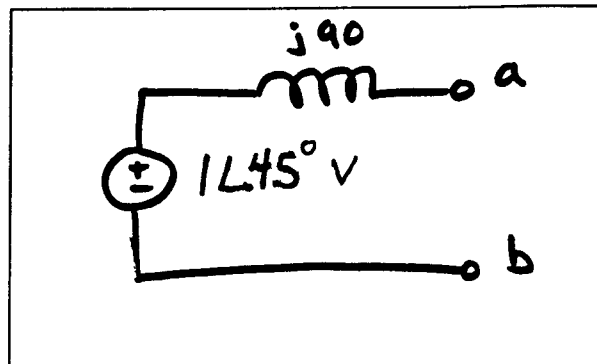


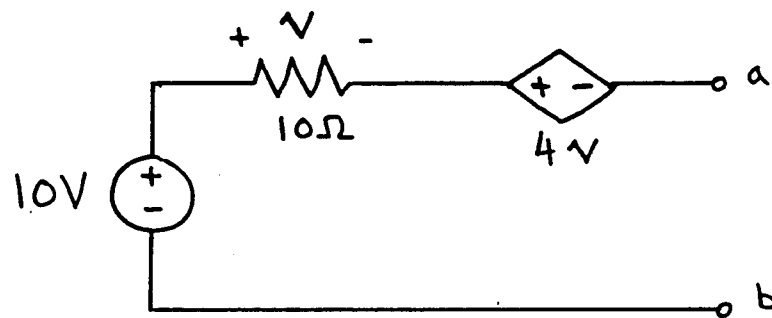5.b (8 pts) Consider the circuit below. Find the Thevenin equivalent voltage V_{th} and Thevenin impedance Z_{th} . Draw the Thevenin equivalent circuit.



i). $V_{th} = V_{ab}^{oc} = 10V$ (no current flows through 10Ω so $v = 0$)

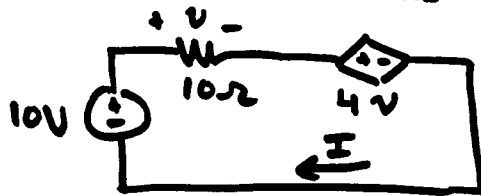ii). $Z_{th} = V_{ab}^{oc} / I_{ab}^{sc}$. $I_{ab}^{sc} = I$ found by KVL around loop




$$-10 + 5v = 0, \quad v = IR = 10I$$

$$\Rightarrow I = \frac{1}{5} = 0.2A. \quad \therefore Z_{th} = \frac{10}{1/5} = 50$$

$V_{th} =$ 10V , $Z_{th} =$ 50Ω

Equivalent circuit

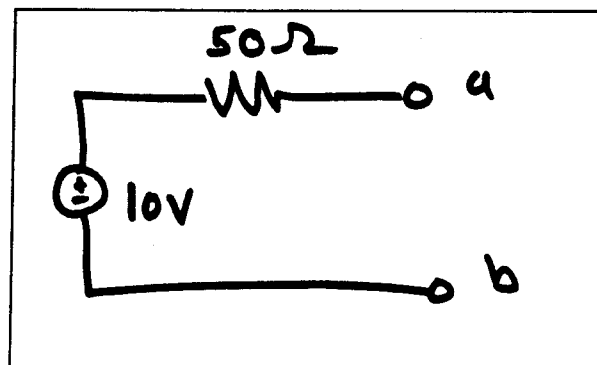

Problem: 6 (16 pts)

A voltage waveform $x(t)$ has the following Fourier series representation

$$x(t) = 2 + \sum_{n=1}^{\infty} \frac{1 + (-1)^n}{2n} \cos(\overset{100}{200}\pi n t + \pi/n) \quad (V)$$

note: odd harmonics are zero.

6.a (2 pts) What is the fundamental frequency (in Hz) of $x(t)$?

$$100 \pi n t = \underbrace{50}_{f} 2 \pi n t$$


$$f = \boxed{50 \text{ Hz}}$$

6.b (2 pts) What is the D.C. value of $x(t)$?

$$V_{D.C.} = \boxed{2}$$

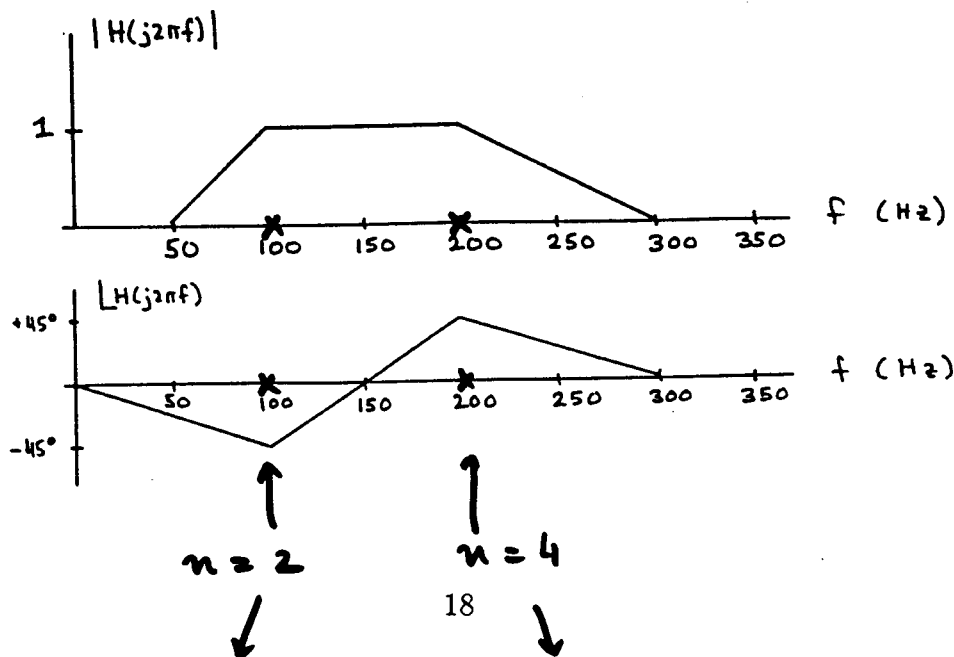6.b (12 pts) A filter has the magnitude and phase response shown in the plot below. Find the output $y(t)$ when the input to the filter is $x(t)$ above.

$$y(t) = \boxed{\frac{1}{2} \cos(200\pi t + 45^\circ) + \frac{1}{4} \cos(400\pi t + 90^\circ)}$$



Harmonic :

Freq. component:
at input of H

$$\frac{1}{2} \cos(200\pi t + 90^\circ)$$

$$\frac{1}{4} \cos(400\pi t + 45^\circ)$$