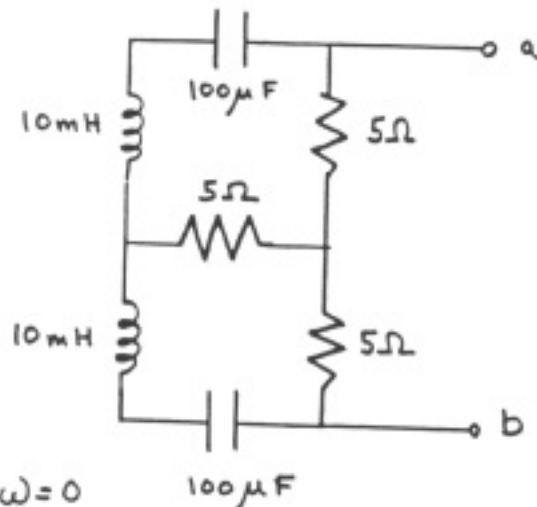


F99 EEC S 210

Midterm #2 Solutions

Problem: 1 (20 pts)


- 1.a. (5 pts) Consider the circuit indicated below. Find the impedance across terminals a, b of the circuit for $\omega = 0$ (D.C.) and the impedance for $\omega = \infty$.



$$Z_C = \frac{1}{j\omega C} = -j\infty @ \omega = 0$$

$$Z_L = j\omega L = j\infty @ \omega = \infty$$


$\therefore$ at either $\omega = 0$ or $\omega = \infty$ series combination of L & C has $|Z_{L+C}| = \infty \Rightarrow$ open-circuit. Thus the above circuit reduces to

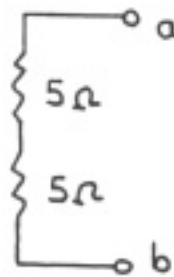

$$Z_{\omega=0} = \underline{10 \Omega}, \quad Z_{\omega=\infty} = \underline{10 \Omega}$$

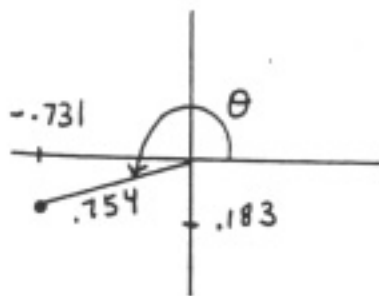1.b. (5 pts) Express the complex variable W below in both polar and rectangular form

$$\begin{aligned}
 W &= \frac{e^{j\pi/3} - 2e^{j\pi/4}}{1+j} \\
 &= \frac{e^{j\pi/3} - 2e^{j\pi/4}}{\sqrt{2} e^{j\pi/4}} \\
 &= \frac{1}{\sqrt{2}} e^{j\pi/2} - \sqrt{2} \\
 &= \frac{1}{\sqrt{2}} (\cos \pi/2 + j \sin \pi/2) - \sqrt{2} \\
 &= .683 + j.183 - \sqrt{2} \\
 &= -.731 + j.183
 \end{aligned}$$



$$r = [(0.731)^2 + (.183)^2]^{1/2} = .754$$

$$\begin{aligned}
 \theta &= \tan^{-1} \left(\frac{.183}{-.731} \right) = 194.055^\circ \\
 &\text{or } -165.945^\circ
 \end{aligned}$$

$$W = \underline{0.754 \angle 194.055^\circ} \text{ (polar form),}$$


$$W = \underline{-0.731 + j.183} \text{ (rectangular form)}$$

1.c. (5 pts) Use phasors to find the quantities A and θ defined by

$$\begin{aligned}\cos(10t + \pi/4) - \sin(10t + \pi/6) &= A \cos(10t + \theta) \\&= \cos(10t + \pi/4) + \cos(10t + \frac{\pi}{6} + \frac{\pi}{2}) \\&= e^{j\pi/4} + e^{j2\pi/3} \\&= \frac{1}{\sqrt{2}} (1+j) + (-\frac{1}{2} + j\frac{\sqrt{3}}{2}) \\&= 0.207 + j1.573 \\ \therefore r &= [(0.207)^2 + (1.573)^2]^{1/2} = 1.587 \\ \theta &= \tan^{-1} \left[\frac{1.573}{0.207} \right] = 1.44 \text{ rad} \\ &\quad (82.5^\circ)\end{aligned}$$

$$A = \underline{1.587}, \quad \theta = \underline{82.5^\circ (1.44 \text{ rad})}$$

1.d. (5 pts) Consider the device below:

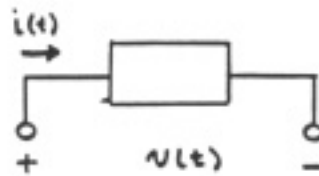

where the voltage $v(t)$ and the current $i(t)$ are

$$v(t) = 2 \cos(\omega t + \pi/3)$$

$$i(t) = \cos(\omega t + \pi/4)$$

Find the impedance Z of the device and the average power P dissipated by the device for $\omega = 20$ rad/sec.

$$\underline{V} = 2 \angle \pi/3$$

$$\underline{I} = 1 \angle \pi/4$$


$$\underline{Z} = \frac{\underline{V}}{\underline{I}} = 2 \angle \pi/12 = 1.932 + j0.518 \Omega$$

$$P = \frac{1}{2} \operatorname{Re}[\underline{V} \cdot \underline{I}^*] = \frac{1}{2} \operatorname{Re}[2 \angle \pi/12] = 0.966 \text{ W}$$

$$\underline{Z} = \underline{1.932 + j0.518 \Omega}, \quad P = \underline{0.966 \text{ W}}$$

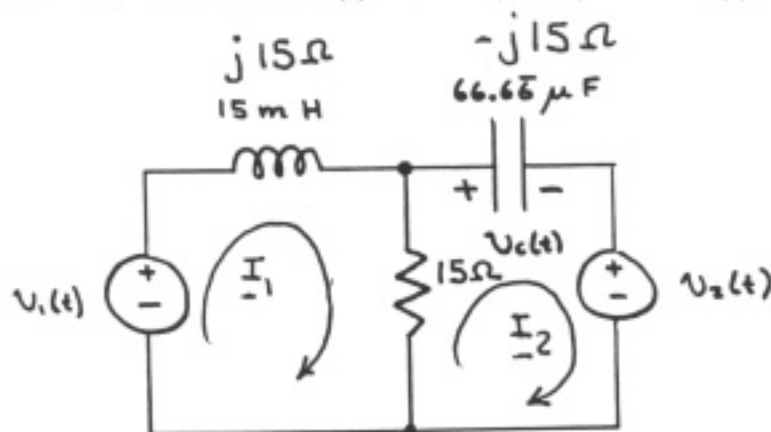Problem: 2 (20 pts)

Consider the following circuit where $v_1(t) = 30 \cos(1000t)$ V and $v_2(t) = 30 \cos(1000t - 90^\circ)$ V:



2.a (5 pts): Draw and label the mesh currents on the circuit diagram.

2.b (10pts) Write down the mesh equations.

$$\text{mesh 1} \quad -30 + j15\mathbf{I}_1 + 15(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$15(\mathbf{I}_2 - \mathbf{I}_1) - j15\mathbf{I}_2 - 30j = 0$$

$$\begin{bmatrix} 15(1+j) & -15 \\ -15 & 15(1-j) \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 30 \\ 30j \end{bmatrix}$$

2.c (5 pts) Solve the mesh equations and find $v_c(t)$.

$$\therefore (1+j)\mathbf{I}_1 - \mathbf{I}_2 = 2$$

$$\mathbf{I}_1 - (1-j)\mathbf{I}_2 = -2j$$


$$\therefore \mathbf{I}_1 = 2 \text{ A} \quad \& \quad \mathbf{I}_2 = 2j \text{ A}$$

$$\mathbf{V}_c = (-j15)(\mathbf{I}_2) = 30 \text{ V}$$

$$v_c(t) = \underline{30 \cos(1000t)} \text{ V}$$

Problem: 3 (20 pts)

Consider the following circuit:

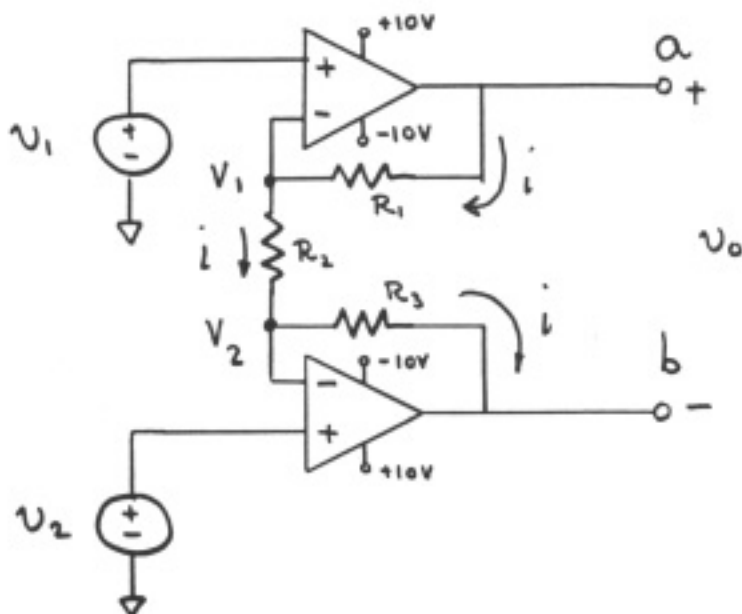

- 3.a (10 pts) Assume that the Op-Amp is ideal and not in saturation. Find the output voltage v_o in terms of the input voltages v_1 , v_2 , and resistances R_1 , R_2 and R_3 .

By Golden Rule #1 $i = (V_1 - V_2) / R_2$

By Golden Rule #2 $i = V_o / (R_1 + R_2 + R_3)$

$$\therefore \frac{V_1 - V_2}{R_2} = \frac{V_o}{R_1 + R_2 + R_3} \implies V_o = \frac{R_1 + R_2 + R_3}{R_2} (V_1 - V_2)$$

$$v_o = \frac{R_1 + R_2 + R_3}{R_2} (V_1 - V_2)$$

- 3.b (10 pts) If $v_2 = 0$ and if $R_1 = R_2 = R_3 = 1000\Omega$ determine how large v_1 can be before the top Op-Amp saturates.

Note: $v_2 = 0$. Thus by a voltage divider $V_1 = \frac{R_2}{R_1 + R_2} V_a$


saturation occurs for $V_a > 10V$

$$\therefore \max V_1 = 5V$$

$$\max v_1 = 5V$$

Problem: 4 (20 pts)


Consider the following circuit:

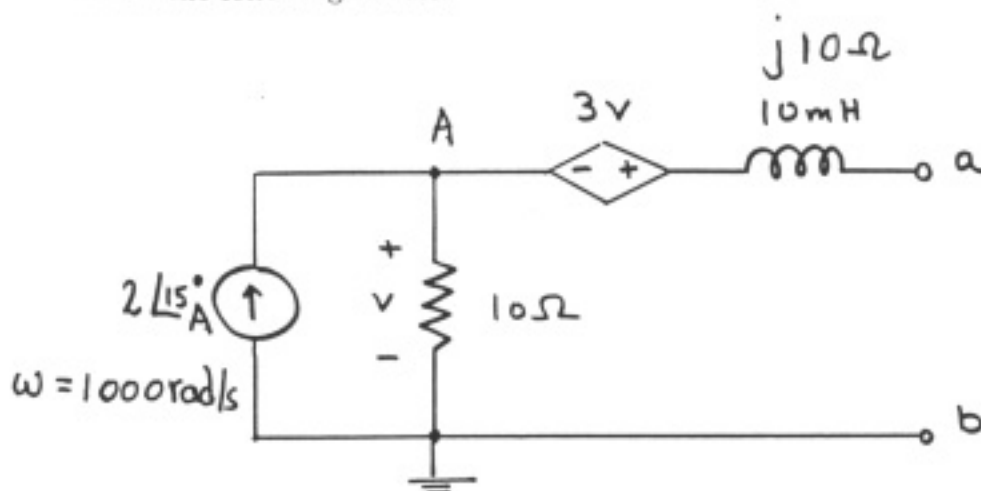

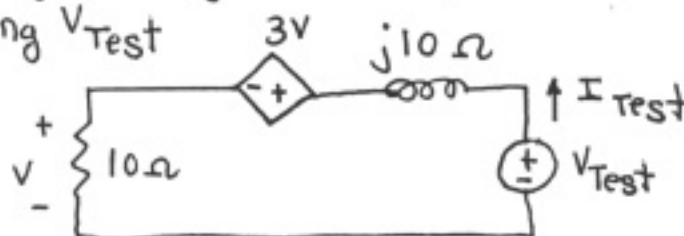4.a (15 pts) Find the Thevenin equivalent voltage V_{th} and impedance Z_{th} .

$$V_T = V_{oc} = V_A + 3V = 4V_A = (4 \times 2 \angle 15^\circ) \times 10 = 80 \angle 15^\circ V$$

Find Z_T by turning off independent current source & applying V_{Test}



$$V_{th} = 80 \angle 15^\circ, \quad Z_{th} = 40 + j10\Omega$$


4.b (5 pts) Draw the Thevenin equivalent circuit.

Apply KVL $\therefore -V - 3V - (j10)I_{Test} + V_{Test} = 0$

$$V = 10 I_{Test}$$


$$\therefore -40 I_{Test} - j10 I_{Test} + V_{Test} = 0$$
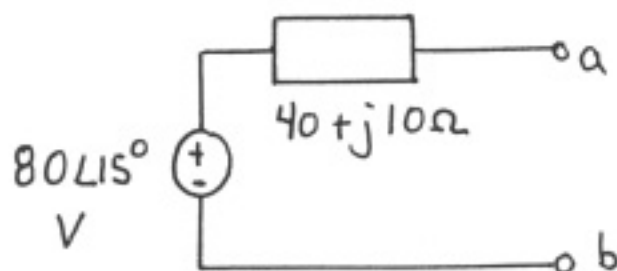
$$Z_{th} = \frac{V_{Test}}{I_{Test}} = 40 + j10\Omega$$



Alternate method for finding Z_T .

Find I_{sc}

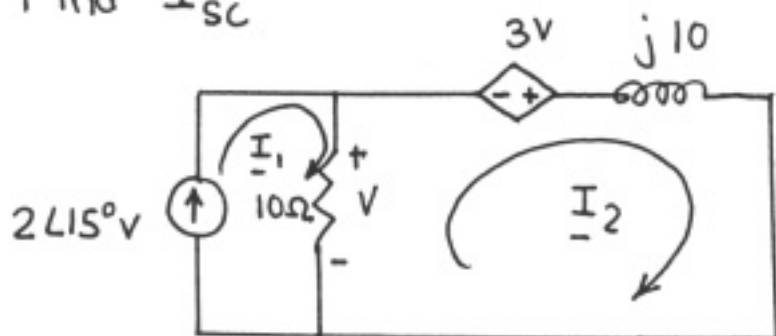

$$\text{mesh 1} \quad \underline{I}_1 = 2 \angle 15^\circ$$

$$\text{mesh 2} \quad (\underline{I}_2 - \underline{I}_1)10 - 3V + j10\underline{I}_2 = 0$$

$$\underline{V} = 10(\underline{I}_1 - \underline{I}_2)$$

$$\therefore 10(\underline{I}_2 - \underline{I}_1) - 30(\underline{I}_1 - \underline{I}_2) + j10\underline{I}_2 = 0$$


substitute $\underline{I}_1 = 2 \angle 15^\circ$ in above equation to get

$$\underline{I}_{sc} = \underline{I}_2 = \frac{80 \angle 15^\circ}{40 + j10}$$

$$Z_T = \frac{\underline{V}_{oc}}{\underline{I}_{sc}} = \frac{80 \angle 15^\circ}{\frac{80 \angle 15^\circ}{40 + j10}} = 40 + j10 \Omega$$

Problem: 5 (20 pts)

Consider the following Op-Amp circuit:

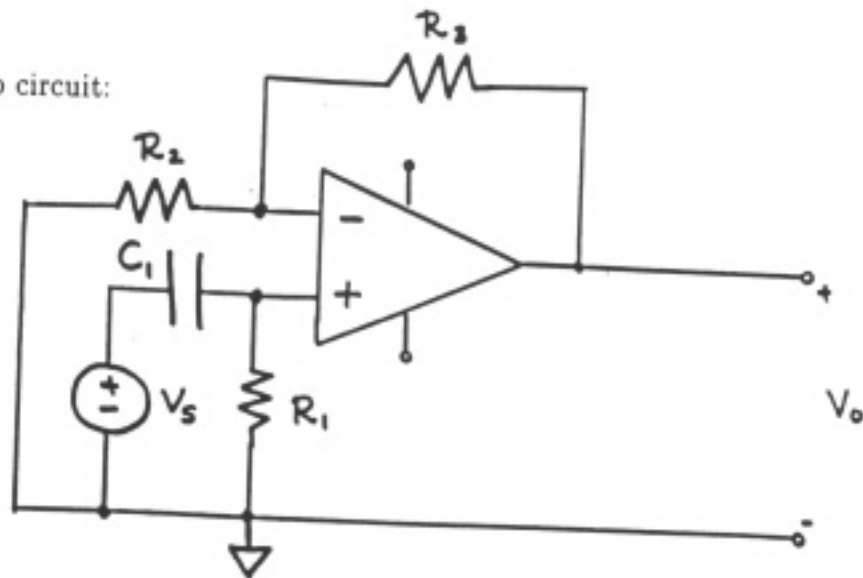

Assume that the Op-Amp is ideal and not in saturation. Compute the transfer function $H(j\omega)$ for $v_o(t)/v_s(t)$

$$V_{(+)} = \frac{R_1}{R_1 + \frac{1}{j\omega C_1}} V_s = \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} V_s \quad (\text{voltage divider})$$

KCL @ (-) terminal

$$V_{(-)} = V_{(+)} \quad (\text{Golden Rule \#1})$$

$$\frac{0 - V_{(-)}}{R_2} + \frac{V_o - V_{(-)}}{R_3} = 0$$

$$\therefore V_o = \left(1 + \frac{R_3}{R_2}\right) V_{(-)} = \left(1 + \frac{R_3}{R_2}\right) \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1}$$

$$H(j\omega) = \frac{\left(1 + \frac{R_3}{R_2}\right) j\omega R_1 C_1}{1 + j\omega R_1 C_1}$$