

**EECS 210 – Final – 12/17/98**  
**Closed book, no notes, calculators are allowed, 2 hours**


Name: \_\_\_\_\_

Lecture Section: 2

I have neither given nor received aid on this exam, nor have I concealed any violation of the Honor Code.


Signature: \_\_\_\_\_

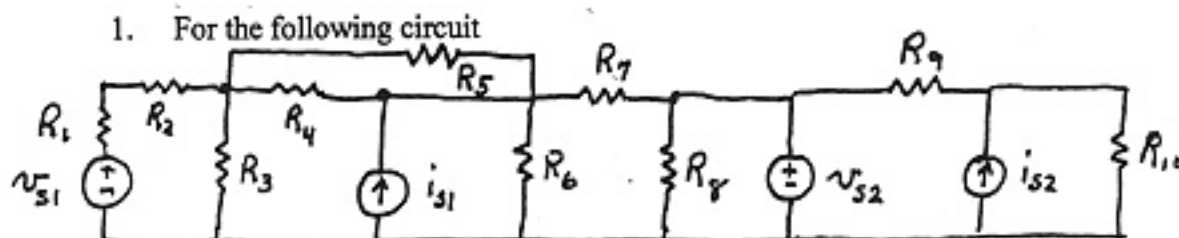Please present analyses and solutions to the following problems in your blue book. Your final answers should be designated by drawing boxes around them. Please include your name and lecture section on the cover of the blue book.




- 3 % (a) List all pairs of resistors that are in series (e.g.,  $R_1$  &  $R_2$ , etc.)
- 3 % (b) List all pairs of resistors that are in parallel
- 3 % (c) List all pairs consisting of a source and a resistor that can be considered to be in Norton form
- 3 % (d) List all pairs consisting of a source and a resistor that can be considered to be in Thevenin form

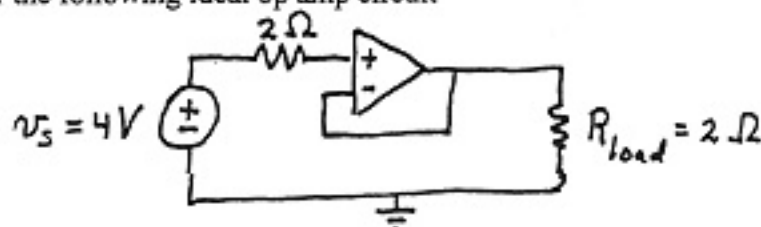2. For the following ideal op amp circuit




- 4 % (a) What is the power being supplied by the source (in watts)?
- 4 % (b) What is the power being supplied by the op amp (in watts)?
- 5 % 3. A 2 ohm resistor is in parallel with a  $1/4$  F capacitor. The voltage across the pair is  $v(t) = 4 \sin(2t)$  V. What is the average dissipated power (in watts)?

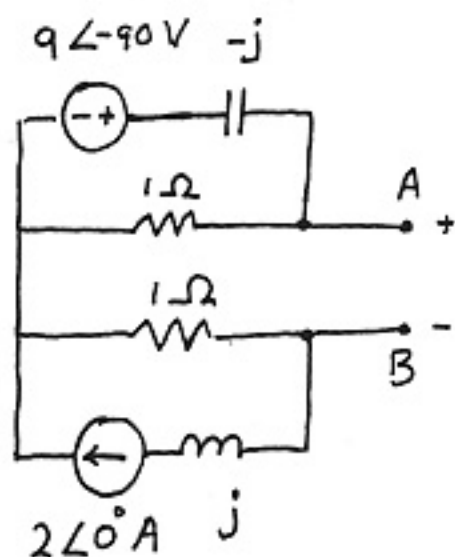- 20 % 4. Replace the circuit between A and B with the phasor form of its Thevenin equivalent circuit. Show the amplitude and phase angle of the Thevenin equivalent voltage,  $V_T$ , and the amplitude and phase angle of the source impedance,  $Z_T$ ?



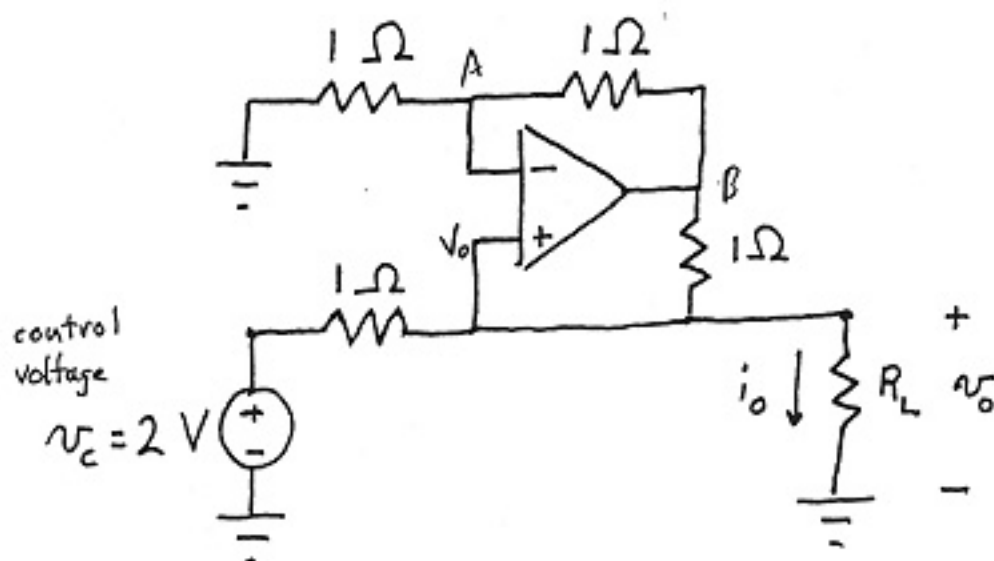- 20 % 5. The following circuit is an example of a voltage controlled current source. Within the linear range of the op amp, you will find that the output current is independent of the choice of load resistance  $R_L$ . What is the current  $i_o$  for a control voltage of 2 V (in amps)?



6. A signal  $x(t)$  can be represented by the following sum

$$x(t) = 3 + \sum_{n=1}^{\infty} \frac{1}{n^2} \cos(2000\pi n t)$$

- 4% (a) What is the period of this signal?  
 4% (b) What is the dc value of this signal?

When the signal  $x(t)$  is the input to a certain filter, the output of the filter is

$$y(t) = 5 + 3 \cos(2000\pi t) + \frac{1}{90} \cos(6000\pi t + 60^\circ)$$

- 6% (c) What are the gain and the phase shift of the frequency response of this filter at frequency 3 kHz?  
 6% (d) Find the output  $y(t)$  of this filter when the input signal is  
 $x(t) = \sin(2000\pi t) + 4 \cos(4000\pi t) + 6 \sin(6000\pi t + 45^\circ)$

7. Given  $H(j\omega) = \frac{j\omega}{j\omega + 1} \frac{2}{j\omega + 2}$

- 5% (a) What kind of filter has this frequency response (low pass, high pass, band pass, notch)?  
 10% (b) Design a filter with this frequency response.

## EECS 210 – Final – 12/21/98

Closed book, no notes, calculators are allowed, 2 hours

Name: \_\_\_\_\_


Lecture Section: 1

I have neither given nor received aid on this exam, nor have I concealed any violation of the Honor Code.

Signature: \_\_\_\_\_


Please present analyses and solutions to the following problems in your blue book. **Your final answers should be designated by drawing boxes around them.** Please include your name and lecture section on the cover of the blue book. Do not worry that your exam sheet and blue book might become separated.

1. For the following circuit

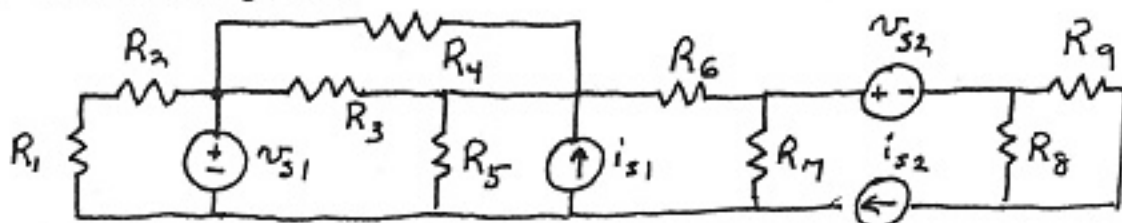


- 3% (a) List all pairs of resistors that are in series (e.g.,  $R_1$  &  $R_2$ , etc.)
- 3% (b) List all pairs of resistors that are in parallel
- 3% (c) List all combinations consisting of a source and one or more resistors that can be considered to be in Norton form
- 3% (d) List all combinations consisting of a source and one or more resistors that can be considered to be in Thevenin form

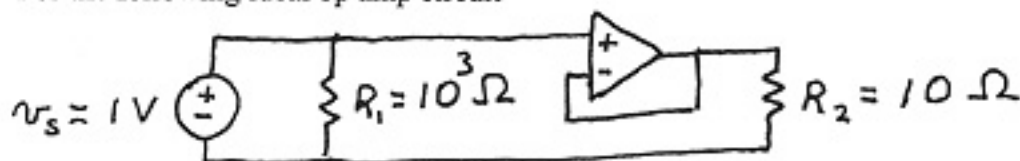2. For the following ideal op amp circuit




- 4% (a) What is the power being supplied by the source  $v_s$  (in watts)?
- 4% (b) What is the power being supplied by the op amp (in watts)?
- 5% 3. A 2 ohm resistor is in series with a  $1/4$  F capacitor. The current through the pair is  $i(t) = 4 \sin(2t)$  A. What is the average dissipated power (in watts)?

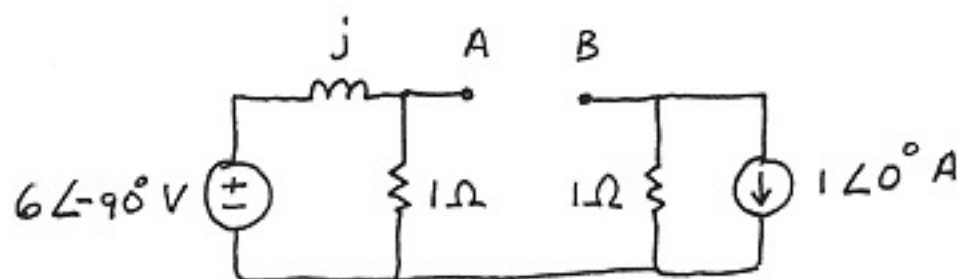- 20% 4. Replace the circuit between A and B with the phasor form of its Thevenin equivalent circuit. Show the amplitude and phase angle of the Thevenin equivalent voltage,  $\underline{V}_T$ , and the amplitude and phase angle of the source impedance,  $\underline{Z}_T$ ?



- 20% 5. The following circuit acts as a capacitance multiplier. The effective impedance between terminals A and B looks like that of a capacitor that is larger than the capacitor in the circuit. For a voltage source,  $\underline{V}_s = 1\angle 0^\circ$ , placed across terminals A and B as shown, what is the effective impedance,  $\underline{Z}_{eff} = \underline{V}_s / \underline{I}_s$  (in ohms)?

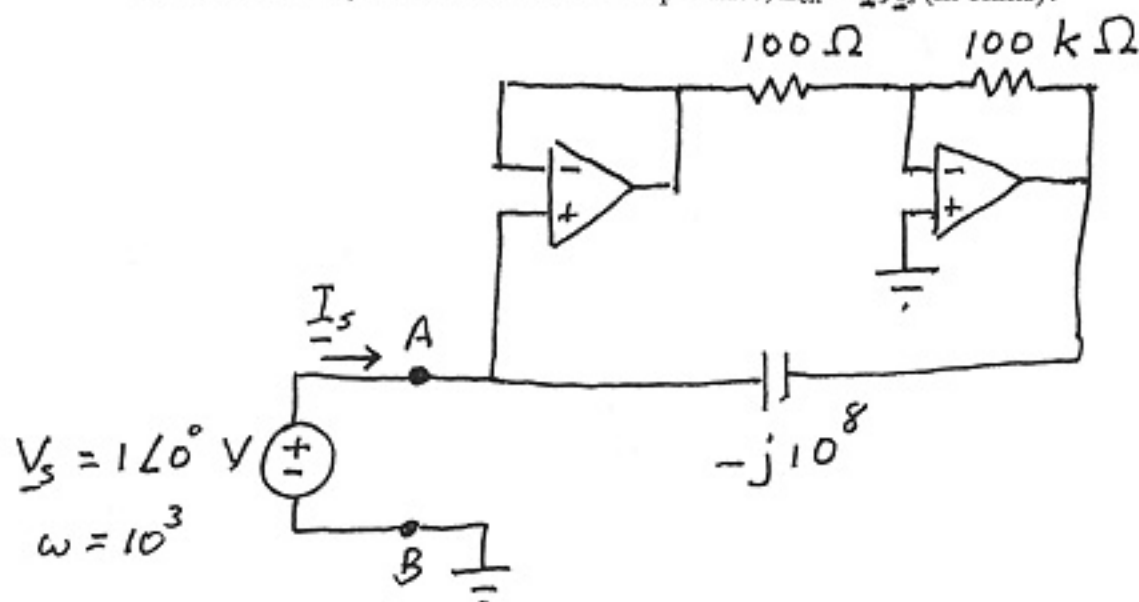

6. A signal  $x(t)$  can be represented by the following sum

$$x(t) = 5 + \sum_{n=1}^{\infty} \frac{1}{n^3} \cos(1000\pi nt)$$

- 4% (a) What is the period of this signal?
- 4% (b) What is the dc value of this signal?

When the signal  $x(t)$  is the input to a certain filter, the output of the filter is

$$y(t) = \frac{1}{6} \cos(1000\pi t + 30^\circ) + \frac{1}{54} \cos(3000\pi t - 30^\circ)$$

- 6% (c) What are the gain and the phase shift of the frequency response of this filter at frequency 1.5 kHz?
- 6% (d) Find the output  $y(t)$  of this filter when the input signal is

$$x(t) = 5 + \sum_{n=1}^{\infty} \frac{1}{n} \sin(1000\pi nt)$$

7. Given  $H(j\omega) = \left( \frac{2}{2 + j\omega} \right)^3$

- 5% (a) What kind of filter has this frequency response (low pass, high pass, band pass, notch)?
- 10% (b) Design a filter with this frequency response.