
 name

1. Short answer questions; no explanations required.
- 5% (a) State the terminal law of a capacitor with capacitance 2 F.
- 5% (b) Is an inductor an open or short circuit at dc steady-state?
- 5% (c) When the input to an RLC circuit is $v_i(t) = \cos \omega t$ the output is

$$v_o(t) = \frac{2\omega}{\sqrt{1+4\omega^2}} \cos \left(\omega t + \tan^{-1} \left(-\frac{1}{2\omega} - 90^\circ \right) \right).$$

Is this circuit a lowpass filter, highpass filter, bandpass filter or none of the above?


- 5% (d) Give the formula for the current $i(t)$ whose phasor representation is $17 \angle -37^\circ$ with frequency 3 Hz.

2. Show how to interconnect several 1 F capacitors to obtain 2.5 F.


10%

3. Find the Thevenin equivalent phasor circuit for the following:

20%

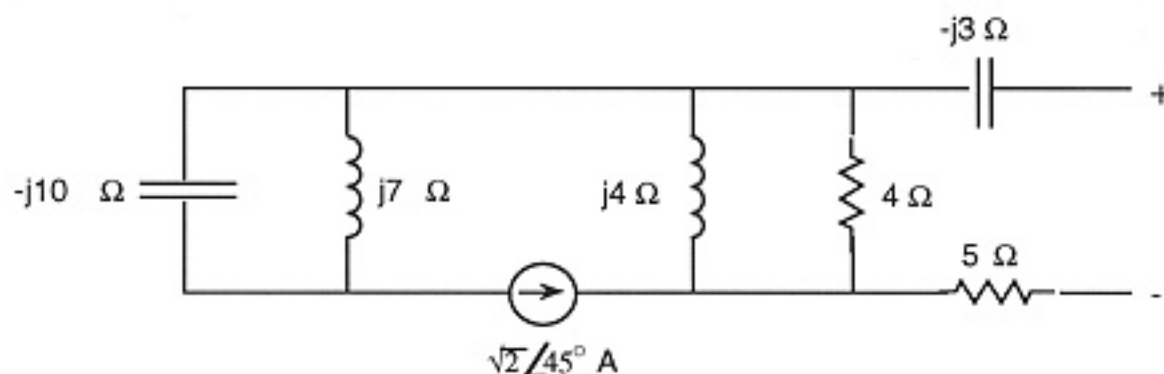

4.

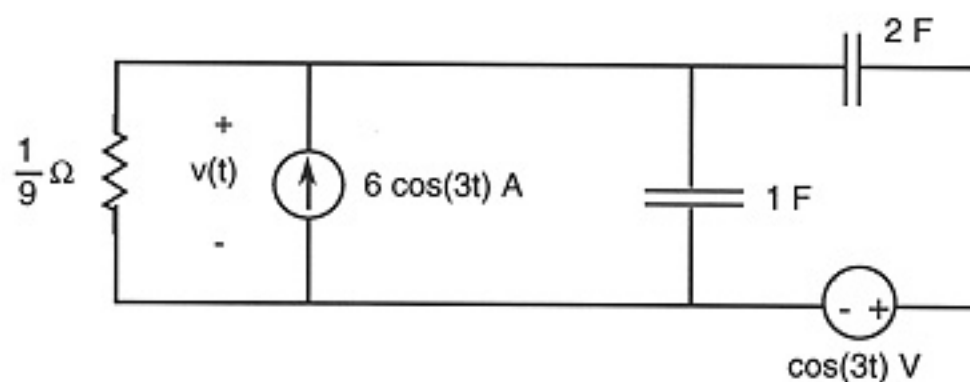


10% (a) Write a differential equation for $v(t)$ in the circuit shown above. Simplify your equation but do not solve.

15% (b) Find the steady-state voltage $v(t)$. You may use any method.

5. Find the steady-state voltage $v_o(t)$ in the circuit shown below.

25%

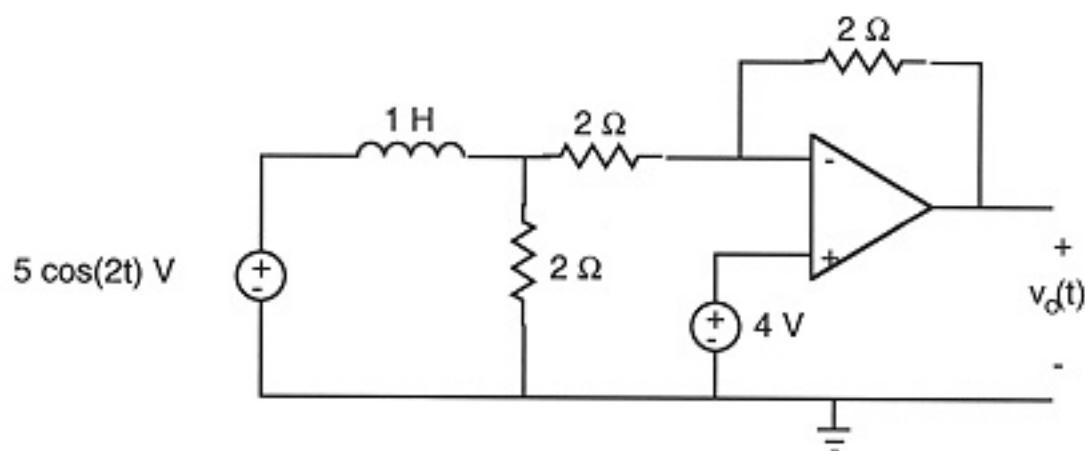

HAVE A HAPPY THANKSGIVING HOLIDAY!

 name

1. Short answer questions; no explanations required.

5% (a) State the terminal law of an inductor with inductance 3 H.

5% (b) Is a capacitor an open or short circuit at dc steady state?

5% (c) When the input to a certain RLC circuit is $v_i(t) = \cos \omega t$ the output is

$$v_o(t) = \sqrt{\frac{1}{1+9\omega^2}} \cos \left(\omega t + \tan^{-1} \left(-\frac{1}{3\omega} \right) \right).$$

Is this circuit a lowpass filter, highpass filter, bandpass filter or none of the above?


5% (d) Give the formula for the voltage $v(t)$ whose phasor representation is $13 \angle -24^\circ$ with frequency 5 Hz.

2. Show how to interconnect several 1 H inductors to obtain $3 \frac{1}{3}$ H.


10%

3 Find the Thevenin equivalent phasor circuit for the following.

20%

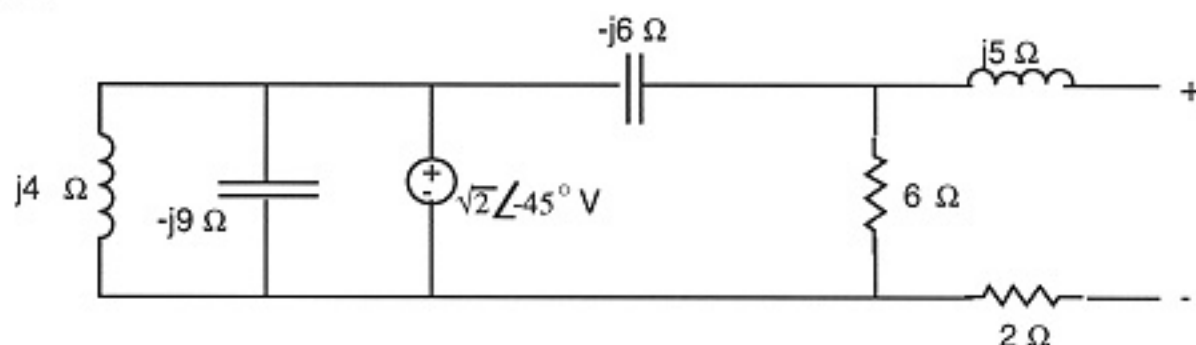

4.

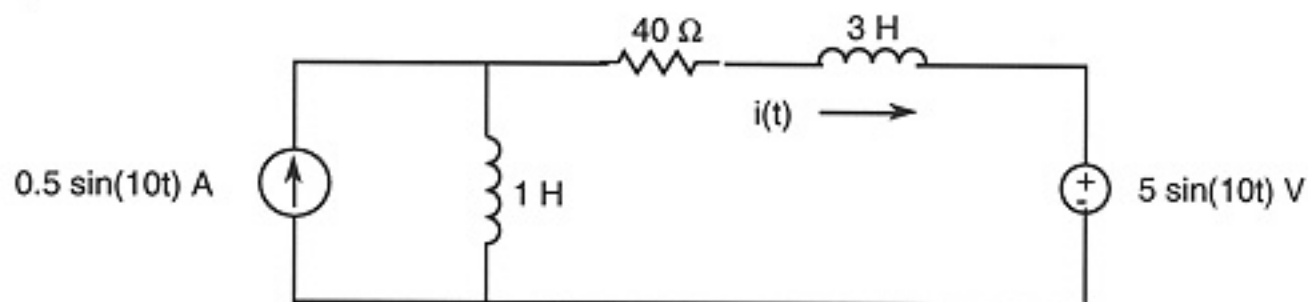


10% (a) Write a differential equation for $i(t)$ in the circuit shown above. Simplify your equation but do not solve.

15% (b) Find the steady-state current $i(t)$. You may use any method.

5. Find the steady-state voltage $v_o(t)$ in the circuit shown below.

25%

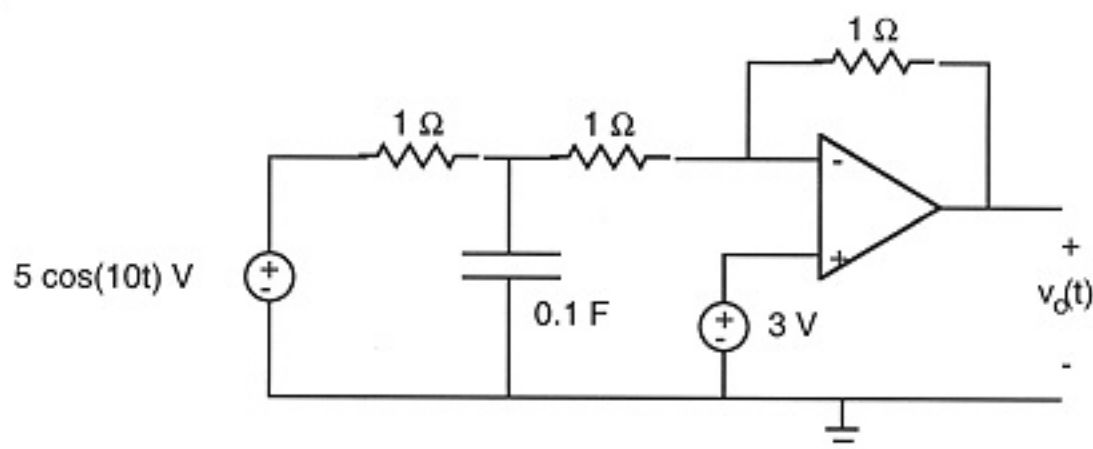

HAVE A HAPPY THANKSGIVING HOLIDAY!