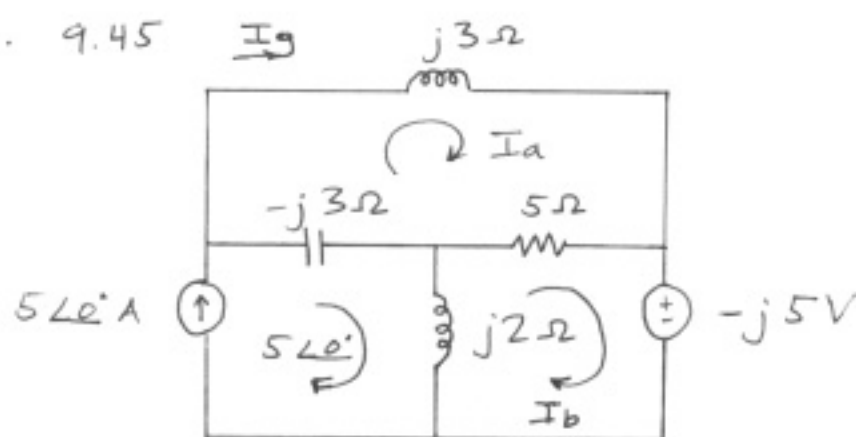


1. 9.45




$$\text{loop A: } j3I_a + 5(I_a - I_b) - j3(I_a - 5) = 0$$

$$\text{loop B: } j2(I_b - 5) + 5(I_b - I_a) - j5 = 0$$

$$\text{Solving: } I_a = -j3A \quad I_g = I_a = -j3 = 3\angle-90^\circ A$$

$$I_b = 0A$$

2. 9.48

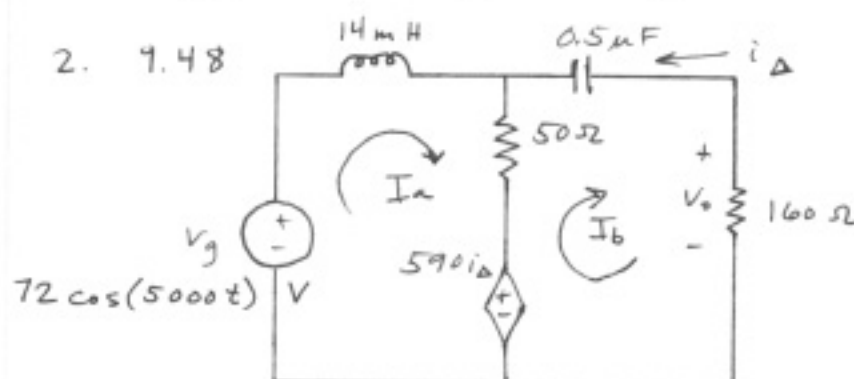

$$j\omega L = j5000(14 \cdot 10^{-3}) = j70\Omega$$

$$\frac{1}{j\omega C} = \frac{-j}{(5000)(0.5 \cdot 10^{-6})} = -j400\Omega$$

$$\text{loop A: } 72\angle 0^\circ = j70I_a + 50(I_a - I_b) + 590(-I_b)$$

$$\text{loop B: } 50(I_b - I_a) - j400(I_b) + 160(I_b) - 590(-I_b) = 0$$


$$\text{Solving } I_b = (50 - j50) \text{ mA} \quad I_a = 0.4 - j1.2 A$$

$$V_0 = 160 I_b = 8 - j8 V = 11.31 \angle -45^\circ V$$

$$V_o = 11.31 \cos(5000t - 45^\circ) \text{ V}$$

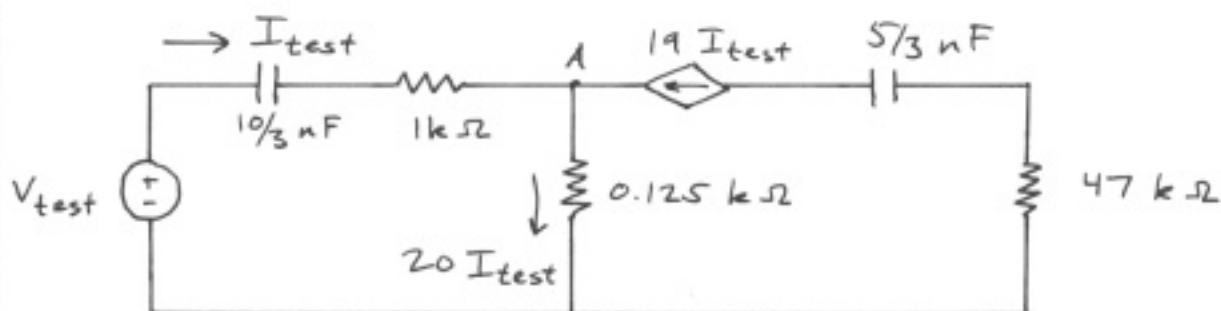3. 9.36

$$\frac{1}{j\omega C_1} = \frac{-j}{(25 \cdot 10^3)(10/3 \cdot 10^{-9})} = -j12 \text{ k}\Omega$$



Apply a test voltage


By KCL at node A, $I_{\text{test}} + 19 I_{\text{test}}$ entering node $\Rightarrow 20 I_{\text{test}}$ must be leaving through $0.125 \text{ k}\Omega$ resistor.

KVL around left loop:

$$V_{\text{test}} = (1 - j12) \text{ k}\Omega I_{\text{test}} + 20 I_{\text{test}} (0.125 \text{ k}\Omega)$$

$$Z_{\text{th}} = \frac{V_{\text{test}}}{I_{\text{test}}} = 3.5 - j12 \text{ k}\Omega$$

4 9.39

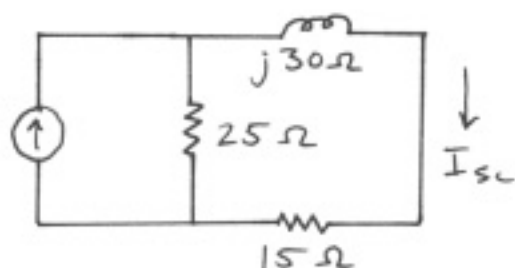

Apply current divider to determine I_{sc}

$$I_{\text{sc}} = \frac{(16 \angle 0^\circ)(25 \Omega)}{25 + 15 + j30} = 6.4 - j4.8 \text{ A}$$

$$Z_{\text{th}} = \frac{(-j50)(40 + j30)}{40 + j30 - j50} = 50 - j25 \Omega$$

5. 9.71

$$a) \frac{1}{j\omega C} = -\frac{j}{(2 \cdot 10^5)(12.5 \cdot 10^{-9})} = -j400 \Omega$$

$$\text{KCL at } V_n: \frac{V_n}{200} + \frac{V_n - V_o}{-j400} = 0$$

$$\frac{V_o}{-j400} = \frac{V_n}{200} + \frac{V_n}{-j400}$$

$$V_o = V_n - j2 V_n = (1 - j2) V_n$$

$$\text{Voltage divider } V_p = \frac{V_g (1/j\omega C_o)}{500 + (1/j\omega C_o)} = \frac{V_g}{1 + j(500)(2 \cdot 10^5) C_o}$$

$$V_g = 10 \angle 0^\circ \text{ V}$$

$$V_p = \frac{10 \angle 0^\circ}{1 + j10^8 C_o} = V_n \text{ by Golden Rules}$$

$$\Rightarrow V_o = \frac{(1 - j2) 10 \angle 0^\circ}{1 + j10^8 C_o}$$

$$|V_o| = \frac{\sqrt{5} (10)}{\sqrt{1 + 10^{16} C_o^2}} = 10 \text{ V} = \text{power supply voltage}$$

$$\text{Solving: } C_o = 20 \text{ nF}$$

$$b) V_o = \frac{10(1 - j2)}{1 + j2} = 10 \angle -126.87^\circ$$

$$v_o = 10 \cos(2 \cdot 10^5 t - 126.87^\circ) \text{ V}$$

6. 10.7

$$\frac{1}{j\omega C} = \frac{-j}{(5000)(80 \cdot 10^{-9})} = -j 2500 \Omega$$

$$Z_f = 7.5 \text{ k}\Omega \parallel 80 \text{ nF} = \frac{-j 2500 (7500)}{7500 - j 2500}$$

$$= 750 - j 2250 \Omega$$

$$Z_i = 1500 \Omega$$

KCL at inverting input, V_n

$$\frac{V_n - V_g}{Z_i} + \frac{V_n - V_o}{Z_f} = 0$$

$$V_n (Z_f - Z_i) - Z_i V_o = Z_f V_g$$

$$V_n = V_p = 0 \text{ by Golden Rules}$$

$$\Rightarrow V_o = - \frac{Z_f}{Z_i} V_g = - \frac{750 - j 2250}{1500} (4V)$$

$$= -(0.5 - j 1.5)(4V) = -2 + j 6 \text{ V}$$


$$= 6.32 \angle 108.43^\circ \text{ V}$$

$$P = \frac{1}{2} \frac{V_o^2}{R} = \frac{1}{2} \frac{40}{1000} = 20 \cdot 10^{-3} \text{ W} = 20 \text{ mW}$$

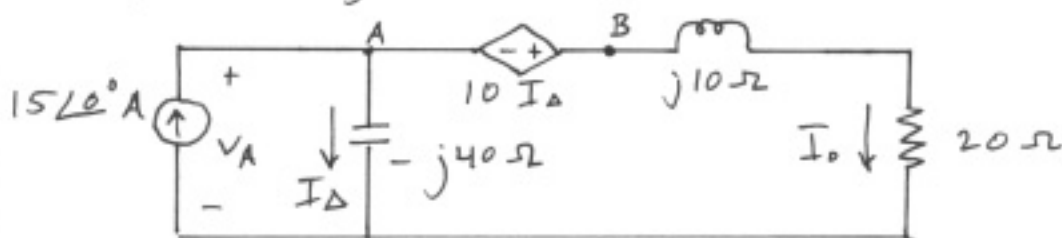7. 10.9

$$j\omega L = j 10,000 (10^{-3}) = j 10 \Omega$$

$$\frac{1}{j\omega C} = \frac{1}{j 10,000 (2.5 \cdot 10^{-6})} = -j 40 \Omega$$



Consider the dependent voltage source to be a supernode.

KCL at supernode:

$$-15 + \frac{V_A}{-j40} + \frac{V_B}{20 + j10} = 0$$

$$V_B - V_A = 10 I_\Delta = 10 \left(\frac{V_A}{-j40} \right)$$

$$V_A = 300 - j100 \text{ V}$$

$$V_B = 325 - j250 \text{ V}$$

$$I_\Delta = \frac{V_A}{-j40} = 2.5 + j7.5 \text{ A}$$

$$I_o = 15 \angle 0^\circ - I_\Delta = 15 - 2.5 - j7.5$$

$$= 12.5 - j7.5 = 14.58 \angle -30.9^\circ \text{ A}$$


$$P_{20\Omega} = \frac{1}{2} |I_o|^2 (20) = 2125 \text{ W}$$

8 10.34

$$j\omega L = j10,000(6) = j60 \text{ k}\Omega$$

$$\frac{1}{j\omega C} = \frac{-j}{10000 \cdot 2.5 \cdot 10^{-9}} = -j40 \text{ k}\Omega$$

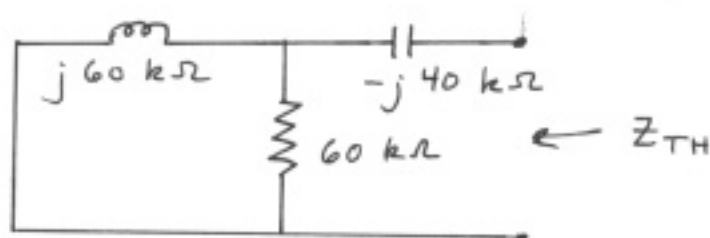a) Find Thevenin impedance equivalent of circuit. Turn off indep. voltage source.



$$Z_{TH} = \frac{1}{j\omega C} + \frac{60(j60)}{60+j60} = -j40 + 30 + j30 \text{ k}\Omega$$

$$= 30 - j10 \text{ k}\Omega$$

Max power when Z_L is conjugate of Z_{TH}

$$\Rightarrow Z_L = 30 + j10 \text{ k}\Omega$$

Find Thevenin voltage by finding V_{oc}

V_{oc} is a voltage divider between L and R

$$V_{TH} = V_{oc} = \frac{90 \angle 0^\circ (60)}{60 + j60} = 45(1-j)$$

$$= 45\sqrt{2} \angle -45^\circ \text{ V}$$

$$I = \frac{45\sqrt{2} \angle -45^\circ}{60 \cdot 10^3} = 0.75\sqrt{2} \angle -45^\circ \text{ mA}$$

$$|I_{rms}| = 0.75 \text{ mA}$$

$$P_L = (0.75 \cdot 10^{-3})^2 \cdot (30 \cdot 10^3) = 16.875 \text{ mW}$$

Equivalent circuit:

