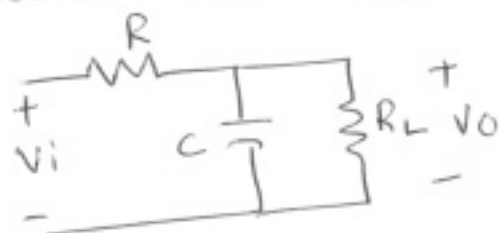


HOMEWORK #11 SOLUTIONS

[2] The lowpass series RC filter with a load resistor R_L can be represented as shown in the following diagram.




(a) Transfer function of the filter

The parallel combination of resistor R_L and capacitor can be represented by an impedance Z , where

$$Z = \frac{\frac{1}{sC} \cdot R_L}{\frac{1}{sC} + R_L}, \text{ where } s = j\omega$$

The equivalent ckt would be

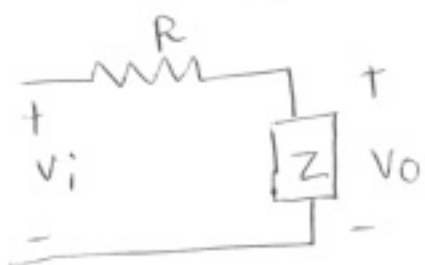

$$\text{and } H(s) = \frac{Z}{Z + R} = \frac{V_o}{V_i}$$

$$H(s) = \frac{\frac{\frac{1}{sC} \cdot R_L}{\frac{1}{sC} + R_L}}{R + \frac{\frac{1}{sC} \cdot R_L}{\frac{1}{sC} + R_L}}$$

$$= \frac{R_L}{R + s R R_L C + R_L}$$

$$= \frac{R_L / R R_L C}{s + \frac{R + R_L}{R R_L C}}$$

$$= \frac{1/RC}{s + \frac{1}{kRC}}, \text{ where } k = \frac{R_L}{R + R_L}$$

$$\text{Thus } H(s) = \frac{1/RC}{s + \frac{1}{kRC}}, \text{ where } k = \frac{R}{R + R_L}$$

Replacing s by $j\omega$ (since $s = j\omega$),

$$H(j\omega) = \frac{1/RC}{j\omega + \frac{1}{kRC}}, \quad k = \frac{R}{R + R_L}$$

(b) $\max |H(j\omega)|$

$$|H(j\omega)| = \frac{1/RC}{\sqrt{\omega^2 + \left(\frac{1}{kRC}\right)^2}}$$

$|H(j\omega)|$ will be maximum for $\omega = 0$

$$\therefore |H(j\omega)|_{\max} = \frac{1/R_C}{\sqrt{0 + (\frac{1}{kR_C})^2}}$$

$$\therefore |H(j\omega)|_{\max} = K = \frac{R_L}{R + R_L}$$

(c) cutoff frequency ω_c

at the cutoff frequency ω_c ,

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} (|H(j\omega)|_{\max})$$

$$\therefore |H(j\omega_c)| = \frac{1}{\sqrt{2}} (K) = \frac{1/R_C}{\sqrt{(\omega_c)^2 + (\frac{1}{kR_C})^2}}$$

Squaring both sides,

$$\frac{K^2}{2} = \frac{(1/R_C)^2}{\omega_c^2 + (\frac{1}{kR_C})^2}$$

$$\therefore K^2 \omega_c^2 + K^2 (\frac{1}{kR_C})^2 = 2 (\frac{1}{R_C})^2$$

$$K^2 \omega_c^2 = (\frac{1}{R_C})^2$$

$$\therefore \boxed{\omega_c = \frac{1}{k} (\frac{1}{R_C})} \text{ is the cutoff frequency}$$

(d)

As we see in parts (a), (b) & (c), loading does affect the low pass filter. It changes the transfer function of the filter, which in turn leads to:

(i) Passband magnitude of the transfer function, which is also its maximum magnitude, is

$$|H(j\omega)|_{\max} = k = \frac{R_L}{R + R_L}, \text{ for the}$$

filter with loading. Without R_L , the value of $|H(j\omega)|_{\max}$ would have been 1.


Thus loading decreases the pass band magnitude

(ii) As seen in part (c), loading increases the cutoff frequency since $\omega_c = \frac{1}{k} \left(\frac{1}{RC} \right)$.

$$k = \frac{R_L}{R + R_L} \therefore k < 1$$

$\therefore \omega_c > \frac{1}{RC}$ The cutoff freq
with no load, is $\frac{1}{RC}$.

3 14.5

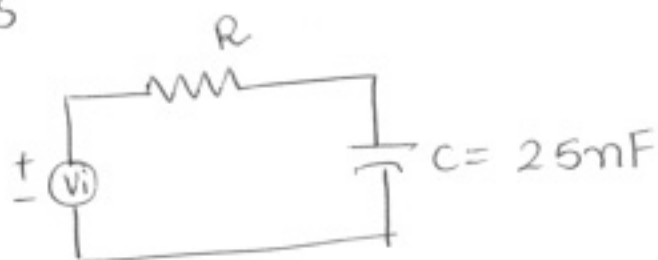

Desired $\omega_c = 160 \text{ k rad/s}$

$$(a) \quad f_c = \frac{\omega_c}{2\pi} = \frac{160 \text{ k}}{2\pi} = 25.46 \text{ kHz}$$

$$f_c = 25.46 \text{ kHz}$$

$$(b) \quad \text{Now } f_c = \frac{1}{2\pi RC}$$

$$\therefore R = \frac{1}{2\pi f_c C}$$

$$= \frac{1}{2\pi \left(\frac{160 \text{ k}}{2\pi} \right) \times 25 \times 10^{-9}}$$

$$\therefore R = 250 \Omega$$

(c) Now from Prob 2 - part (c),
for a series RC low pass filter
with load resistor R_L , as
shown in ckt diagram given
below, the cutoff freq is
given by,

$$\omega_c = \frac{1}{K} \left(\frac{1}{RC} \right)$$

$$\text{where } K = \frac{R_L}{R + R_L}$$



Now given $\omega_c = 160 \text{ krad/s}$

Let $\omega_{c\text{-new}} = 8\% \text{ more than } \omega_c$

$$= 1.08 \times 160$$

$$= 172.8 \text{ krad/s}$$

$$\therefore 172.8 \text{ krad/s} = \frac{1}{K} \left(\frac{1}{RC} \right)$$

$$= \frac{1}{K} \left(\frac{1}{250 \times 25 \times 10^{-9}} \right)$$

$$\therefore K = 0.9259$$

$$\left[\begin{array}{l} \text{OR } \omega_{c\text{-new}} = \frac{1}{K} \omega_c \\ \therefore K = \frac{\omega_c}{\omega_{c\text{-new}}} = \frac{1}{1.08} = 0.9259 \end{array} \right]$$

$$\text{Since } K = \frac{R_L}{R + R_L}$$

$$\therefore 0.9259 = \frac{R_L}{250 + R_L}$$

$$\therefore (0.9259)(250) = R_L(1 - 0.9259)$$

$$\therefore R_L = 3125 \Omega$$

is the smallest load resistor that could be connected across the o/p terminals of the filter

(d) Using expression derived in part (b) of problem 2,


$$|H(\omega)|_{\omega=0} = |H(\omega)|_{\text{max}}$$

$$= \frac{R_L}{R + R_L}$$

$$= K$$

$$\therefore |H(\omega)|_{\omega=0} = 0.9259$$


4

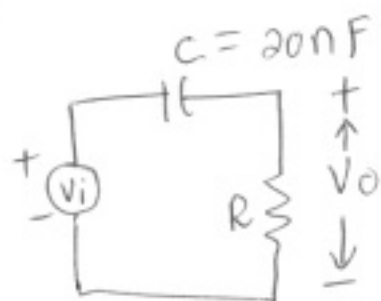14.10Desired $f_c = 800 \text{ Hz}$

$$(a) \quad f_c = \frac{1}{2\pi RC}$$

$$\therefore 800 = \frac{1}{2\pi R (20 \times 10^{-9})}$$

$$\therefore R = 9.95 \text{ k}$$

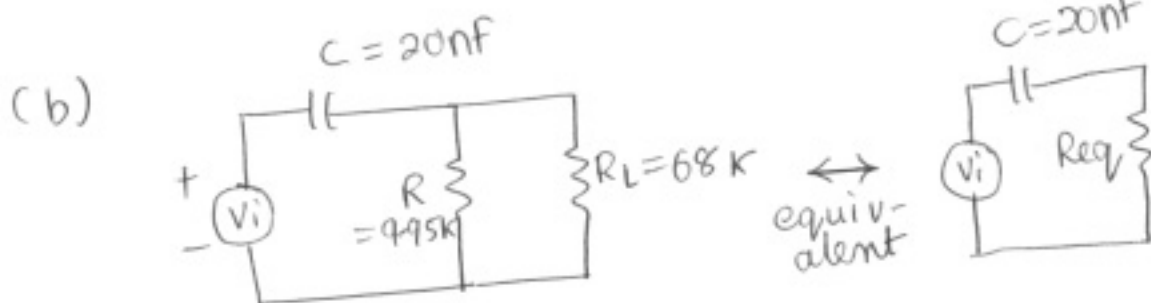

$$\begin{aligned} \text{Now } R_{eq} &= R \parallel R_L = \frac{R \cdot R_L}{R + R_L} \\ &= \frac{(9.95 \text{ k})(68 \text{ k})}{9.95 \text{ k} + 68 \text{ k}} \end{aligned}$$


$$\therefore R_{eq} = 8.68 \text{ k}$$

$$f_c = \frac{1}{2\pi R_{eq} C} = \frac{1}{2\pi (8.68 \text{ k})(20 \times 10^{-9})}$$

$$\therefore f_c = 917.26 \text{ Hz}$$

5

14.12

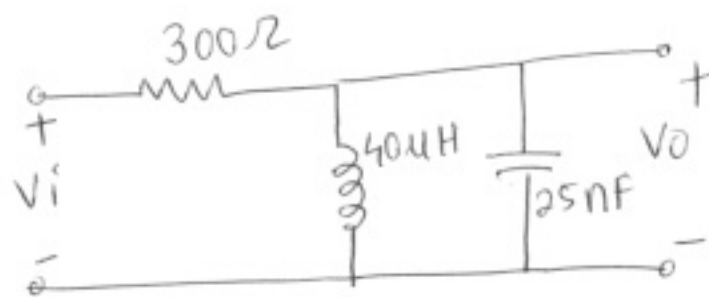

Note:- For derivations of formulae used here, refer to Example 14.6, of the Text Book.

$$(a) \quad \omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{40 \times 10^{-6} \times 25 \times 10^{-9}}}$$

$$\omega_0 = 10^6 \text{ rad/s} = 1 \text{ Mrad/s}$$

$$(b) \quad f_0 = \frac{\omega_0}{2\pi} = \frac{10^6}{2\pi} = 159.15 \text{ kHz}$$

$$f_0 = 159.15 \text{ kHz}$$

$$(c) \quad \beta = \frac{1}{RC} = \frac{1}{(300)(25 \times 10^{-9})} = 133.33 \text{ krad/s}$$

$$\text{and } Q = \omega_0 / \beta$$

$$\therefore Q = \frac{10^6}{133.33 \text{ k}}$$

$$Q = 7.5$$

$$(d) \quad \omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

substituting $\beta = 133.33 \text{ krad/s}$
and $\omega_0 = 1 \text{ Mrad/s}$, we get

$$\boxed{\omega_{c1} = 935.55 \text{ krad/s}}$$

$$(e) \quad f_{c1} = \frac{\omega_{c1}}{2\pi} = \frac{935.55 \text{ k}}{2\pi}$$

$$\therefore \boxed{f_{c1} = 148.90 \text{ kHz}}$$

$$(f) \quad \omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$\therefore \boxed{\omega_{c2} = 1068.89 \text{ krad/s}}$$


$$(g) \quad \therefore f_{c2} = \frac{\omega_{c2}}{2\pi}$$

$$\therefore \boxed{f_{c2} = 170.12 \text{ kHz}}$$

$$(h) \quad \beta = \frac{\omega_0}{Q} = \frac{1}{RC}$$

$$\therefore \boxed{\beta = 133.33 \text{ krad/s or } 21.22 \text{ kHz}}$$

Problem 6. (14.17)

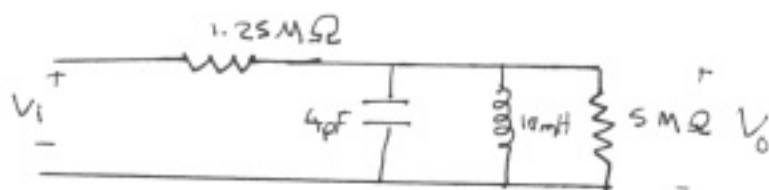

$$\text{Let } Z_p = Z_C // Z_L // R_L \quad \left. \begin{aligned} Z_C // Z_L &= \frac{Z_C Z_L}{Z_C + Z_L} \\ Z_C // Z_L &= \frac{Z_C Z_L}{Z_C + Z_L} \end{aligned} \right\} \Rightarrow Z_p = \frac{\frac{Z_C Z_L R_L}{Z_C + Z_L}}{\frac{Z_C Z_L}{Z_C + Z_L} + R_L} = \frac{Z_C Z_L R_L}{Z_C Z_L + R_L(Z_C + Z_L)}$$

$$Z_L = sL$$

$$Z_C = \frac{1}{sC}$$

$$\Rightarrow Z_p = \frac{\frac{L R_L}{C}}{\frac{L}{C} + R_L \left(\frac{1}{sC} + sL \right)}$$

$$= \frac{R_L L}{L + C R_L \left(\frac{1}{sC} + sL \right)} = \frac{R_L L}{L + \frac{R_L}{s} + s C L R_L}$$

$$= \frac{R_L L s}{s^2 (R_L L C) + s L + R_L}$$

$$H(s) = \frac{V_o}{V_i} = \frac{Z_p}{Z_p + R} = \frac{\frac{R_L L s}{s^2 (R_L L C) + s L + R_L}}{R + \frac{R_L L s}{s^2 (R_L L C) + s L + R_L}}$$

$$= \frac{R_L L s}{s^2 R_L L C + L(R + R_L)s + R R_L} = \frac{s/R_C}{s^2 + s \frac{(R + R_L)}{C(R_L)} + \frac{1}{LC}}$$

general expression:

$$H(s) = \frac{K \beta s}{s^2 + \beta s + \omega_0^2}$$

(a)

$$\Rightarrow \omega_0^2 = \frac{1}{LC} = \frac{1}{4 \times 10^{-12} \times 10 \times 10^{-3}} = 25 \times 10^{12} \Rightarrow \underline{\underline{\omega_0 = 5 \text{ M rad/sec}}}$$

(b)

$$\beta = \frac{R + R_L}{C R R_L} = \frac{1.25 \times 10^6 + 5 \times 10^6}{4 \times 10^{-12} \times 1.25 \times 10^6 \times 5 \times 10^6} = \underline{\underline{250 \text{ K rad/sec}}}$$

$$(c) \quad Q = \frac{\omega_0}{\delta} = \frac{5}{0.25} = \underline{\underline{20}}$$

$$(d) \quad \text{At resonance } \omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

Combination of L and C has impedance $Z_p = \frac{1}{j\omega C} // j\omega L$

$$\Rightarrow Z_p = \frac{\frac{1}{j\omega C} \cdot j\omega L}{\frac{1}{j\omega C} + j\omega L} = \frac{L/C}{\frac{1}{j\omega C} + j\omega L}$$

$$\text{at } \omega = \omega_0 = \frac{1}{\sqrt{LC}}, \quad Z_p = \frac{L/C}{-j\sqrt{L/C} + j\sqrt{L/C}} = \frac{L/C}{0} = \infty$$

$\Rightarrow$ Can replace combination of L and C with open circuit

$$\Rightarrow H(j\omega) \Big|_{\omega=\omega_0} = \frac{V_o}{V_i} = \frac{R_L}{R + R_L} =$$

$$= \frac{5}{6.25} = 0.8 \angle 0^\circ \Rightarrow \text{Gain is } 0.8 \angle 0^\circ$$


$$\Rightarrow V_o = 0.8 V_i = 0.8 \times 750 \cos(\omega_0 t) = \underline{\underline{600 \cos(5 \times 10^6 t) \text{ mV}}}$$

(e)


$$\left. \begin{aligned} b &= \frac{R + R_L}{C R R_L} \\ \omega_0 &= \sqrt{\frac{1}{LC}} \\ Q &= \frac{\omega_0}{\delta} \end{aligned} \right\} \Rightarrow Q = \frac{\omega_0}{\frac{R + R_L}{C R R_L}} = \frac{\omega_0 C R R_L}{R + R_L} = \frac{\omega_0 R C}{1 + R/R_L}$$

$$= \frac{5 \times 10^6 \times 5 \times 10^{-6}}{1 + \frac{1.25}{R_L}} = \frac{25}{1 + \frac{1.25}{R_L}} \quad QED$$


Problem 6, Solution, Magnitude plot

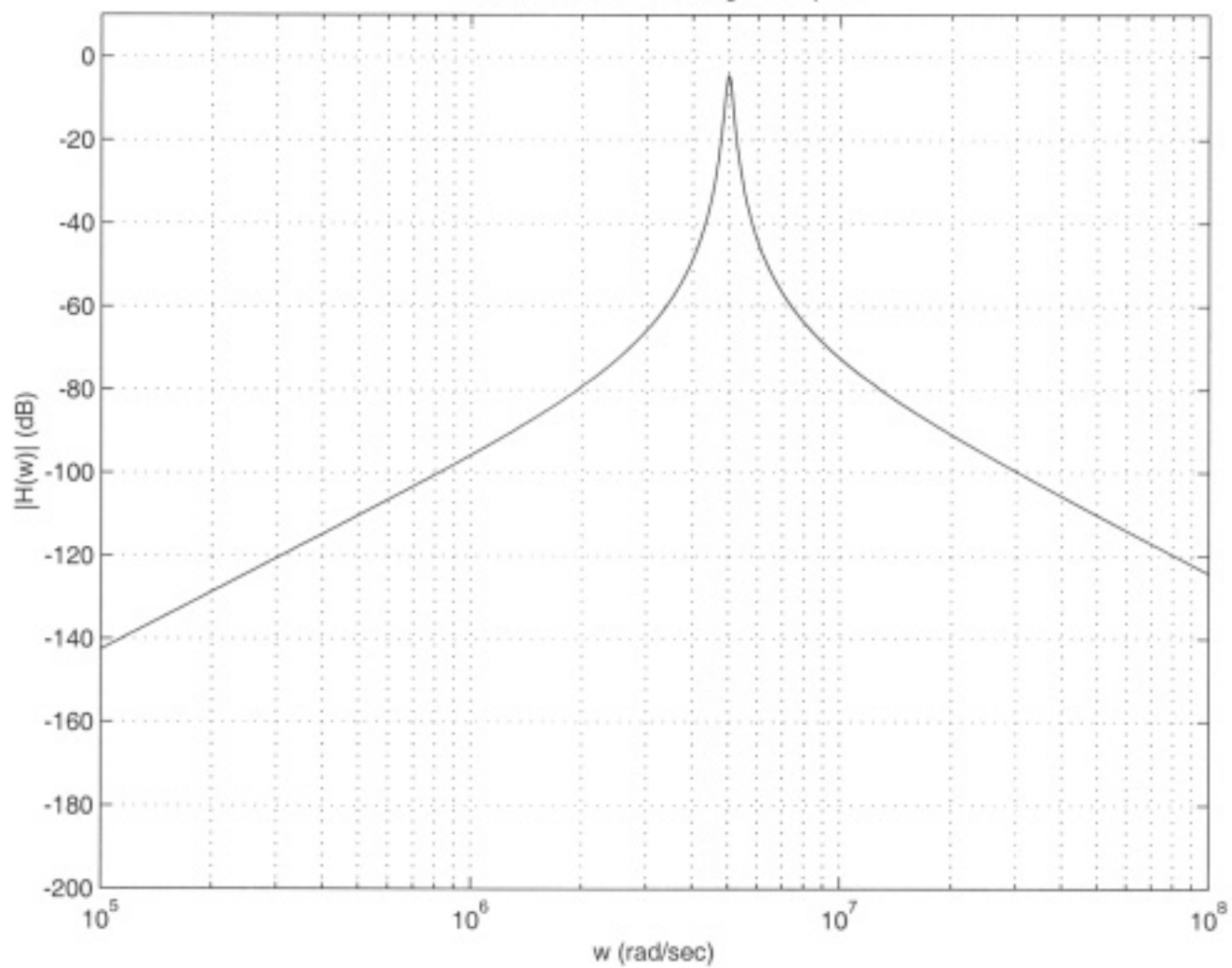

Problem 6, Solution, Phase plot

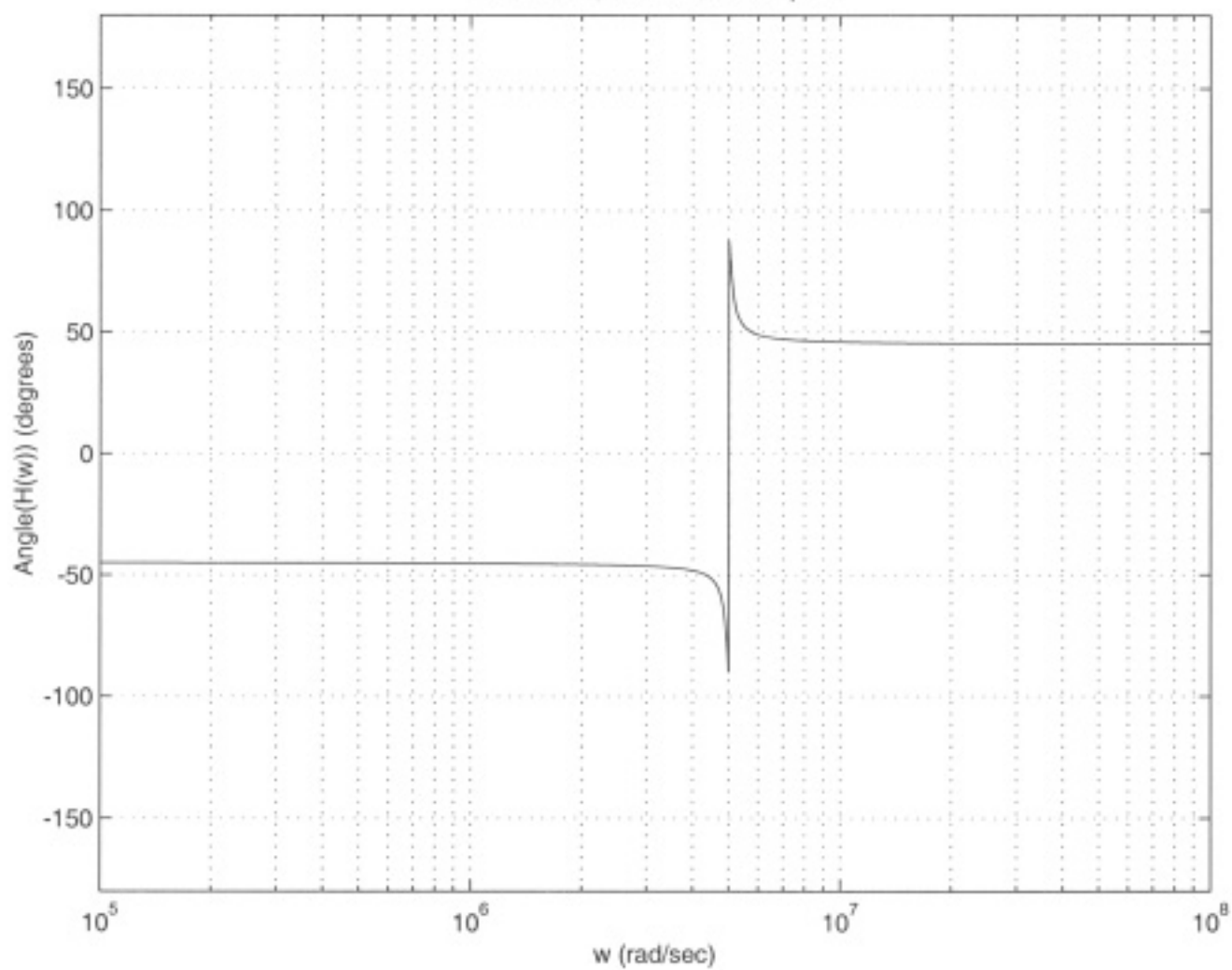


Problem 6, Solution, R vs Q

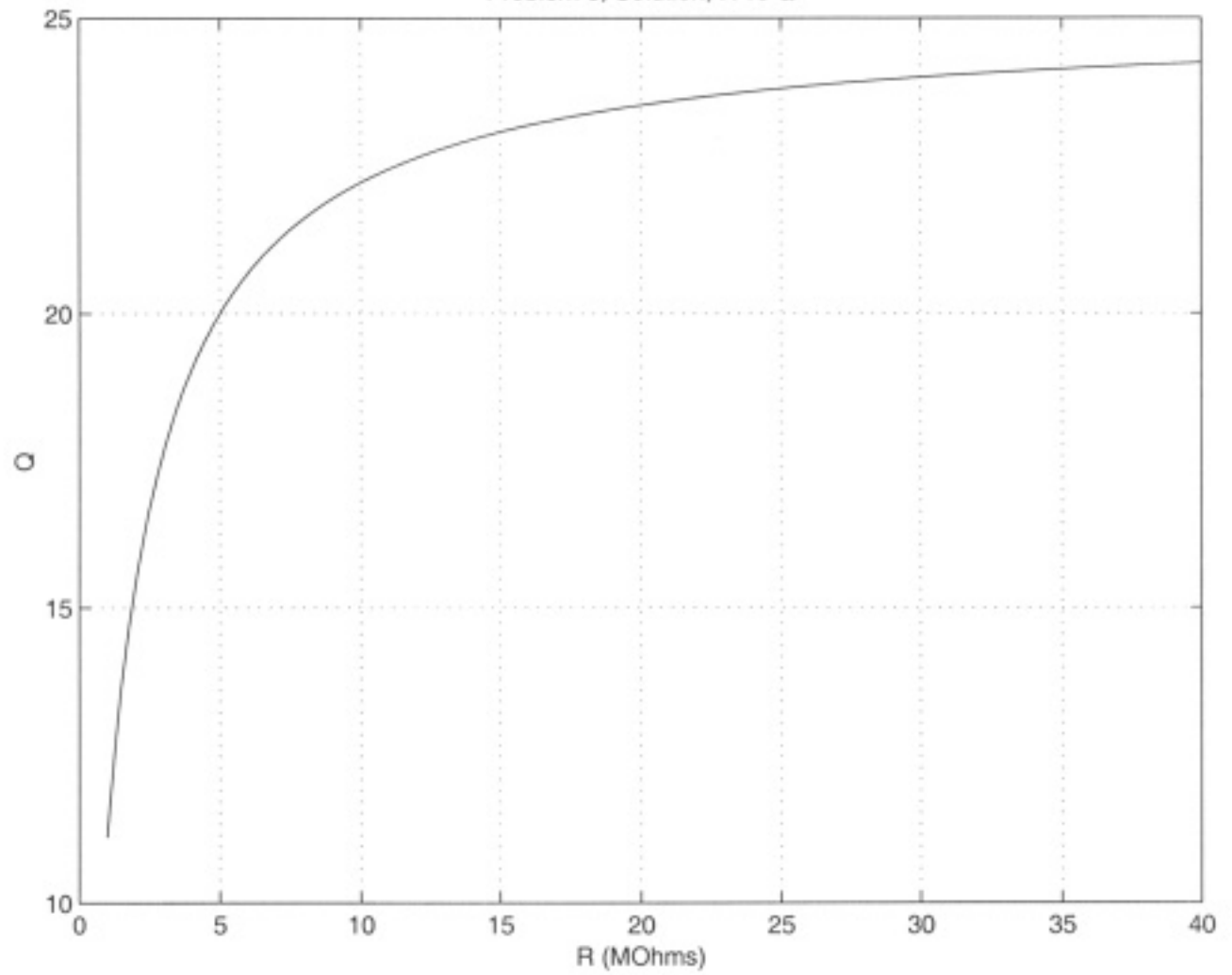

Problem 7. (14.19)

Note:

$$B = \Delta\omega$$

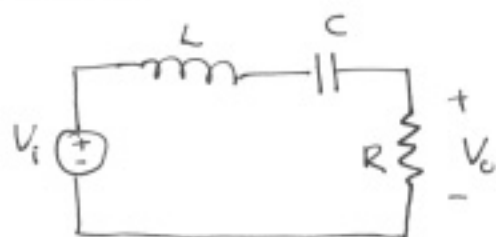

$$C = 20 \text{ nF}, f_o = 20 \text{ kHz} \Rightarrow \omega_o = 2\pi \times 20 \text{ kHz} \\ Q = 5$$

(a) Following the analysis pg. 719-722,

$$\omega_o = \frac{1}{\sqrt{LC}} \quad (\text{eq. 14.31}) \Rightarrow L = \frac{1}{\omega_o^2 C} = \frac{1}{(2\pi \times 20 \times 10^3)^2 \times 20 \times 10^{-9}}$$

$$\Rightarrow L = 0.00317 \text{ H} = \underline{\underline{3.17 \text{ mH}}}$$

Recall that

$$B = \frac{R}{L} \text{ and } Q = \frac{\omega_o}{B}. \text{ Therefore } R = \frac{\omega_o L}{Q}$$

$$\Rightarrow R = \frac{20 \times 10^3 \times 3.17 \times 10^{-3}}{5} \times 2\pi = \underline{\underline{79.7 \Omega}}$$

$$(b) \omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \quad (\text{eq. 14.29})$$

$$= -\frac{79.7}{2 \times 3.17 \times 10^{-3}} + \sqrt{\left(\frac{79.7}{2 \times 3.17 \times 10^{-3}}\right)^2 + \left(\frac{1}{3.17 \times 10^{-3} \times 20 \times 10^{-9}}\right)}$$


$$= 113.65 \text{ Krad/sec}$$

$$f_{c1} = \frac{\omega_{c1}}{2\pi} = \underline{\underline{18.09 \text{ kHz}}}$$

$$(c) \omega_o = \sqrt{\omega_{c1} \omega_{c2}} \Rightarrow \omega_{c2} = \frac{\omega_o^2}{\omega_{c1}} = \frac{(2\pi \times 20 \times 10^3)^2}{2\pi \times 18.09 \times 10^3} = 138.95 \text{ Krad/sec} \\ \Rightarrow \underline{\underline{f_{c2} = 22.11 \text{ kHz}}}$$

$$(d) \text{ bandwidth (Hz)} = \frac{B}{2\pi} = \frac{\omega_o}{2\pi Q} = \frac{20 \times 10^3}{5} = \underline{\underline{4 \text{ kHz}}}$$

Problem 8 (14.27)

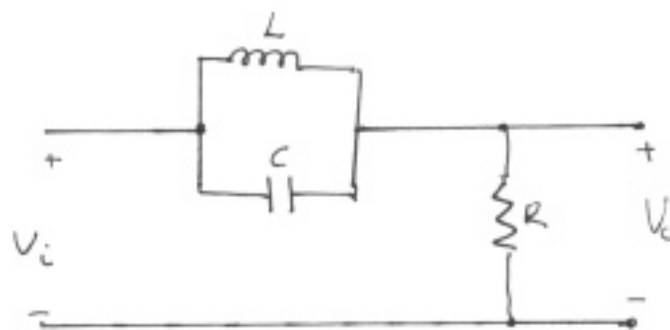

$$L = 625 \mu\text{H}$$

$$C = 25 \text{ pF}$$

$$R = 80 \text{ k}\Omega$$

$$Z_R = R$$

$$Z_C = \frac{1}{sC}$$

$$Z_L = sL$$

$$\text{Let } Z_p = Z_L // Z_C$$

$$\Rightarrow Z_p = \frac{Z_C Z_L}{Z_L + Z_C} = \frac{sL / sC}{sL + 1/sC}$$

$$\Rightarrow Z_p = \frac{sL}{1 + s^2 LC}$$

$$H(s) = \frac{V_o}{V_i} = \frac{R}{R + Z_p} \quad (\text{Voltage divider})$$

$$= \frac{R}{R + \frac{sL}{1 + s^2 LC}} = \frac{R(1 + s^2 LC)}{sL + R(1 + s^2 LC)}$$

$$= \frac{LCR s^2 + R}{RLC s^2 + sL + R} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{1}{CR} s + \frac{1}{LC}}$$

(a) General expression of $H(s)$ is $H(s) = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$ (eq. 14.55)

$$\Rightarrow \omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{625 \times 10^{-6} \times 25 \times 10^{-12}}} = \underline{\underline{8 \text{ Mrad/sec}}}$$

(b) $f_0 = \frac{\omega_0}{2\pi} = \frac{8 \times 10^6}{2\pi} = \underline{\underline{1.27 \text{ MHz}}}$

(c) $\beta = \frac{1}{RC} = \frac{1}{80 \times 10^3 \times 25 \times 10^{-12}} = 500 \text{ krad/sec} \Rightarrow \text{Bandwidth(Hz)} = 79.58 \text{ KHz}$

$$Q = \frac{\omega_0}{\beta} = \frac{8 \times 10^6}{500 \times 10^3} = \underline{\underline{16}}$$

$$(d) \quad \omega_{c1} = \omega_0 \left[-\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right] \quad (\text{eq. 14.53})$$

$$\Rightarrow \omega_{c1} = 8 \times 10^6 \left[-\frac{1}{32} + \sqrt{1 + \left(\frac{1}{32}\right)^2} \right]$$

$$\Rightarrow \underline{\underline{\omega_{c1} = 7.75 \text{ Mrad/sec}}}$$

$$(e) \quad f_{c1} = \frac{\omega_{c1}}{2\pi} = \underline{\underline{1.23 \text{ MHz}}}$$

$$(f) \quad \omega_{c2} = \omega_0 \left[\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right] \quad (\text{eq. 14.54})$$

$$\Rightarrow \omega_{c2} = 8 \times 10^6 \left[\frac{1}{32} + \sqrt{1 + \frac{1}{32^2}} \right]$$

$$\Rightarrow \underline{\underline{\omega_{c2} = 8.25 \text{ Mrad/sec}}}$$

$$(g) \quad f_{c2} = \frac{\omega_{c2}}{2\pi} = \frac{8.25 \times 10^6}{2\pi} = \underline{\underline{1.31 \text{ MHz}}}$$

$$(h) \quad b = 2\pi(f_{c2} - f_{c1}) = 1.31 - 1.23 \approx \underline{\underline{80 \text{ kHz}}}$$


(agrees with b calculated in part (c))

For Matlab plots:

$$\frac{1}{LC} = 64 \times 10^{12} \left(\frac{\text{rad}}{\text{sec}}\right)^2, \quad \frac{1}{RC} = 5 \times 10^5 \frac{\text{rad}}{\text{sec}}$$

$$\Rightarrow H(s) = \frac{s^2 + 64 \times 10^{12}}{s^2 + 5 \times 10^5 s + 64 \times 10^{12}}$$

Problem 8, Solution, Magnitude plot

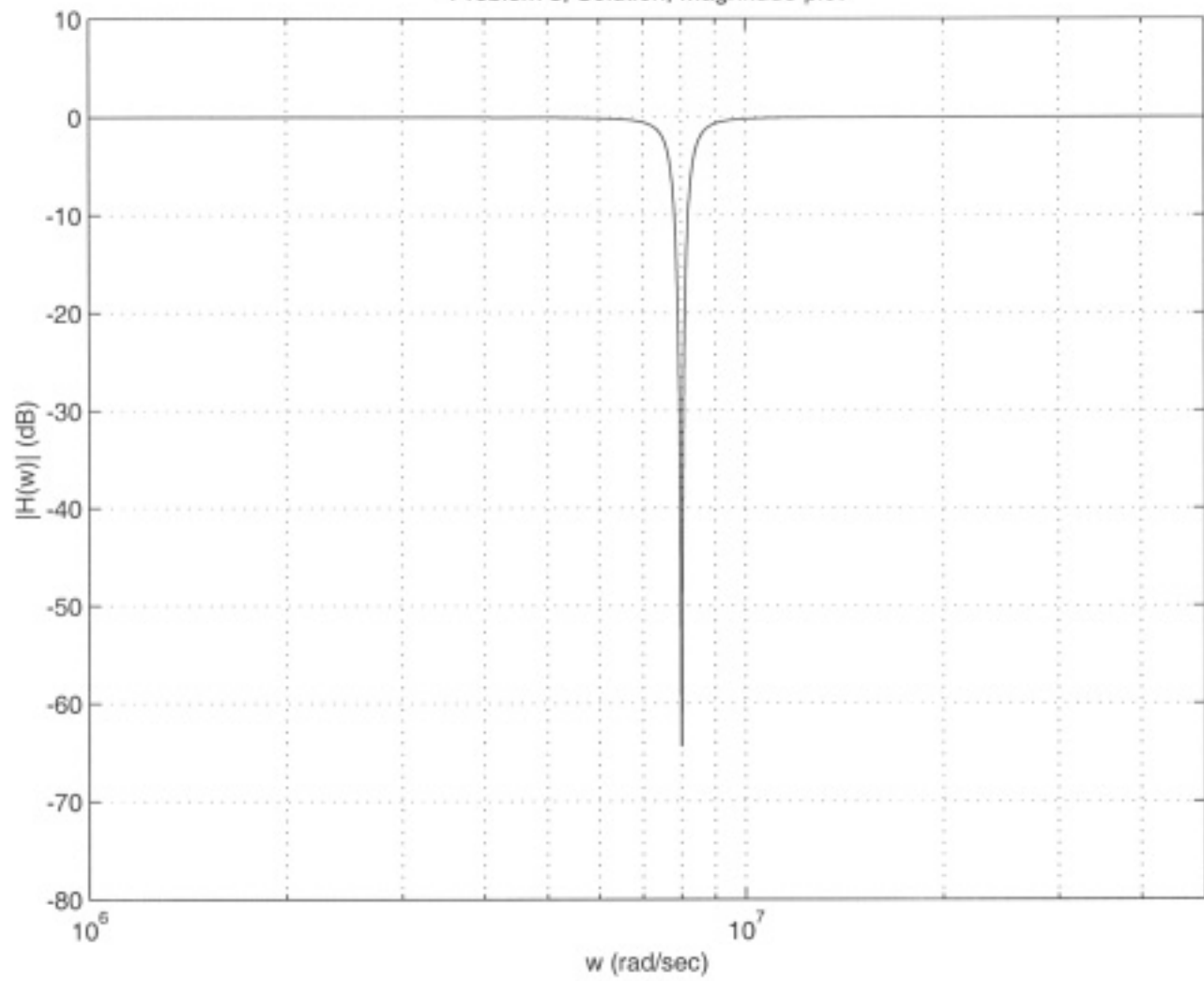

Problem 8, Solution, Phase plot

