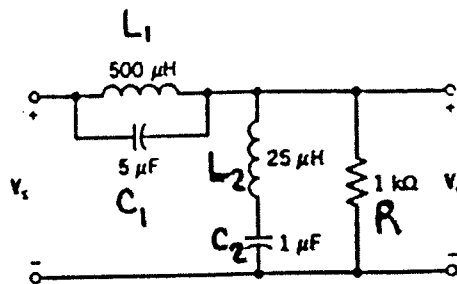



1. The following circuit is used to reject two unwanted signal frequencies. To simplify calculations let  $s = j\omega$ .



- Find the transfer function  $H(s) = \frac{V_o}{V_s}$ .
  - Make a Bode plot (magnitude & phase, use the Matlab command bode)
  - What are the two rejected frequencies?
2. Make a pole/zero for the following transfer function and sketch the asymptotic Bode plot.


$$H(s) = \frac{10s + 400}{s^3 + 10s^2 + 100s}$$

3. Consider the following circuit

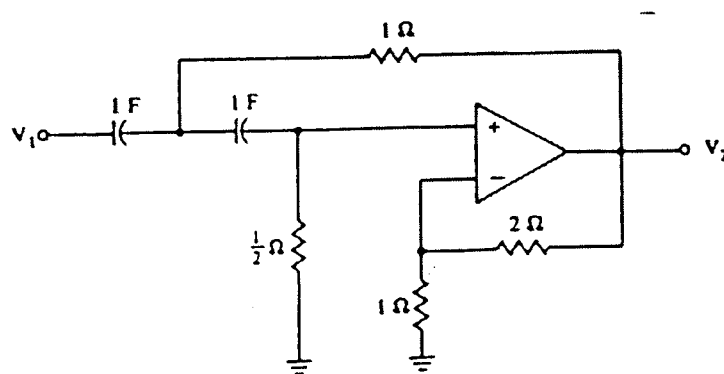


- (a) Derive the system transfer function  $H(s) = \frac{V_2}{V_1}$ . What kind of filter is this ?
- (b) Scale the circuit to obtain a high pass filter with a 3dB cutoff frequency  $\omega_c = 10 \text{ rad/s}$  ( $|H(\omega_c)| = 0.707|H(\infty)|$ ) using a  $0.02\mu\text{F}$  capacitors to replace the  $1\mu\text{F}$  capacitors.

4. Consider the following circuit

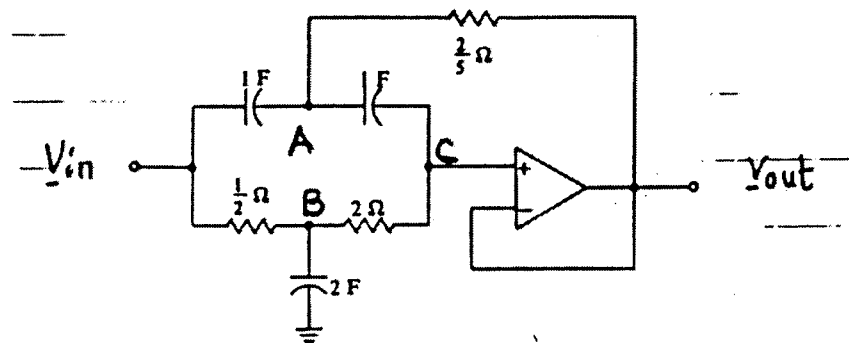

- (a) Write node equations at nodes A, B and C.
- (b) Derive the transfer function  $H(s) = \frac{V_{out}}{V_{in}}$ .
- (c) Show that the circuit acts as a bandstop filter with a center frequency of 1 rad/s & a Q of 1.
- (d) Scale the circuit to obtain a center frequency of 60Hz using capacitors of 1 and 2nF in place of 1F and 2F.

5. Consider the following circuit.

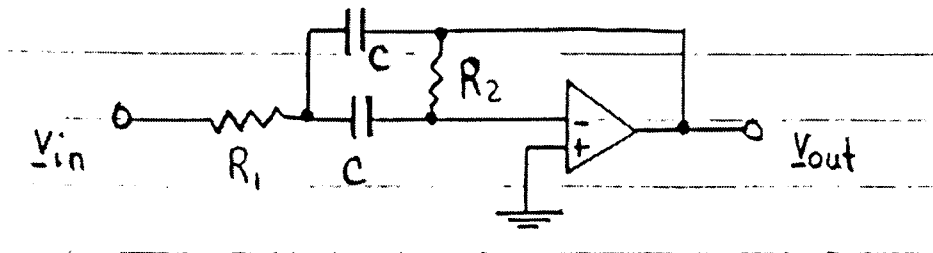

- (a) Derive the transfer function for this bandpass filter.
  - (b) Compute its center frequency and 3dB full-width bandwidth.
  - (c) The filter is to have a center frequency of 500Hz & a 3dB full-width bandwidth of 50Hz. Find  $R_1$ ,  $R_2$  if  $C=10\text{nF}$ . What is the filter gain at  $\omega_0$ ?
6. (a) Construct an asymptotic Bode plot (magnitude & phase) for the system transfer function

$$H(s) = \frac{10(1 + 0.1s)(1 + 0.01s)}{(1 + s)}$$

- (b) Plot the exact Bode plots using the Matlab command bode.

7. Determine the system transfer function associated with the following Bode plot.

