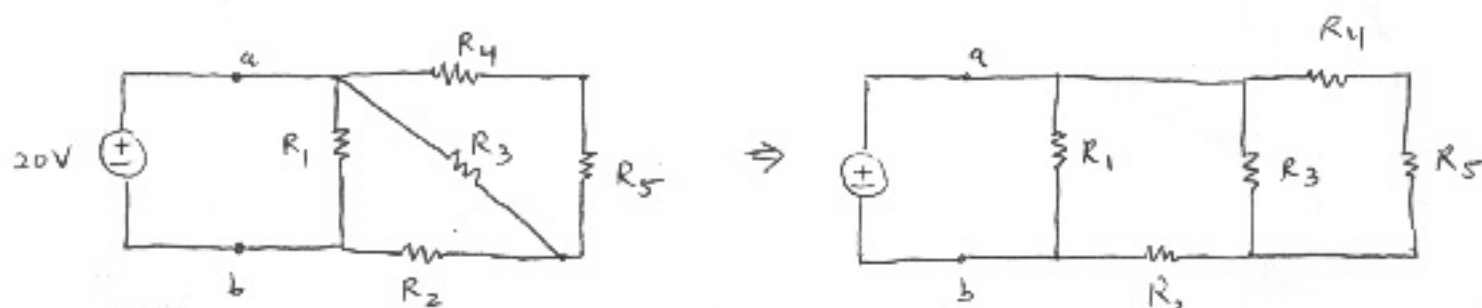
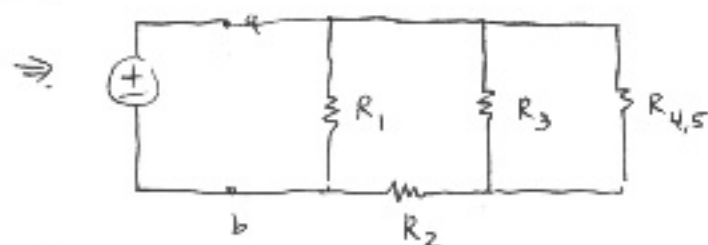
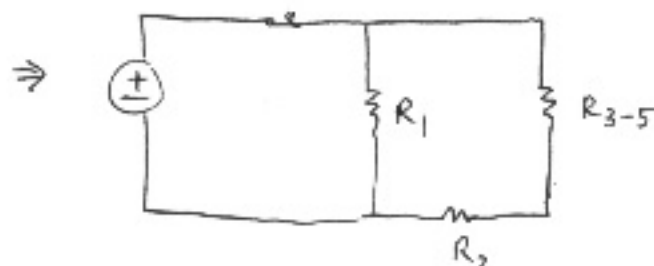


① 3.7a) Find R_{ab} .

Let circuit 3.7 a be:


• Note that R_4 and R_5 are in series.

$$\begin{aligned} \text{where } R_{4,5} &= R_4 + R_5 \\ &= 10 + 6 \\ &= \underline{16 \Omega} // \end{aligned}$$

• Note that R_3 and $R_{4,5}$ are in parallel.

$$\begin{aligned} \text{where } R_{3-5} &= \frac{R_3 \cdot R_{4,5}}{R_3 + R_{4,5}} \\ &= \frac{48 \cdot 16}{48 + 16} = \frac{48 \cdot 16}{64} \end{aligned}$$

$$R_{3-5} = \underline{12 \Omega} //$$

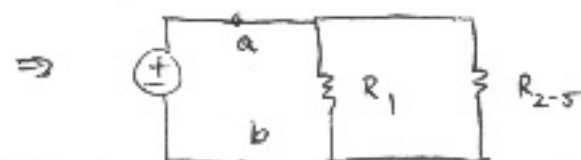
• Note that R_2 and R_{3-5} are in series.

$$\begin{aligned} \text{where } R_{2-5} &= R_2 + R_{3-5} \\ &= 18 + 12 \\ &= \underline{30 \Omega} // \end{aligned}$$

① 3.7

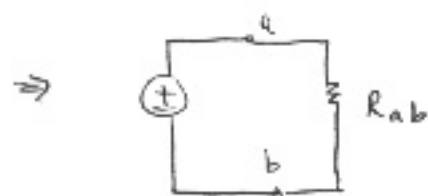(a) continued.

Note that R_1 and R_{2-5} are in parallel.





$$R_{ab} = \frac{R_1 \cdot R_{2-5}}{R_1 + R_{2-5}}$$


$$= \frac{15 \cdot 30}{15 + 30} = \frac{15 \cdot 30}{45}$$

$$R_{ab} = 10 \Omega$$

(a) circuit 3.7 b:

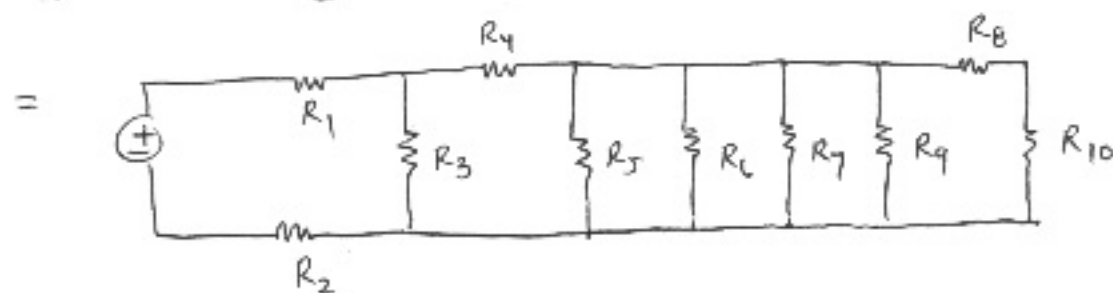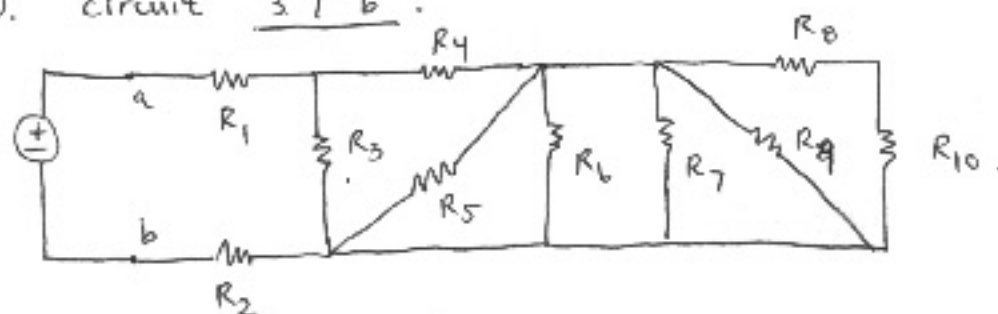

• Note R_3 and R_{10} are in series

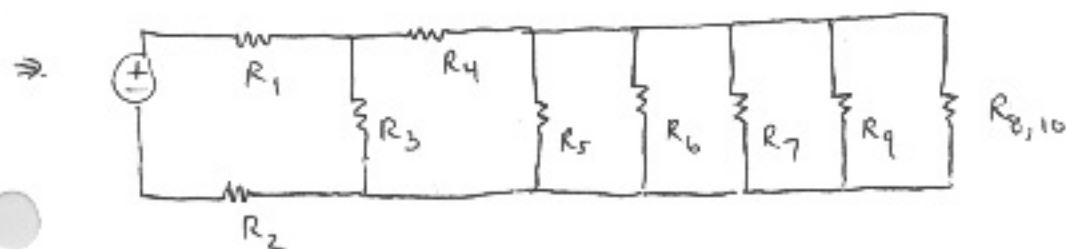


$$\begin{aligned} R_{8,10} &= R_8 + R_{10} \\ &= 6 + 14 \\ &= 20 \Omega \end{aligned}$$

• Note that $R_5, R_6, R_7, R_9, R_{8,10}$ are in parallel.

① 3.7

② continued.

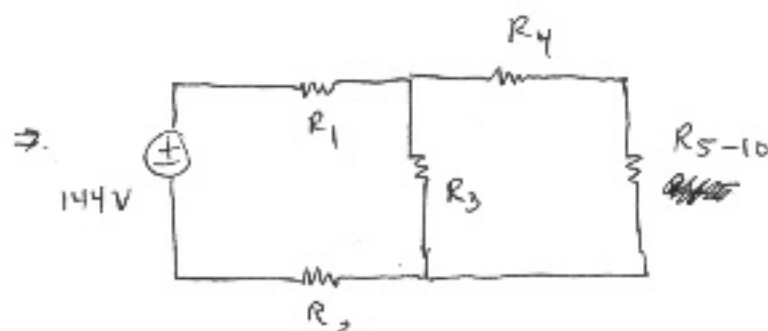


where

$$\frac{1}{R_{5-10}} = \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_7} + \frac{1}{R_4} + \frac{1}{R_{8,10}}$$

$$= \frac{1}{12} + \frac{1}{4} + \frac{1}{20} + \frac{1}{15} + \frac{1}{20}$$

$$= \frac{30}{60} \Rightarrow \underline{R_{5-10} = 2\Omega}$$

Note R_4 and R_{5-10} are in series.

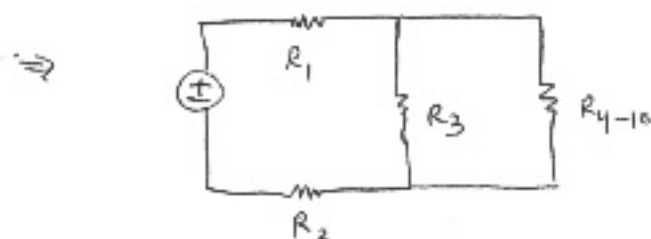


$$R_{4-10} = R_4 + R_{5-10}$$

$$= 16 + 2$$

$$= \underline{18\Omega}$$


Note R_3 and R_{4-10} are in parallel.

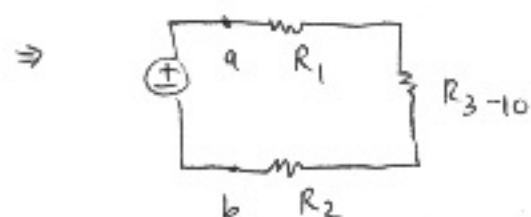

$$R_{3-10} = \frac{R_3 \cdot R_{4-10}}{R_3 + R_{4-10}}$$

$$= \frac{18 \cdot 18}{18 + 18} = \underline{9\Omega}$$

Note R_1 , R_{3-10} , R_2 are in series.

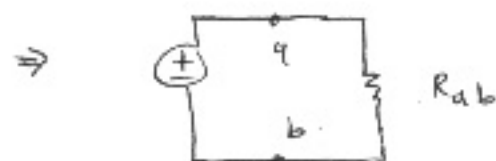


$$R_{ab} = R_1 + R_{3-10} + R_2$$


$$R_{ab} = 8 + 9 + 10 = \boxed{27\Omega}$$

① 3.7

circuit 3.7 c :

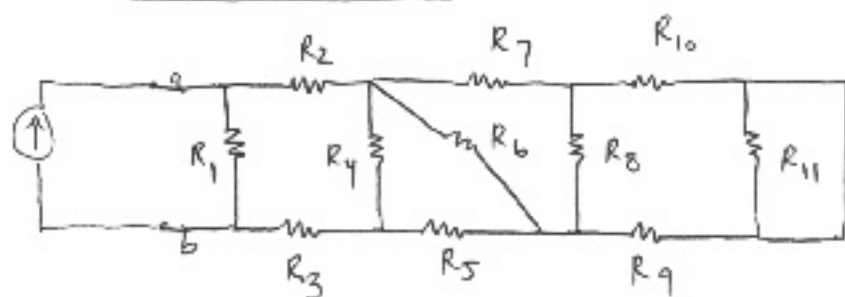

Note R_{11} is shorted.

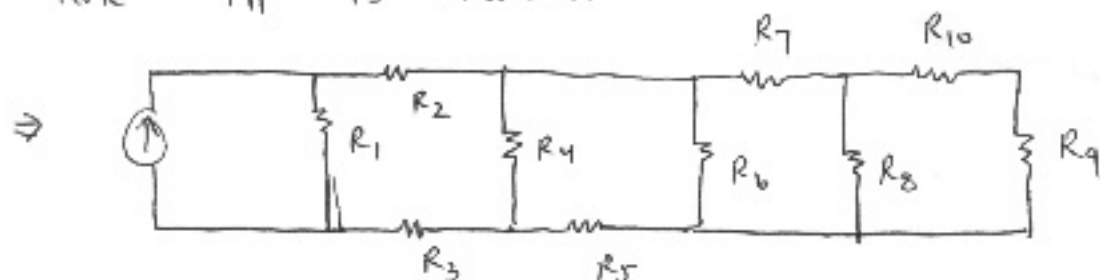


Note R_{10} and R_9 are in series.




$$\begin{aligned} R_{9,10} &= R_{10} + R_9 \\ &= 6 + 10 = 16\Omega \end{aligned}$$

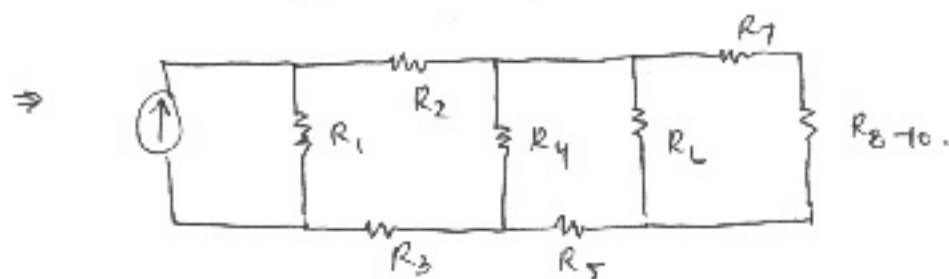Note. R_8 and $R_{9,10}$ are in parallel.



$$\begin{aligned} R_{8-10} &= \frac{R_8 \cdot R_{9,10}}{R_8 + R_{9,10}} \\ &= \frac{48 \cdot 16}{48 + 16} = 12\Omega \end{aligned}$$

Note R_7 and R_{8-10} are in series.

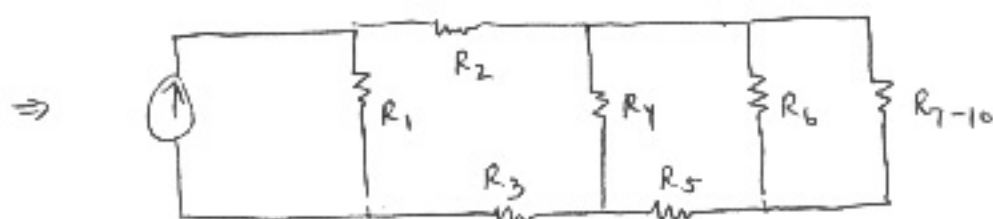


$$\begin{aligned} R_{7-10} &= R_7 + R_{8-10} \\ &= 8 + 12 = 20\Omega \end{aligned}$$

① 3.7

④ continued


Note R_6 and R_{7-10} are in parallel.

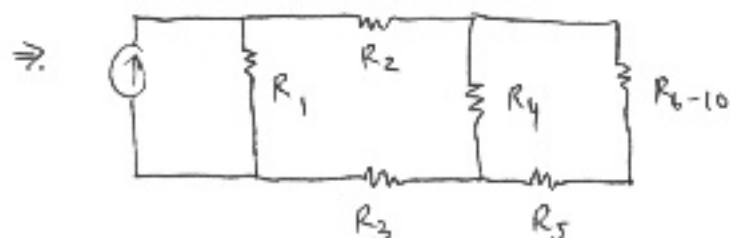

$$R_{6-10} = \frac{R_6 \cdot R_{7-10}}{R_6 + R_{7-10}}$$

$$= \frac{30 \cdot 20}{30 + 20} = \underline{12 \Omega}$$


Note R_5 and R_{6-10} are in series.

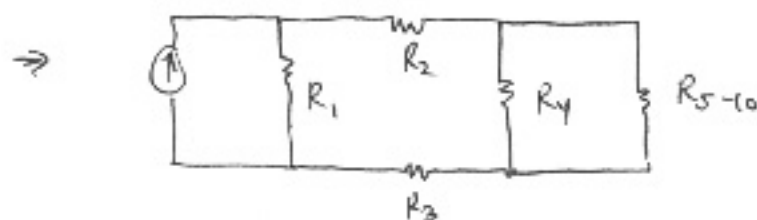

$$R_{5-10} = R_5 + R_{6-10}$$

$$= 18 + 12 = \underline{30 \Omega}$$


Note R_4 and R_{5-10} are in parallel.

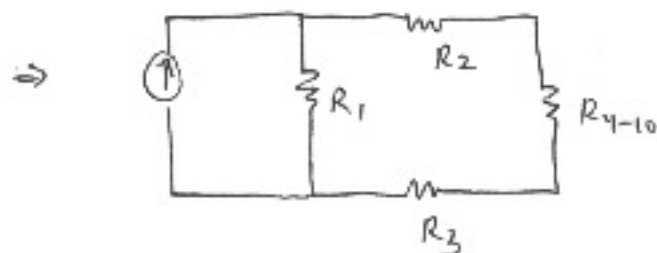

$$R_{4-10} = \frac{R_4 \cdot R_{5-10}}{R_4 + R_{5-10}} = \frac{15 \cdot 30}{15 + 30}$$

$$= \underline{10 \Omega}$$

Note R_2 , R_{4-10} , R_3 are in series.

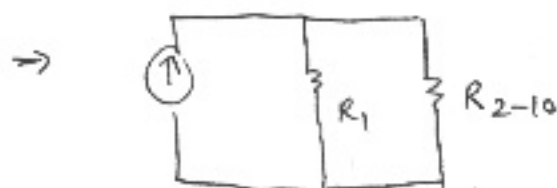


$$R_{2-10} = R_2 + R_{4-10} + R_3$$

$$= 20 + 10 + 10$$

$$= \underline{40 \Omega}$$

Note R_1 and R_{2-10} are in parallel.

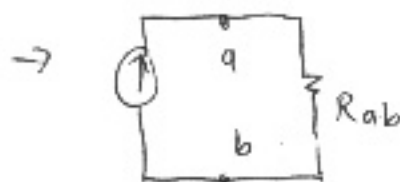

$$R_{ab} = \frac{R_1 \cdot R_{2-10}}{R_1 + R_{2-10}} = \frac{60 \cdot 40}{60 + 40} = \boxed{24 \Omega}$$

① 3.7

⑥. Find power delivered by each source.

ckt 3.7 a:

Recall



$$P = -IV$$

$$V = IR$$

$$\Rightarrow I = \frac{V}{R}$$

$$P = -\left(\frac{V}{R}\right)V$$

$$P = -\frac{V^2}{R}$$

$$\Rightarrow P_s = -\frac{V_s^2}{R_{ab}} = -\frac{(20\text{ V})^2}{10\Omega} = \boxed{-40\text{ W}} \quad \left(\begin{array}{l} 40\text{ W} \\ \text{delivered} \\ \text{power.} \end{array} \right)$$

ckt 3.7 b:




$$P = -IV$$

$$P = -\frac{V^2}{R}$$

$$\Rightarrow P_s = -\frac{V_s^2}{R_{ab}}$$

$$= -\frac{(144)^2}{27} = \boxed{+768\text{ W}} \quad \left(\begin{array}{l} 768\text{ W} \\ \text{delivered} \\ \text{power.} \end{array} \right)$$

ckt 3.7 c:

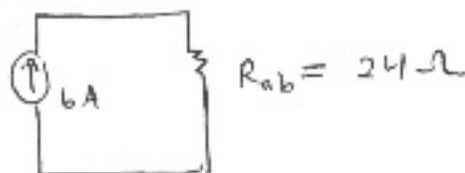

$$P = -IV$$

$$P = -I(IR)$$

$$P = -I^2 R$$


$$\Rightarrow P_s = -I_s^2 R_{ab}$$

$$= -(6\text{ A})^2 (24\Omega) = \boxed{-864\text{ W}} \quad \left(\begin{array}{l} 864\text{ W} \\ \text{delivered} \end{array} \right)$$

3.18

(a) Specify R_1, R_2 .

If no load resistor,

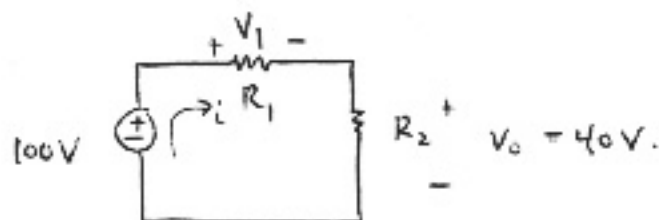

by KVL: $-100 + V_1 + 40 = 0$

$$V_1 = 100 - 40 = \underline{60V}$$

$$V_0 = i R_2$$

$$V_0 = \left(\frac{100}{R_1 + R_2} \right) R_2 \stackrel{\Delta}{=} 40V$$

Because

$$100 = i(R_1 + R_2)$$

$$i = \frac{100}{R_1 + R_2}$$


$$\Rightarrow \frac{R_2}{R_1 + R_2} = \frac{2}{5}$$

$$5R_2 = 2R_1 + 2R_2$$


$$3R_2 = 2R_1$$

$$\Rightarrow \boxed{R_1 = \frac{3}{2} R_2}$$

• Now with R_L ,

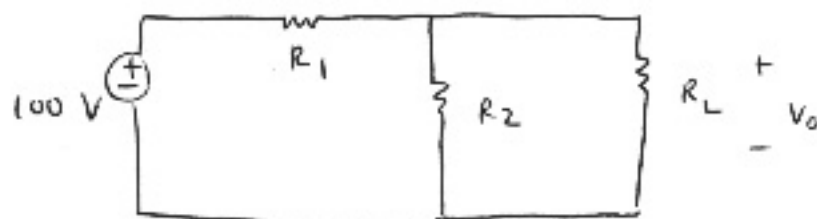

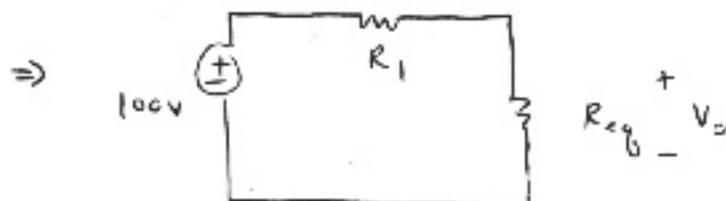let $R_{eq} = \frac{R_2 \cdot R_L}{R_2 + R_L}$



3.18

(a)

From simple circuit analysis,

$$V_o = 100 \cdot \frac{R_{eq}}{R_1 + R_{eq}}$$

$$V_o \geq 36 \text{ V} \quad (\text{given in problem}).$$

$$\Rightarrow 100 \cdot \frac{R_{eq}}{R_1 + R_{eq}} \geq 36$$

$$100 R_{eq} \geq 36 R_1 + 36 R_{eq}$$

$$64 R_{eq} \geq 36 R_1$$

$$\Rightarrow R_1 \leq \left(\frac{64}{36} \right) R_{eq}$$

$$R_1 \leq \left(\frac{64}{36} \right) \left[\frac{R_2 \cdot R_L}{R_2 + R_L} \right]$$

$$R_1 \leq \left(\frac{64}{36} \right) \left[\frac{\frac{2}{3} R_1 R_L}{\frac{2}{3} R_1 + R_L} \right]$$

$$\left(\frac{2}{3} R_1 + R_L \right) R_1 \leq \frac{16}{9} \left(\frac{2}{3} R_1 R_L \right)$$

$$\frac{2}{3} R_1 \leq \frac{32}{27} R_L - R_L$$

$$R_1 \leq \frac{3}{2} \left(\frac{5}{27} R_L \right)$$

$$R_1 \leq \frac{5}{18} R_L$$

$$R_1 \leq \frac{5}{18} \cdot 54 \text{ k}\Omega$$

$$\boxed{R_1 \leq 15 \text{ k}\Omega}$$

(a). We have derived that the requirement

$R_1 \leq 15 \text{ k}\Omega$ must be upheld in order for $V_o \geq 36 \text{ V}$

when $R_L = 54 \text{ k}\Omega$.

Let us make a chart for different values of R_1 and R_2 .

R_1	$R_2 = \frac{2}{3} R_1$	$R_{eq} = \frac{R_2 R_L}{R_2 + R_L}$	$V_o = V_s \frac{R_{eq}}{R_{eq} + R_1}$	$P_{R_1} = \frac{V_1^2}{R_1}$	$P_{R_2} = \frac{V_o^2}{R_2}$
15 k Ω	10 k Ω	8.4375 k Ω	36 V	0.2731 W	0.1296 W
12 k Ω	8 k Ω	6.968 k Ω	36.94 V	0.3413 W	0.162 W
9 k Ω	6 k Ω	5.4 k Ω	37.5 V	0.4551 W	0.216 W
6 k Ω	4 k Ω	3.724 k Ω	38.30 V	0.6827 W	0.324 W
3 k Ω	2 k Ω	1.93 k Ω	39.15 V	1.365 W	0.648 W

So, we can see that for $R_1 \leq 15 \text{ k}\Omega$ and the corresponding R_2 ($R_2 = \frac{2}{3} R_1$), the design specifications are met.

(b). if we select $R_1 = 15 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$, then, we can use resistors with power rating = 1 W

since $P_{R_1} = 0.2731 \text{ W} < 1 \text{ W}$ AND

$P_{R_2} = 0.1296 \text{ W} < 1 \text{ W}.$

3.19

Power rating for resistors = 0.5 W

From (3.18) chart, $8.192 \text{ k}\Omega \leq R_1 \leq 15 \text{ k}\Omega$.

will meet this requirement. (where $P_{R_1} = \frac{V_1^2}{R_1} \leq 0.5 \text{ W} \Rightarrow R_1 \geq 8.192 \text{ k}\Omega$)

We would like to find the smallest R_L possible before R_1 or R_2 is at its dissipation limit.

For the ensuing analysis we will use $R_1 = 15 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$.

$$\begin{aligned}\Rightarrow P_{R_1} &= \frac{V_1^2}{R_1} \leq 0.5 \text{ W} \\ V_1^2 &\leq 0.5 R_1 \\ V_1 &\leq \sqrt{0.5 (15,000)} \\ V_1 &\leq 86.6 \text{ V} \quad \parallel\end{aligned}$$

$$\begin{aligned}\text{by KVL,} \\ -V_s + V_1 + V_o &= 0 \\ V_o &= V_s - V_1 \\ V_o &= 100 - V_1 \\ V_o &\geq 100 - 86.6 \text{ V} \\ V_o &\geq 13.4 \text{ V} \quad \parallel\end{aligned}$$

Recall that

$$V_o = V_s \frac{R_{eq}}{R_1 + R_{eq}} \geq 13.4$$

$$\frac{R_{eq}}{R_1 + R_{eq}} \geq \frac{13.4}{100}$$

$$R_{eq} \geq 0.134 R_1 + 0.134 R_{eq}$$

$$0.866 R_{eq} \geq 0.134 (15,000)$$

$$R_{eq} \geq 2321 \Omega$$

3.19.

Recall that

$$R_{eq} = \frac{R_2 R_L}{R_2 + R_L} \geq 2321 \Omega.$$

$$\Rightarrow \frac{10000 R_L}{10,000 + R_L} \geq 2321$$

$$10,000 R_L \geq 2321(10^4) + 2321 R_L$$

$$7679 R_L \geq 2321 \times 10^4$$


$$R_L \geq 3022.5 \Omega.$$

So, $R_L \approx 3 \text{ k}\Omega$ is the smallest possible value

when $R_1 = 15 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$.

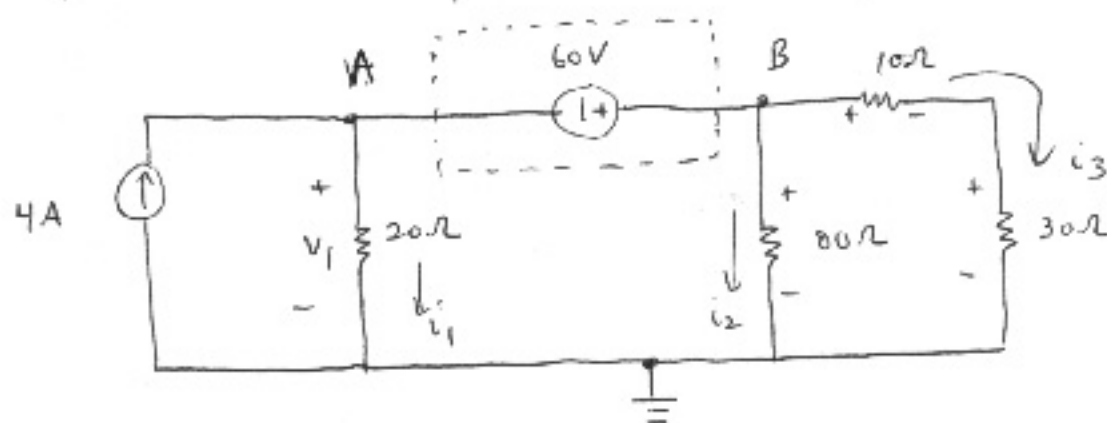4.3

Use the node-voltage method to find V_1 and the power delivered by the 60 V source.



- Use a super-node
- Sum currents leaving supernode.

$$\textcircled{1} \quad -4 + \frac{V_A}{20} + \frac{V_B}{80} + \frac{V_B}{10+30} = 0$$

$$\textcircled{2} \quad \text{Note that } V_B - V_A = 60 \text{ V.}$$

$$\text{Simplifying } \textcircled{1} \Rightarrow -320 + 4V_A + V_B + 2V_B = 0$$

$$4V_A + 3V_B = 320$$

$$4V_A + 3(V_A + 60) = 320$$

$$7V_A = 140$$

$$\boxed{V_A = 20 \text{ V}}$$

$$\Rightarrow V_B = V_A + 60$$

$$\boxed{V_B = 80 \text{ V}}$$

$$\therefore \boxed{V_1 = V_A = 20 \text{ V}}$$

4.3

Power delivered by 60 V source?

$$P_{60V} = -I V$$


$$= - (i_2 + i_3) (60V)$$

$$= - \left(\frac{V_B}{80} + \frac{V_B}{10+30} \right) (60)$$

$$= - (1 + 2) 60$$

$$= \boxed{-180 \text{ W}} \quad \left(\begin{array}{c} 180 \text{ W} \\ \text{delivered} \end{array} \right)$$

4.9

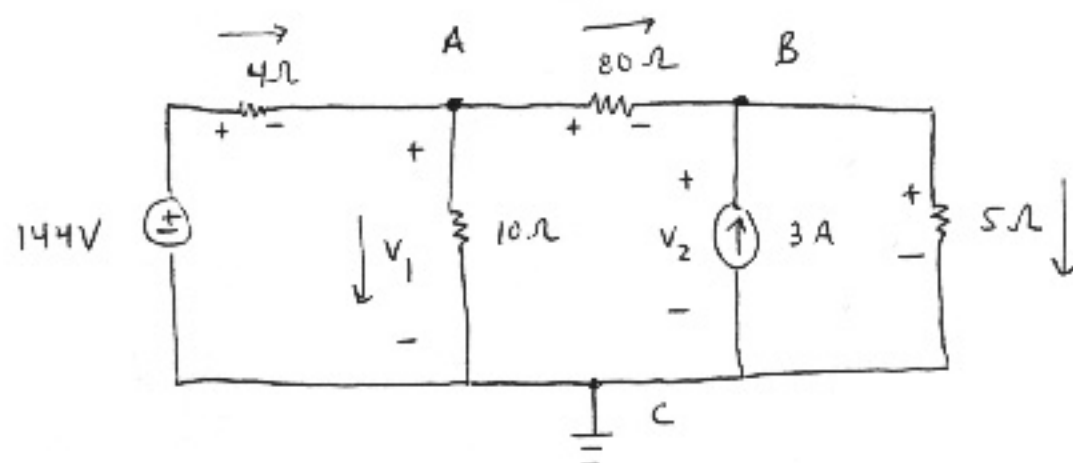Use node-voltage method to find V_1 and V_2 

Step 1: Sum currents going away from node A.

$$\textcircled{1} \quad -\frac{(-V_A + 144)}{4} + \frac{V_A}{10} + \frac{V_A - V_B}{80} = 0$$

$\uparrow$ current going through 4Ω Resistor
 $\uparrow$ current going through 10Ω resistor
 $\uparrow$ current going through 80Ω Resistor

Step 2: Sum currents going away from node B.

$$\textcircled{2} \quad -\frac{(V_A - V_B)}{80} - 3 + \frac{V_B}{5} = 0$$

$\uparrow$ current entering B through 80Ω
 $\swarrow$ current entering B from current source
 $\nwarrow$ current leaving B through 5Ω

$\therefore$ So we have 2 equations and 2 unknowns (V_A, V_B).

$$\textcircled{1} \Rightarrow \frac{V_A}{4} + \frac{-144}{4} + \frac{V_A}{10} + \frac{V_A}{80} - \frac{V_B}{80} = 0$$

$$\Rightarrow 20V_A - \frac{144(20)}{1} + 8V_A + V_A - V_B = 0$$

$$\underline{29V_A - V_B = 2880} //$$

4.9 :

Eqn (2) becomes :

$$-\frac{V_A}{80} + \frac{V_B}{80} - 3 + \frac{V_B}{5} = 0$$

$$-V_A + V_B - 240 + 16 V_B = 0$$

$$-V_A + 17 V_B = 240$$

$$V_A = 17 V_B - 240.$$

Substitute into (1) :

$$29 V_A - V_B = 2880$$

$$29 (17 V_B - 240) - V_B = 2880$$

$$493 V_B - 6960 - V_B = 2880$$

$$492 V_B = 6960 + 2880$$

$$V_B = 20 \text{ V}$$

$$V_A = 17 (20) - 240$$


$$V_A = 100 \text{ V}$$

Note,

$$V_1 = V_A = 20 \text{ V.}$$

$$V_2 = V_B = 100 \text{ V}$$

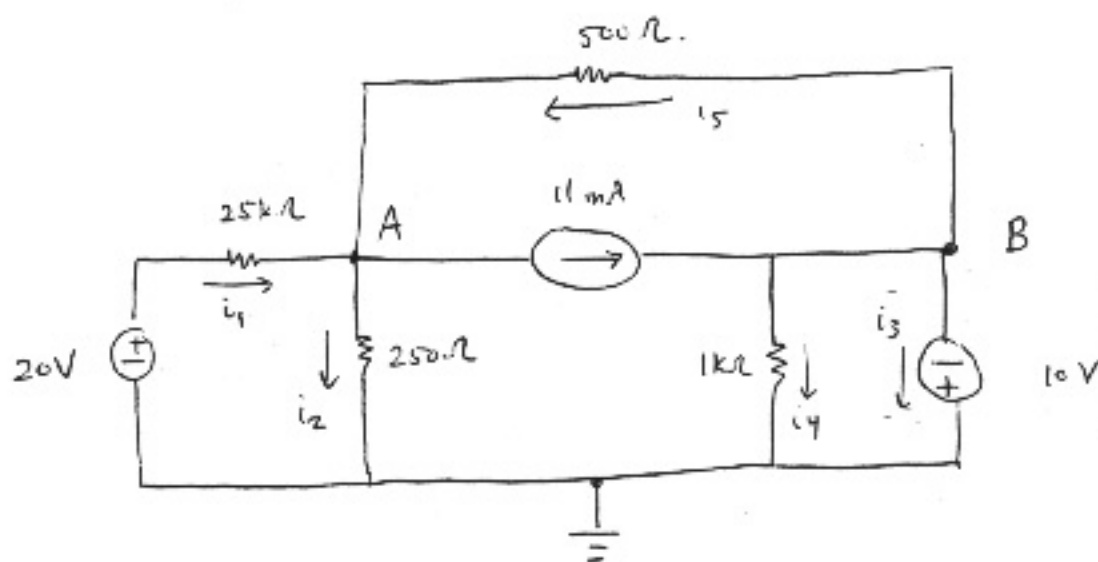4.16. (a) Use node-voltage method to find i_1 , i_2 , i_3



Step 1: Sum the currents going away from node A.

$$\textcircled{1} \quad \underbrace{-\frac{(20 - V_A)}{25\text{ k}\Omega}}_{\substack{\uparrow \\ -i_1}} + \underbrace{\frac{V_A}{250}}_{\substack{\uparrow \\ +i_2}} + \underbrace{0.011}_{\substack{\uparrow \\ \text{current source}}} - \underbrace{\frac{(V_B - V_A)}{500}}_{\substack{\uparrow \\ \text{current entering node A across } 500\ \Omega}} = 0$$

Note: $0 - V_B = 10\text{ V}$

$$V_B = -10\text{ V}$$

We can now solve for V_A in $\textcircled{1}$.

$$\textcircled{1} \Rightarrow \frac{-20}{25,000} + \frac{V_A}{25,000} + \frac{V_A}{250} + 0.011 - \frac{V_B}{500} + \frac{V_A}{500} = 0$$

$$V_A \left[\frac{1}{25,000} + \frac{1}{250} + \frac{1}{500} \right] = -0.011 + \frac{20}{25,000} + \frac{(-10)}{500}$$

$$V_A [1 + 100 + 50] = -275 + 20 - 500$$

$$V_A = \left(\frac{1}{151} \right) (-755) = -5\text{ V}$$

4.16

$$i_1 = \frac{20 - V_A}{25 \text{ k}\Omega}$$

$$= \frac{20 - (-5)}{25 \text{ k}\Omega}$$

$$i_1 = \frac{25}{25 \text{ k}\Omega} = 0.001 \text{ A}$$

$$i_2 = \frac{V_A}{250} = \frac{-5}{250} = -0.02 \text{ A}$$

$$i_3 = ?$$

by KCL at node B:

$$-i_3 + 0.011 - i_4 - i_5 = 0.$$

$$i_3 = 0.011 - i_4 - i_5$$

$$= 0.011 - \frac{V_B}{1000} - \frac{(V_B - V_A)}{500}$$

$$= 0.011 - \frac{(-10)}{1000} - \frac{(-10 - (-5))}{500}$$

$$i_3 = 0.031 \text{ A}$$

⑥. Check that power dissipated (absorbed) equals power developed (delivered).

$$P_{20V} = -(20V)(i_1)$$

$$= -(20V)(0.001A) \quad 0.02 \text{ W}$$

$$P_{20V} = -0.02 \text{ W}; \quad \text{(delivered)} //$$

4.16

①

$$\begin{aligned}
 P_{11mA} &= -VI \\
 &= -(V_B - V_A) \cdot 0.011A \\
 &= -(-10 - (-5)) 0.011 \\
 &= -(-5) 0.011 \quad (.055W) \\
 P_{11mA} &= 0.055W \quad (\text{absorbed})
 \end{aligned}$$

$$\begin{aligned}
 P_{10V} &= -VI \\
 &= -(V_B)(i_3) \\
 &= -(+10)(0.031A) \\
 P_{10V} &= -0.31W \quad (.31W \text{ delivered})
 \end{aligned}$$

$$\begin{aligned}
 P_{25k\Omega} &= i_1^2 R \\
 &= (0.001)^2 (25,000) \\
 &= 0.025W \quad (.025W \text{ absorbed})
 \end{aligned}$$

$$\begin{aligned}
 P_{250\Omega} &= i_2^2 (250) \\
 &= (-0.02)^2 (250) = 0.1W \quad (.1W \text{ absorbed})
 \end{aligned}$$

$$P_{500\Omega} = \frac{(V_B - V_A)^2}{500} = \frac{25}{500} = 0.05W \quad (.05W \text{ absorbed})$$


$$P_{1k\Omega} = \frac{V_B^2}{1000} = \frac{(100)}{1000} = 0.1W \quad (.1W \text{ absorbed})$$

$$\begin{aligned}
 P_{\text{Total absorbed}} &= 0.025W + 0.1W + 0.05W + 0.1W + 0.055W \\
 &= 0.33W
 \end{aligned}$$

$$P_{\text{Total delivered}} = -0.31 + -0.02 = -0.33W$$

$$P_{\text{Total absorbed}} + P_{\text{Total delivered}} = 0 \quad \checkmark$$

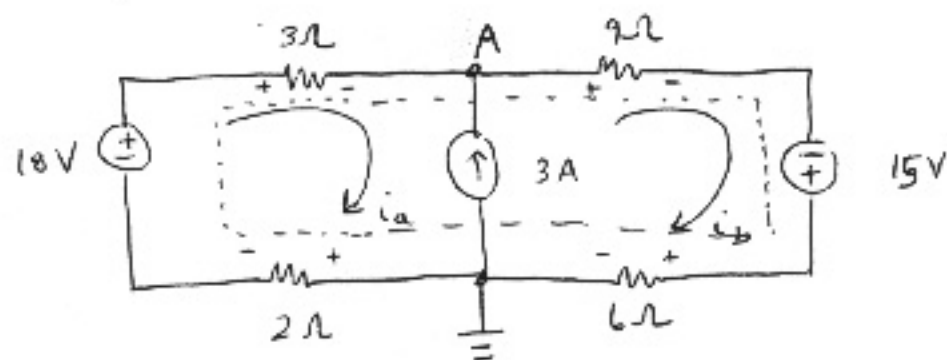4.27 : Use mesh-current method to find total power dissipated.



We can use super-mesh concept to simplify the analysis (refer to p. 130 in text).

Step 1 : Express voltages across resistors in terms of mesh currents and sum voltages around perimeter of circuit.

$$\textcircled{1} \quad -18 + i_a(3) + 9i_b - 15 + 6i_b + 2i_a = 0$$

$$\Rightarrow 5i_a + 15i_b = 33$$

Step 2 : The relationship between the mesh currents is :

$$i_b - i_a = 3 \text{ A}$$

$$\textcircled{2} \quad \Rightarrow i_b = i_a + 3$$

$\Rightarrow$ Substitute $\textcircled{2}$ into $\textcircled{1}$.

$$\Rightarrow 5i_a + 15(i_a + 3) = 33$$

$$5i_a + 15i_a + 45 = 33$$

$$20i_a = -12$$

$$\boxed{i_a = -\frac{3}{5} \text{ A}}$$

4.27

So,

$$i_b = i_a + 3$$

$$i_b = -\frac{3}{5} + 3$$

$$i_b = \underline{2\frac{2}{5} \text{ A}}$$

Now calculate power absorbed and delivered.

$$\begin{aligned} P_{18V} &= -1V \\ &= -i_a (18V) = -\left(-\frac{3}{5}\right)(18) = \underline{+10.8 \text{ W}} \quad \left(\begin{array}{l} 10.8 \text{ W} \\ \text{absorbed} \end{array} \right) \end{aligned}$$

$$\begin{aligned} P_{15V} &= -1V \\ &= -i_b (15V) = -\left(\frac{12}{5}\right)(15) = \underline{-36 \text{ W}} \quad \left(\begin{array}{l} 36 \text{ W} \\ \text{delivered} \end{array} \right) \end{aligned}$$

$$\begin{aligned} P_{3A} &= -1V \\ &= -(3A) \cdot V_A; \quad \text{where } V_A \text{ is the node voltage at } A \end{aligned}$$

Note from circuit,

$$2i_a - 18 + 3i_a + V_A = 0$$

$$V_A = 18 - 2i_a - 3i_a$$

$$V_A = 18 - 5i_a = 18 - 5\left(-\frac{3}{5}\right) = \underline{21V}$$

$$\Rightarrow P_{3A} = -3(21) = \underline{-63 \text{ W}} \quad \left(\begin{array}{l} 63 \text{ W} \\ \text{delivered} \end{array} \right)$$

$$\therefore P_{\text{Total delivered}} = -36 \text{ W} - 63 \text{ W} = \underline{-99 \text{ W}} \quad \left(\begin{array}{l} 99 \text{ W} \\ \text{delivered} \end{array} \right)$$

$$P_{3\Omega} = i_a^2 3 = \left(-\frac{3}{5}\right)^2 3 = \frac{9}{25} \cdot 3 = \frac{27}{25} = \underline{1.08 \text{ W}} \quad \left(\begin{array}{l} 1.08 \text{ W} \\ \text{absorbed} \end{array} \right)$$

$$P_{2\Omega} = i_a^2 2 = \left(-\frac{3}{5}\right)^2 2 = \frac{9}{25} \cdot 2 = \frac{18}{25} = \underline{0.72 \text{ W}} \quad \left(\begin{array}{l} 0.72 \text{ W} \\ \text{absorbed} \end{array} \right)$$


$$P_{4\Omega} = i_b^2 (4) = \left(\frac{12}{5}\right)^2 4 = \frac{144}{25} \cdot 4 = \underline{51.84 \text{ W}} \quad \left(\begin{array}{l} 51.84 \text{ W} \\ \text{absorbed} \end{array} \right)$$

$$P_{6\Omega} = i_b^2 (6) = \frac{144}{25} \cdot 6 = \underline{34.56 \text{ W}} \quad \left(\begin{array}{l} 34.56 \text{ W} \\ \text{absorbed} \end{array} \right)$$

$$\therefore P_{\text{Total Absorbed}} = \underline{99 \text{ W}} \quad \checkmark$$

4.31:

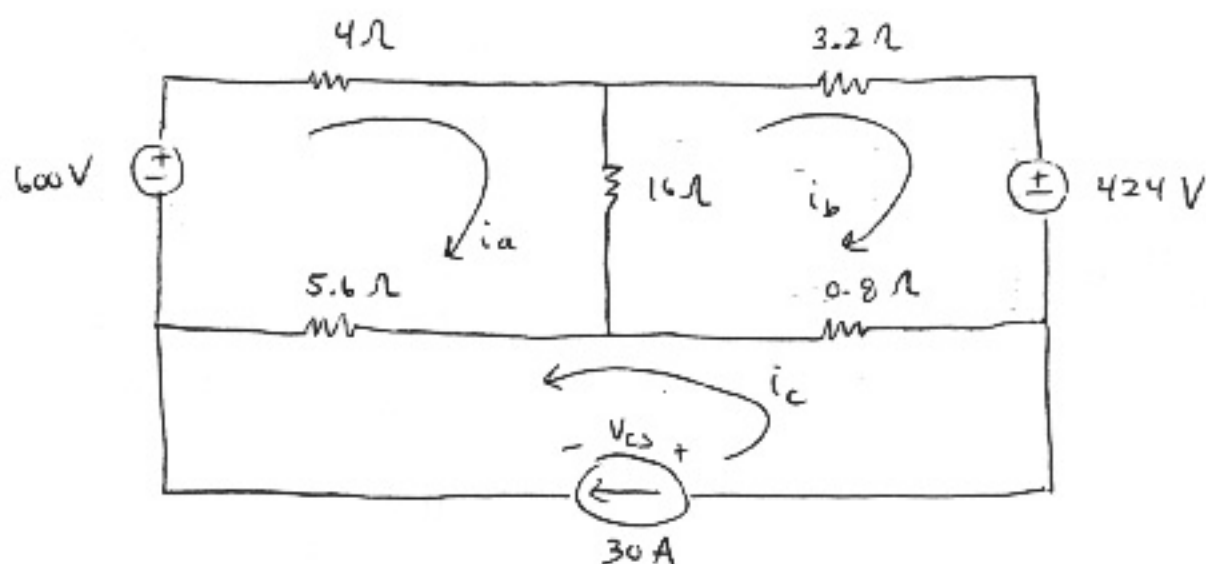- (a) Use mesh-current to find how much power 30A source delivers.



Step 1: Obtain mesh current equations from circuit.

- From top-left loop,

$$\textcircled{1} \quad -600 + i_a 4 + 16(i_a - i_b) + 5.6(i_a + i_c) = 0$$

$$\Rightarrow \boxed{-600 + 25.6 i_a - 16 i_b + 5.6 i_c = 0}$$

- From top-right loop,

$$\textcircled{2} \quad 3.2 i_b + 424 + 0.8(i_b + i_c) + 16(i_b - i_a) = 0$$

$$\Rightarrow \boxed{424 - 16(i_a) + 20 i_b + 0.8 i_c = 0}$$

- From bottom loop,

$$\textcircled{3} \quad \boxed{i_c = -30 \text{ A}} //$$

4.31 a)

Substituting ③ into ① and ②.

$$\textcircled{1} \Rightarrow -600 + 25.6 i_a - 16 i_b + 5.6(-30) = 0$$

$$i_a = 0.625 i_b + 30$$

$$\textcircled{2} \Rightarrow 424 - 16 i_a + 20 i_b + 0.8(-30) = 0$$

$$20 i_b = -400 + 16 i_a$$

$$i_b = \frac{4}{5} i_a - 20$$

$$\Rightarrow \text{so, } i_a = 0.625 \left(\frac{4}{5} i_a - 20 \right) + 30$$

$$\boxed{i_a = 35 \text{ A}}$$

$$i_b = \frac{4}{5} (35) - 20$$

$$\boxed{i_b = 8 \text{ A}}$$

Step 2: Find V_{cs} .

$$V_{cs} = 0.8 (i_c + i_b) + 5.6 (i_c + i_a)$$

$$\begin{aligned} V_{cs} &= 0.8 (-30 + 8) + 5.6 (-30 + 35) \\ &= 0.8 (-22) + 5.6 (5) \end{aligned}$$

$$\boxed{V_{cs} = 10.4 \text{ V}}$$

$$P_{cs} = -I \cdot V_{cs}$$

$$= -(-30 \text{ A})(10.4)$$

$$\boxed{P_{cs} = +312 \text{ W} \left(\begin{smallmatrix} 312 \text{ W} \\ \text{absorbed} \end{smallmatrix} \right)}$$

(cs: current source.)

4.31.

(b) Find power delivered.

$$\begin{aligned}P_{600V} &= -IV \\&= -i_a(600V) \\&= -35A(600V) \\&= \underline{-21 \text{ kW} \text{ (delivered.)} \text{ } ^{21 \text{ kW}}}\end{aligned}$$

$$\begin{aligned}P_{424V} &= -IV \\&= -(-i_b)(424V) \\&= (8A)(424V) \\&= \underline{3.392 \text{ kW} \text{ (absorbed.)} \text{ } ^{3.392 \text{ kW}}}\end{aligned}$$

So, total power delivered is 21 kW.

$$\therefore \textcircled{c}. \quad P_{4\Omega} = (i_a^2)4 = 35^2 4 = \underline{4900 \text{ W}}.$$

$$P_{5.6\Omega} = (i_a + i_b)^2 5.6 = 5^2 (5.6) = \underline{140 \text{ W}}$$

$$P_{3.2\Omega} = i_b^2 (3.2) = \underline{204.8 \text{ W}}.$$

$$P_{0.8\Omega} = (i_b + i_c)^2 (0.8) = \underline{387.2 \text{ W}}$$

$$P_{16\Omega} = (i_b - i_a)^2 (16) = \underline{11.664 \text{ kW}}.$$

Sum of power absorbed in all resistors = 17.296 kW.

$$\begin{aligned}\text{Total power absorbed} &= 17.296 \text{ kW} + 3.392 \text{ kW} \\&= \underline{21 \text{ kW}}.\end{aligned}$$