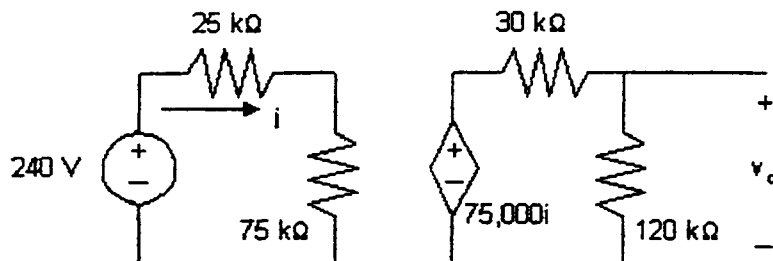


$$75 \parallel 150 = 50 \text{ k}\Omega$$

$$v_{o1} = \frac{240}{(25 + 50)}(50) = 160 \text{ V}$$

$$v_o = \frac{v_{o1}}{(150)}(120) = 128 \text{ V}, \quad v_o = 128 \text{ V}$$

[b]



$$i = \frac{240}{100} = 2.4 \text{ mA}$$

$$75,000i = 180 \text{ V}$$

$$v_o = \frac{180}{150}(120) = 144 \text{ V}; \quad v_o = 144 \text{ V}$$

[c] It removes loading effect of second voltage divider on the first voltage divider. Observe that the open circuit voltage of the first divider is

$$v'_{o1} = \frac{240}{(100)}(75) = 180 \text{ V}$$

Now note this is the input voltage to the second voltage divider when the current controlled voltage source is used.

P 3.18 [a] 
$$v_o = \frac{200R_2}{(R_1 + R_2)} \frac{150}{40}; \quad \text{Therefore } R_2 = 3R_1$$

$$\text{Let } R_e = R_2 \parallel R_L = \frac{R_2 R_L}{R_2 + R_L}$$

$$v_o = \frac{200R_e}{R_1 + R_e} = 100; \quad \text{Therefore } R_1 = R_e$$

$$\text{Thus, } R_2/3 = \frac{60R_2}{60 + R_2}$$

$$R_2 = 120 \text{ k}\Omega; \quad R_1 = 40 \text{ k}\Omega$$

[b] Power dissipated in  $R_1$  will be maximum when the voltage across  $R_1$  is maximum. This will occur under load conditions.

$$v_{R_1} = 200 - 100 = 100 \text{ V}; \quad P_{R_1} = \frac{(100)^2}{40 \times 10^3} = 250 \text{ mW}$$

So specify a  $1/4 \text{ W}$  power rating for the resistor.

P 3.19 Refer to the solution of Problem 3.18. The divider will reach its dissipation limit when the power dissipated in  $R_1$  equals  $1 \text{ W}$

$$\text{So } (v_{R_1}^2/40) = 1000; \quad v_{R_1} = 200 \text{ V} \quad v_o = 200 - 200 = 0 \text{ V}$$

$$\text{Therefore, } \frac{200R_e}{40 + R_e} = 0, \quad \text{and} \quad R_e = 0 \text{ k}\Omega$$

Thus,  $R_L = 0 \text{ k}\Omega$  (short circuit)

$$\text{P 3.20 [a]} \quad v_o = \frac{16(3.3)}{(4.7 + 3.3)} = 66 \text{ V}$$

$$\text{[b]} \quad i = 160/8 = 20 \text{ mA}$$

$$P_{R_1} = (400 \times 10^{-6})(4.7 \times 10^3) = 1.88 \text{ W}$$

$$P_{R_2} = (400 \times 10^{-6})(3.3 \times 10^3) = 1.32 \text{ W}$$

[c] Since  $R_1$  and  $R_2$  carry the same current and  $R_1 > R_2$  to satisfy the voltage requirement, first pick  $R_1$  to meet the  $0.5 \text{ W}$  specification

$$i_{R_1} = \frac{160 - 66}{R_1}, \quad \text{Therefore, } \left(\frac{94}{R_1}\right)^2 R_1 \leq 0.5$$

$$\text{Thus, } R_1 \geq \frac{94^2}{0.5} \quad \text{or} \quad R_1 \geq 17,672 \Omega$$

Now use the voltage specification:

$$\frac{R_2}{R_2 + 17,672}(160) = 66$$

$$\text{Thus, } R_2 = 12,408 \Omega$$

$$\text{P 3.21} \quad \frac{(24)^2}{R_1 + R_2 + R_3} = 36, \quad \text{Therefore, } R_1 + R_2 + R_3 = 16 \Omega$$

$$\frac{(R_1 + R_2)24}{(R_1 + R_2 + R_3)} = 12$$