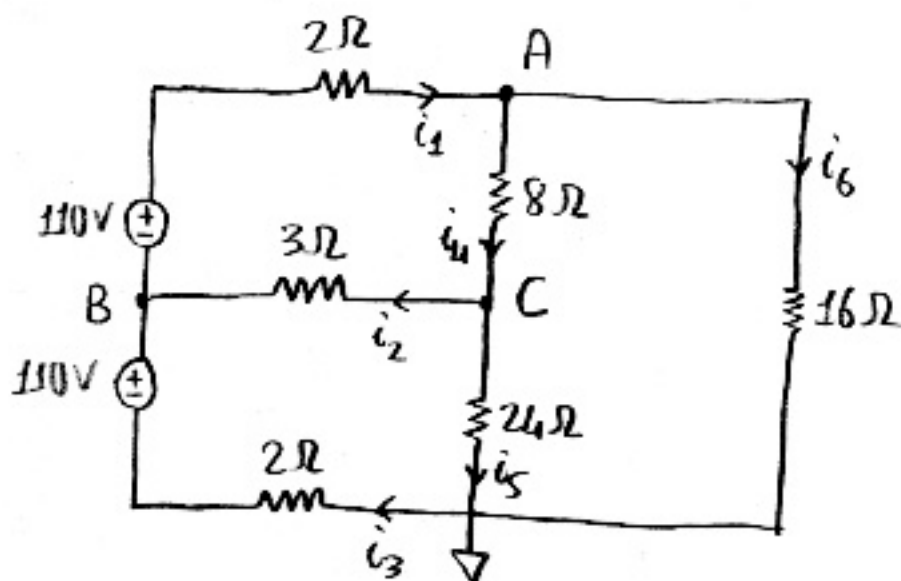


EECS 210

Homework #5 Solutions

(2) Problem 4.6 (a)



$$\text{Node A} \rightarrow \frac{V_A - (V_B + 110)}{2} + \frac{V_A - V_C}{8} + \frac{V_A}{16} = 0$$

$$\text{Node B} \rightarrow \frac{V_B - V_C}{3} + \frac{V_B - 110}{2} + \frac{V_B + 110 - V_A}{2} = 0$$

$$\text{Node C} \rightarrow \frac{V_C - V_B}{3} + \frac{V_C - V_A}{8} + \frac{V_C}{24} = 0$$

$$11V_A - 8V_B - 2V_C = 880$$

$$\Rightarrow -3V_A + 8V_B - 2V_C = 0$$

$$-3V_A - 8V_B + 12V_C = 0$$

$$\Rightarrow \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 157.14 \\ 82.5 \\ 94.285 \end{bmatrix} \text{ V}$$

(1)

$$i_1 = \frac{V_B + 110 - V_A}{2} = 17.68 \text{ A}$$

$$i_2 = \frac{V_C - V_B}{3} = 3.93 \text{ A}$$

$$i_3 = - \frac{(V_B - 110)}{2} = 13.75 \text{ A}$$

$$i_4 = \frac{V_A - V_C}{8} = 7.86 \text{ A}$$

$$i_5 = \frac{V_C}{24} = 3.93 \text{ A}$$

$$i_6 = 9.82 \text{ A}$$

Check KCL:


$$i_1 \stackrel{?}{=} i_4 + i_6 \quad \checkmark$$

$$i_4 \stackrel{?}{=} i_2 + i_5 \quad \checkmark$$

$$i_3 \stackrel{?}{=} i_5 + i_6 \quad \checkmark$$

$$i_1 \stackrel{?}{=} i_2 + i_3 \quad \checkmark$$

③ Problem 4.22

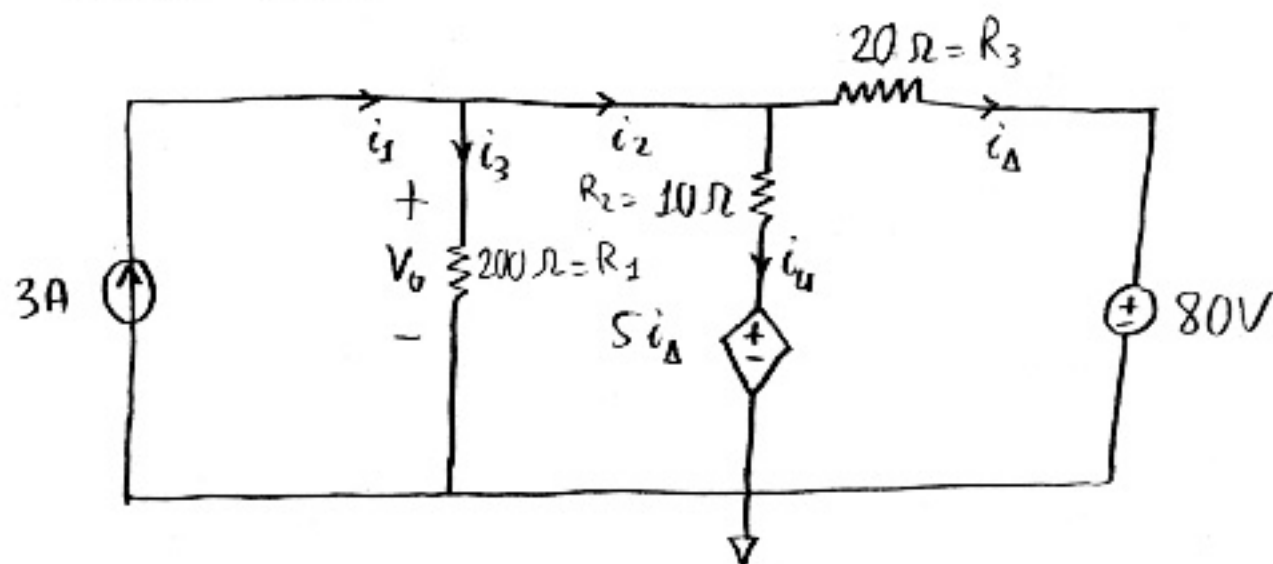

a) Find V_0 .

$$i_\Delta = \frac{V_0 - 80}{20}$$

$$-3 + \frac{V_0}{200} + \frac{V_0 - 5i_\Delta}{10} + \frac{V_0 - 80}{20} = 0$$

Inserting i_Δ in this equation yields:

$$V_0 = 38.46 \text{ V}$$

b) $i_\Delta = \frac{V_0 - 80}{20} = -2.077 \text{ A}$

$$i_4 = \frac{V_0 - 5i_\Delta}{10} = 4.8845 \text{ A} \Rightarrow P = i_4 \cdot 5i_\Delta = -50.7255 \text{ W}$$

(source is delivering power)

$$c) P_v = -80. \quad i_{\Delta} = -166.16 \text{ W} \quad (\text{source is delivering})$$

$$P_c = -V_o \cdot 3 = -115.2 \text{ W} \quad (\text{source is delivering})$$

$$\Rightarrow P_v + P_c = -231.36 \text{ W} //$$


Power check: $P_{\text{delivered}} = -50.72 - 166.16 - 115.2 = -332.08 \text{ W} //$

$$P_{\text{absorbed}} = \underbrace{P_{R_1} + P_{R_2} + P_{R_3}}_{\text{Use } \frac{V_i^2}{R_i}} = +332.08 \text{ W} // \checkmark$$

$$i_3 = i_2 - i_1 = \frac{V_B - V_C}{1} - \left(\frac{V_A - V_B}{2} \right) = -3.1 \text{ A}$$

$$\Rightarrow P = -20 \cdot i_3 = 62 \text{ W} // \text{ (source is absorbing power)}$$

⑤ Problem 4.37

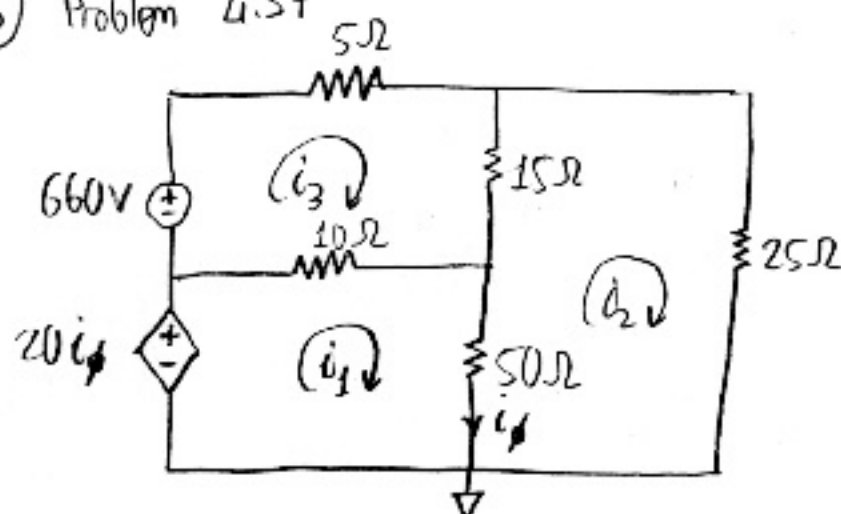

$$i_\phi = i_1 - i_2$$

$$-20i_\phi + 10(i_1 - i_3) + 50(i_1 - i_2) = 0$$

$$50(i_2 - i_1) + 15(i_2 - i_3) + 25i_2 = 0$$


$$5i_3 + 15(i_3 - i_2) + 10(i_3 - i_1) - 660 = 0$$

$$\Rightarrow \begin{aligned} 40i_1 - 30i_2 - 10i_3 &= 0 \\ -50i_1 + 90i_2 - 15i_3 &= 0 \\ -10i_1 - 15i_2 + 30i_3 &= 660 \end{aligned} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 27 \\ 22 \\ 42 \end{bmatrix} \text{ A}$$

$$\Rightarrow P = -20i_\phi \cdot i_1 = -20(i_1 - i_2) i_1 = -2700 \text{ W} //$$

(source is delivering power)

⑥ Problem 4.58

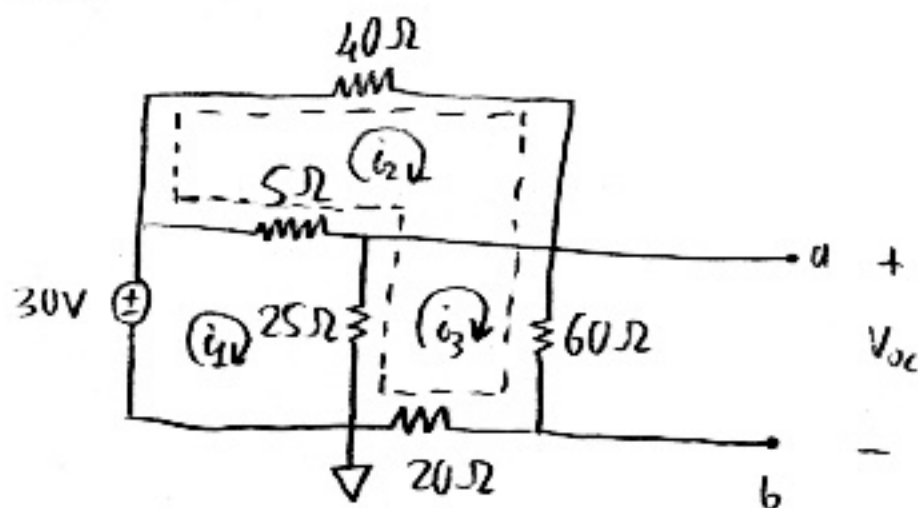

Supermesh: ① $25(i_3 - i_1) + 5(i_2 - i_1) + 40i_2 + 60i_3 + 20i_3 = 0$

② $i_3 - i_2 = 1.5$

③ $-30 + 5(i_1 - i_2) + 25(i_1 - i_3) = 0$

From ① and ②: $-30i_1 + 45i_2 + 105i_3 = 0$


$\Rightarrow \boxed{-30i_1 + 150i_2 = -157.5}$

From ② and ③: $30i_1 - 5i_2 - 25i_3 = 30$, $i_3 = i_2 + 1.5$

$\Rightarrow \boxed{30i_1 - 30i_2 = 67.5}$

$\Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1.5 \\ -0.75 \end{bmatrix} \Rightarrow V_{oc} = 60i_3 = 60(1.5 + i_2) = 45V //$

ii) I_{sc} :

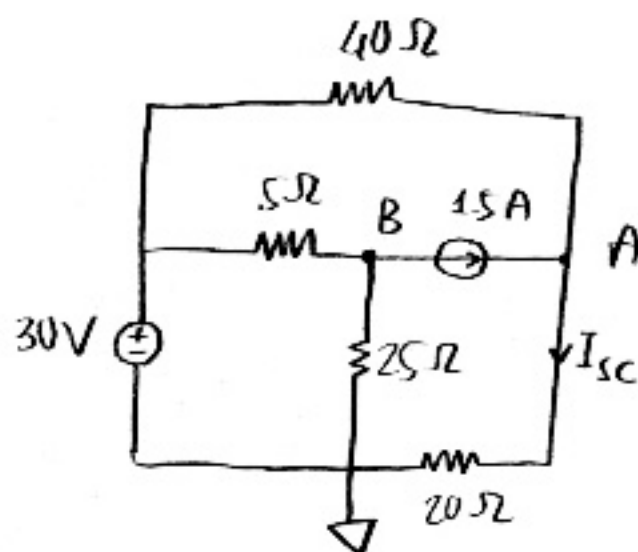

$$\text{Node A} \rightarrow -1.5 + \frac{V_A - 30}{40} + \frac{V_A}{20} = 0$$

$$\text{Node B} \rightarrow \frac{V_B - 30}{5} + \frac{V_B}{25} + 1.5 = 0$$


$$\Rightarrow V_A = 30V$$

$$V_B = 31.25V$$


$$\Rightarrow I_{sc} = \frac{V_A}{20} = 1.5A$$

$$R_T = \frac{V_{oc}}{I_{sc}} = \frac{45}{1.5} = 30\Omega$$


Thevenin:

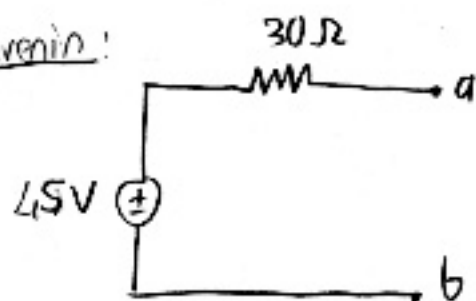

Norton:

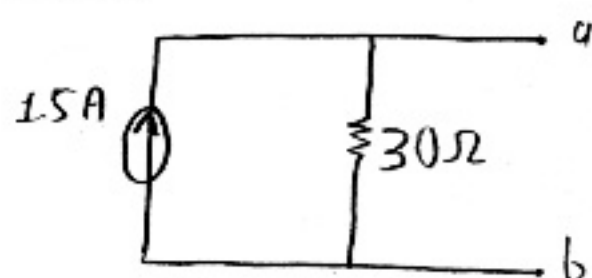

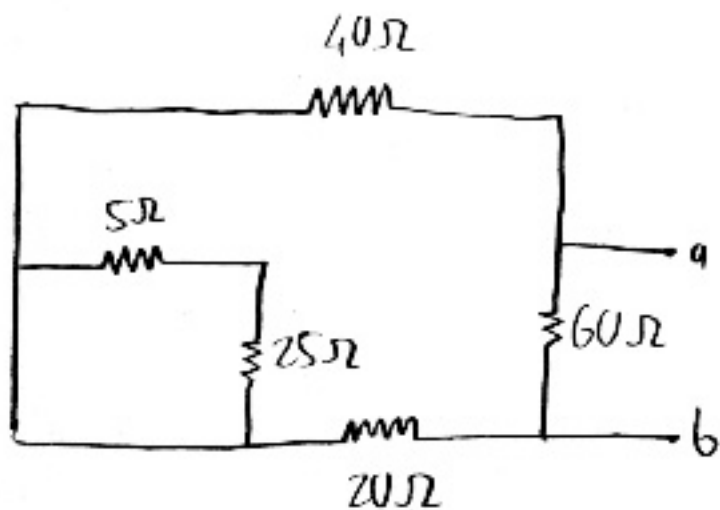
- b) Voltage source $\rightarrow$ O.C.
Current source $\rightarrow$ S.C.



$\leftarrow R_T = 60 // 60 = 30\Omega //$
Same result.

⑦ Problem 4.66

a) i) V_{oc} :

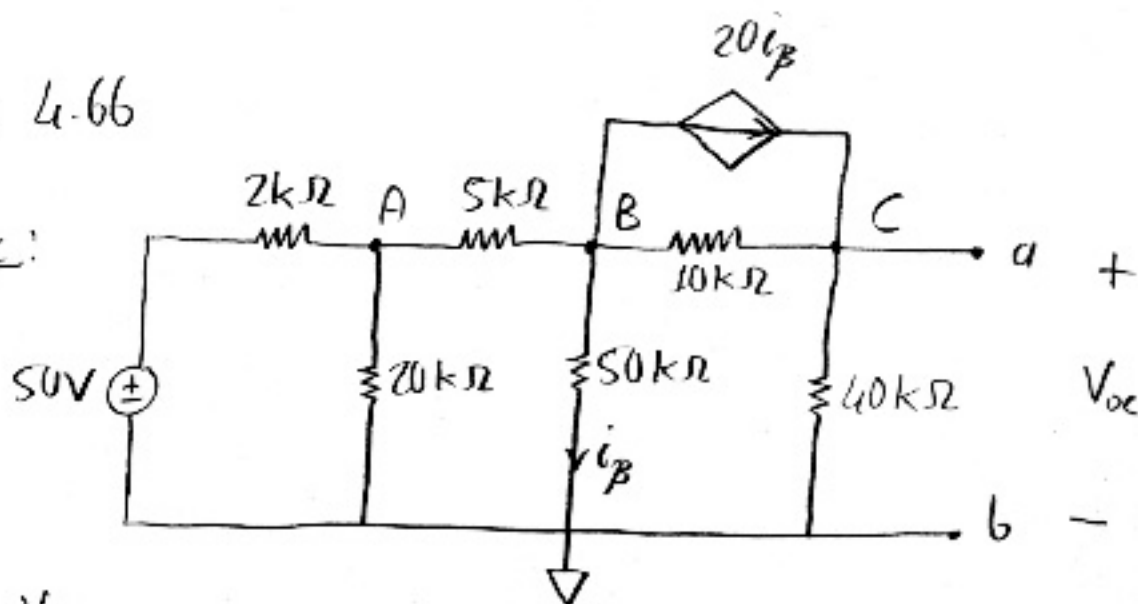

$$i_B = \frac{V_B}{50k}$$

$$\text{Node A} \rightarrow \frac{V_A - 50}{2k} + \frac{V_A - V_B}{5k} + \frac{V_A}{20k} = 0$$

$$\text{Node B} \rightarrow \frac{V_B - V_A}{5k} + \frac{V_B}{50k} + \frac{V_B - V_{oc}}{10k} + 20i_B = 0$$

$$\text{Node C} \rightarrow \frac{V_{oc} - V_B}{10k} - 20i_B + \frac{V_{oc}}{40k} = 0$$

$$15V_A - 4V_B = 500$$

$$V_A = 40V$$


$$\Rightarrow -10V_A + 36V_B - 5V_{oc} = 0 \Rightarrow$$

$$V_B = 25V$$

$$-100V_B + 25V_{oc} = 0$$

$$V_{oc} = 100V //$$

ii) I_{sc} :

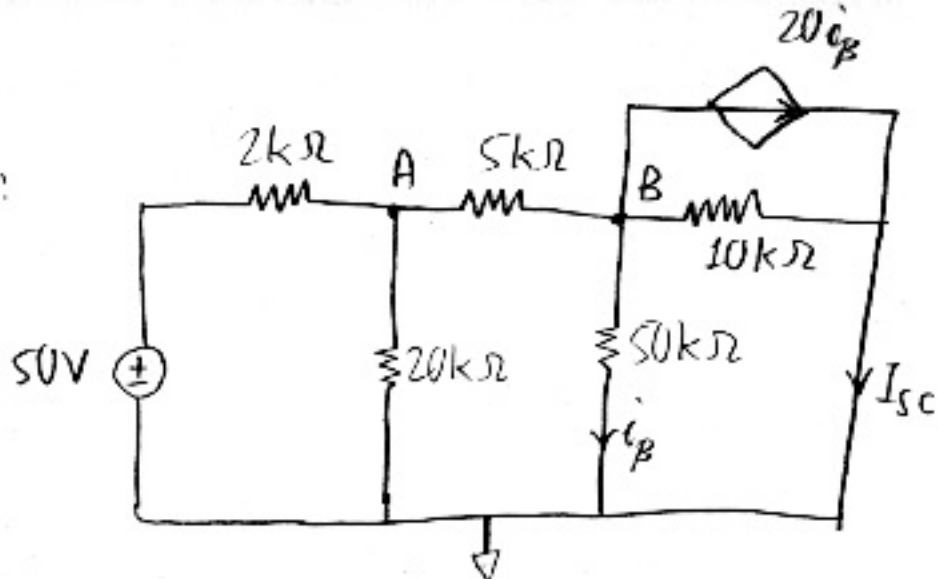

$$\text{Node A} \rightarrow \frac{V_A - 50}{2k} + \frac{V_A - V_B}{5k} + \frac{V_A}{20k} = 0$$


$$\text{Node B} \rightarrow \frac{V_B - V_A}{5k} + \frac{V_B}{50k} + \frac{V_B}{10k} + 20 \underbrace{i_B}_{\frac{V_B}{50k}} = 0$$

$$\Rightarrow \begin{aligned} 15V_A - 4V_B &= 500 \\ -10V_A + 36V_B &= 0 \end{aligned} \Rightarrow \begin{aligned} V_A &= 36V \\ V_B &= 10V \end{aligned}$$

$$I_{sc} = \frac{V_B}{10k} + 20 \underbrace{i_B}_{\frac{V_B}{50k}} = 5 \text{ mA}$$

$$\Rightarrow R_T = \frac{V_{oc}}{I_{sc}} = \frac{100}{5m} = 20 \text{ k}\Omega //$$

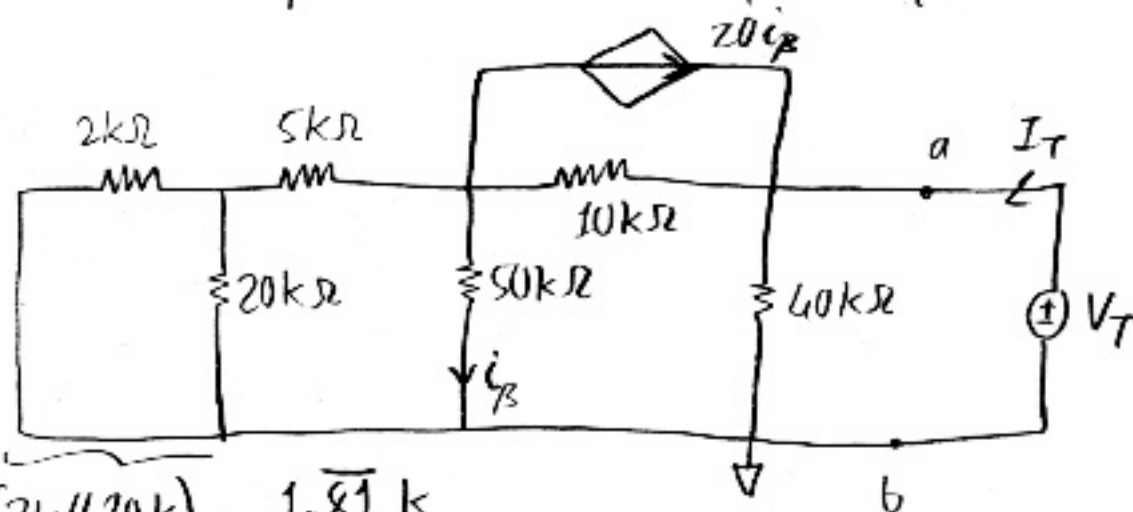b) Turn off independent sources to find R_T !




$$(2k // 20k) = 1.81 k$$

$$1.81 k + 5k = 6.81 k$$

$$6.81 k // 50k = 6 k\Omega$$

The circuit becomes:

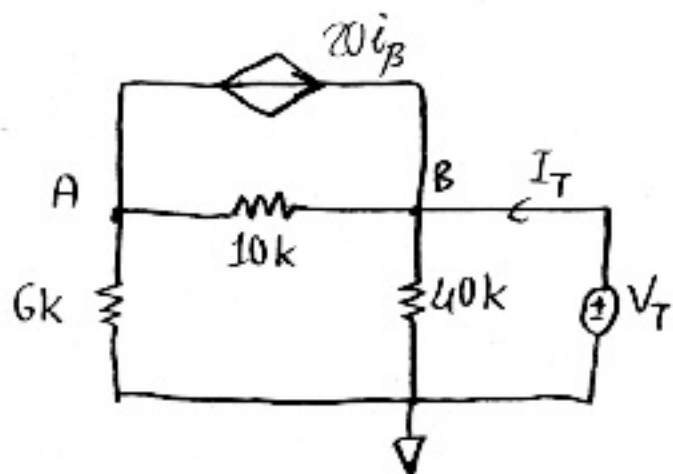

$$i_B = \frac{V_A}{50k}$$

$$\text{Node A} \rightarrow \frac{V_A}{6k} + \frac{V_A - V_T}{10k} + 20i_B = 0$$

$$\Rightarrow \boxed{V_A = \frac{3}{20} V_T}$$

$$\text{KCL at node B} \Rightarrow -20i_B - \frac{V_A - V_T}{10k} - I_T + \frac{V_T}{40k} = 0$$


$$\Rightarrow -\frac{2V_A}{5k} - \frac{V_A}{10k} + \frac{V_T}{10k} + \frac{V_T}{40k} = -I_T$$

$$\text{Using } V_A = \frac{3}{20} V_T, \text{ we get:}$$

$$\left(\frac{2}{5k} \cdot \frac{3}{20} + \frac{3}{200k} - \frac{1}{10k} - \frac{1}{40k} \right) V_T = -I_T$$

$$\Rightarrow R_T = \frac{V_T}{I_T} = 20 k\Omega // \text{ Same result as before.}$$

(2) Problem 4.70

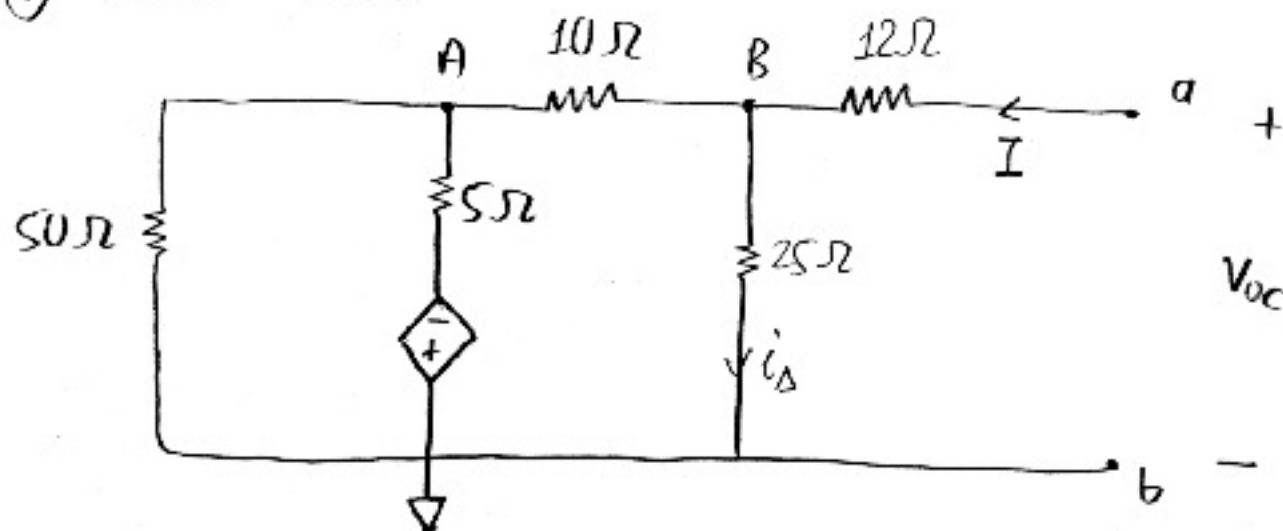

$$\text{Node A} \rightarrow \frac{V_A}{50} + \frac{V_A + 6.5i_A}{5} + \frac{V_A - V_B}{10} = 0$$

$$\text{Node B} \rightarrow \frac{V_B - V_A}{10} + \frac{V_B}{25} - I = 0 \quad i_A = \frac{V_B}{25}$$

$$\Rightarrow V_B = 6.6 V_A, \quad I = 0.83 V_A$$

$$V_{OC} = V_B + 12I = \frac{6.6}{0.83} I + 12I = 20I$$

$$\Rightarrow \boxed{R_T = 20\Omega, \quad V_{OC} = I_{SC} = 0}$$

(The voltage for the Thevenin equivalent and the current for the Norton equivalent are zero)