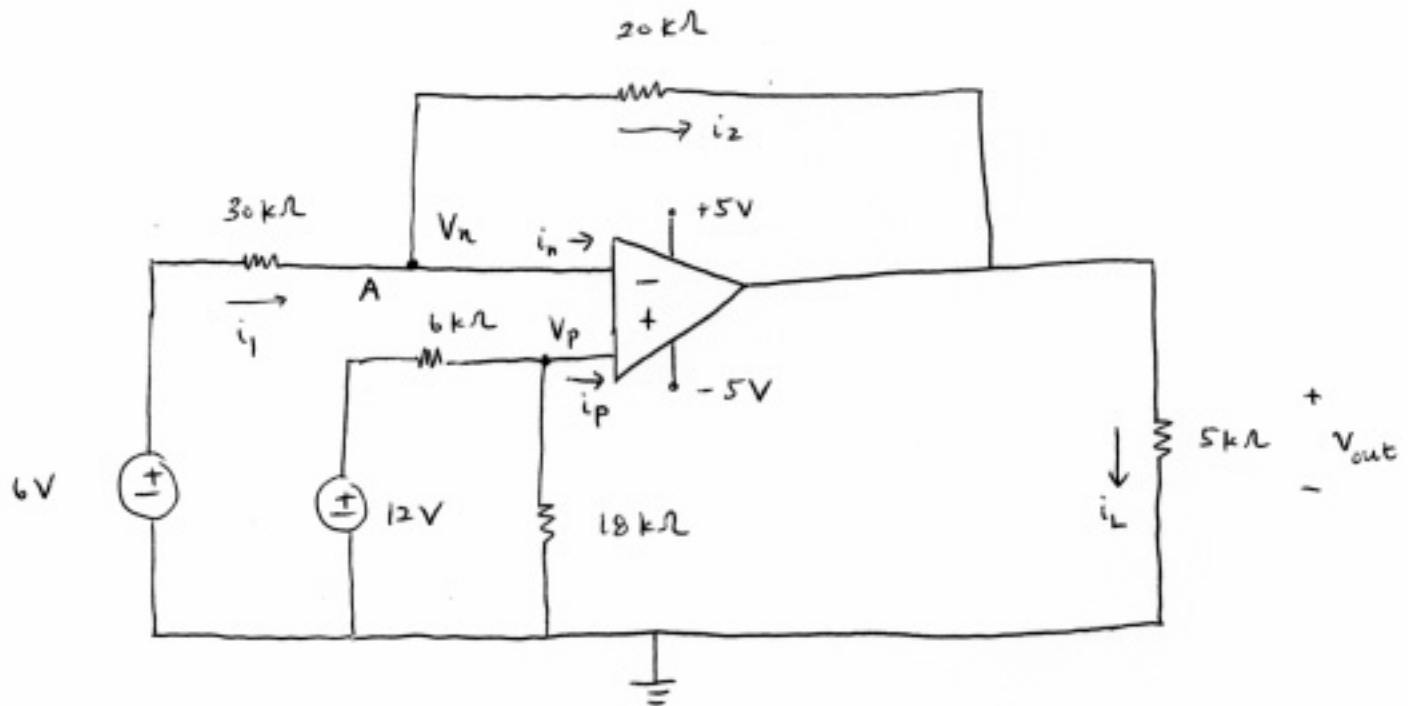


5.2Find i_L in the circuit.

- Since $i_p = 0$, by a voltage divider

$$V_p = \frac{18 \text{ (1000)}}{18,000 + 6000} (12 \text{ V}) = 9 \text{ V}$$

From the golden rules, $V_p = V_n = 9 \text{ V}$.

- Apply node-voltage analysis at node A:

$$i_n = 0$$

$$-i_1 + i_2 = 0$$


$$-\frac{(6 - 9)}{30,000} + \frac{(9 - V_{out})}{20,000} = 0$$

$$\Rightarrow \underline{V_{out} = 11 \text{ V}}$$

- (a) Because $+V_{cc} = 5 \text{ V}$, op amp output saturated at 5 V .

$$i_L = \frac{5 \text{ V}}{5000 \Omega} = 1 \text{ mA} = \boxed{1000 \mu \text{ A}}$$

- (b) Since $-15 \text{ V} \leq V_{out} \leq 15 \text{ V}$, $\underline{V_{out} = 11 \text{ V}} \Rightarrow i_L = \frac{11 \text{ V}}{5000 \Omega} = \boxed{2200 \mu \text{ A}}$

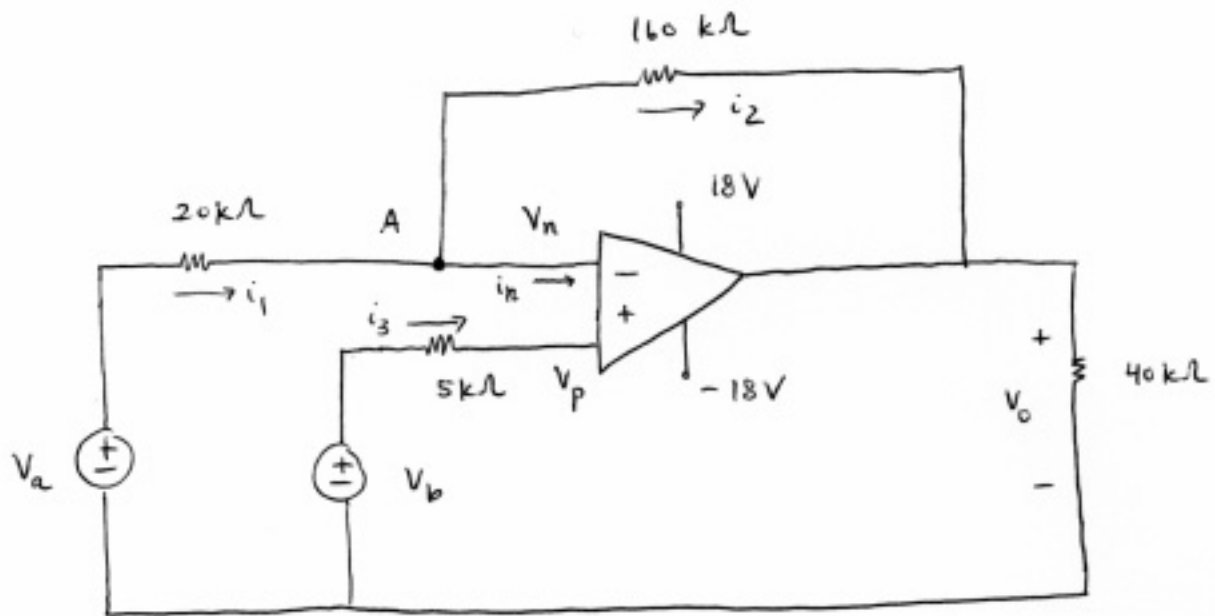5.3Find V_o :Node-voltage analysis at node A:

$$i_n = 0$$

$$-i_1 + i_2 = 0$$

$$\Rightarrow \frac{V_a - V_n}{20,000} = \frac{V_n - V_o}{160,000} \quad \text{eqn ①}$$

Note that $i_3 = 0$

$$\Rightarrow V_p = V_b$$

$$\text{Also, } V_p = V_n = V_b.$$

From eqn ①,

$$\frac{V_a - (V_b)}{20,000} = \frac{(V_b) - V_o}{160,000}$$

$$\Rightarrow \boxed{V_o = 9V_b - 8V_a}$$

5.3. Now substitute in given values of v_b and v_a

(a) $V_o = 9(0) - 8(1.5 \text{ V})$

$$V_o = -12 \text{ V}$$

(b) $V_o = -24 \text{ V}$

But $-V_{cc} = -18 \text{ V}$ so output of op amp saturates at -18 V .

$$V_o = -18 \text{ V}$$

(c) $V_o = 10 \text{ V}$

(d) $V_o = -14 \text{ V}$

(e) $V_o = 24 \text{ V}$. But $+V_{cc} = 18 \text{ V}$, so output of op amp saturates at 18 V .

$$V_o = 18 \text{ V}$$

(f) $v_b = 4.5 \text{ V}$. Specify range of v_a such that op amp does NOT saturate.


$$\Rightarrow -18 \leq V_o \leq 18$$

$$-18 \leq (9v_b - 8v_a) \leq 18$$

$$\Rightarrow \boxed{2.81 \text{ V} \leq v_a \leq 7.31 \text{ V}}$$

5.4

4

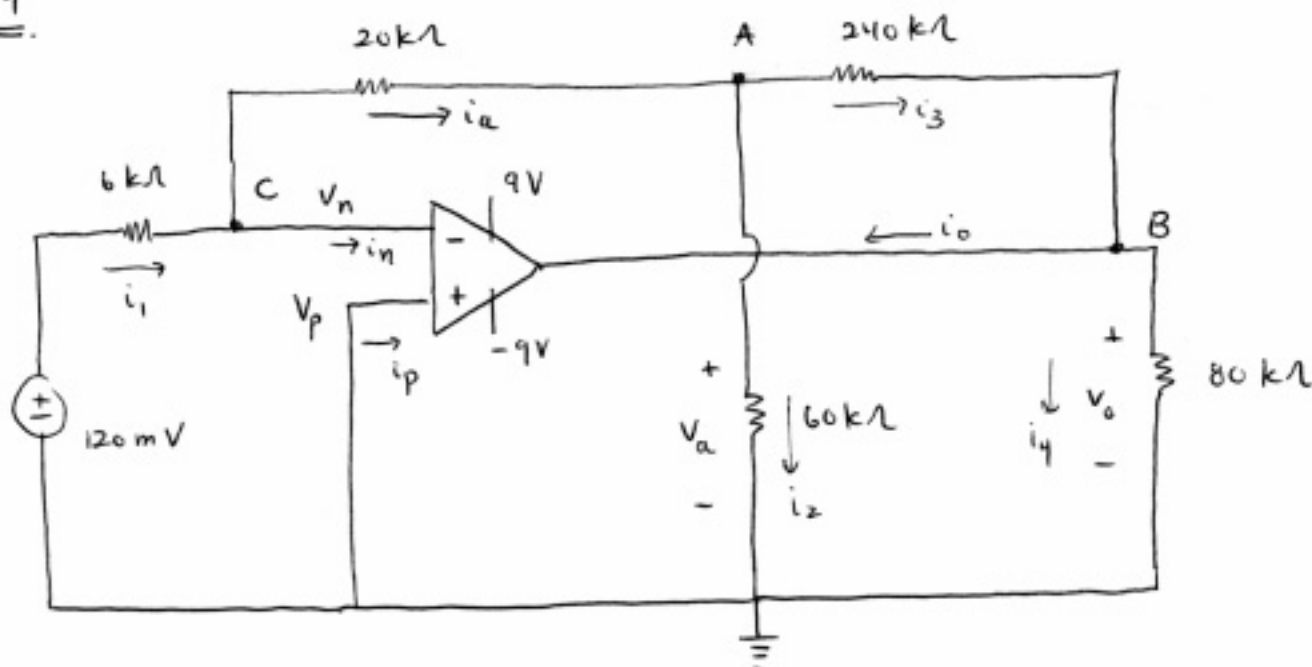(a) Find V_a

• Node-voltage analysis at node C:

$$\begin{aligned}
 i_n &= 0 \\
 -i_1 + i_a &= 0 \\
 \Rightarrow i_a &= i_1 \\
 \frac{V_n - V_A}{20,000} &= \frac{0.120 - V_n}{6000}
 \end{aligned}$$

Note that $V_p = 0$
 $V_n = V_p = 0.$

$$\Rightarrow \frac{-V_A}{20,000} = \frac{0.120}{6000}$$

$$V_A = -0.4 \text{ V}$$

$$\boxed{V_a = -0.4 \text{ V}}$$

(b) Find V_o :

• Node-voltage analysis at node A:

$$\begin{aligned}
 -i_a + i_2 + i_3 &= 0 \\
 \Rightarrow -\frac{(V_n - V_A)}{20,000} + \frac{V_A}{60,000} + \frac{V_A - V_B}{240,000} &= 0
 \end{aligned}$$

$$\boxed{V_B = -6.8 \text{ V}} \Rightarrow V_o = V_B = -6.8 \text{ V} //$$

5.4(c) Find i_a .

$$i_a = \frac{V_h - V_A}{20,000} = \frac{0.4}{20,000} = \boxed{20 \mu A} //$$

(d) Find i_o KCL at node B:

$$i_o - i_3 + i_4 = 0$$


$$i_o = i_3 - i_4$$

$$= \frac{V_A - V_B}{240,000} - \frac{V_B}{80,000}$$

$$= \frac{V_a - V_o}{240,000} - \frac{V_o}{80,000}$$

$$\boxed{i_o = 111.7 \mu A}$$

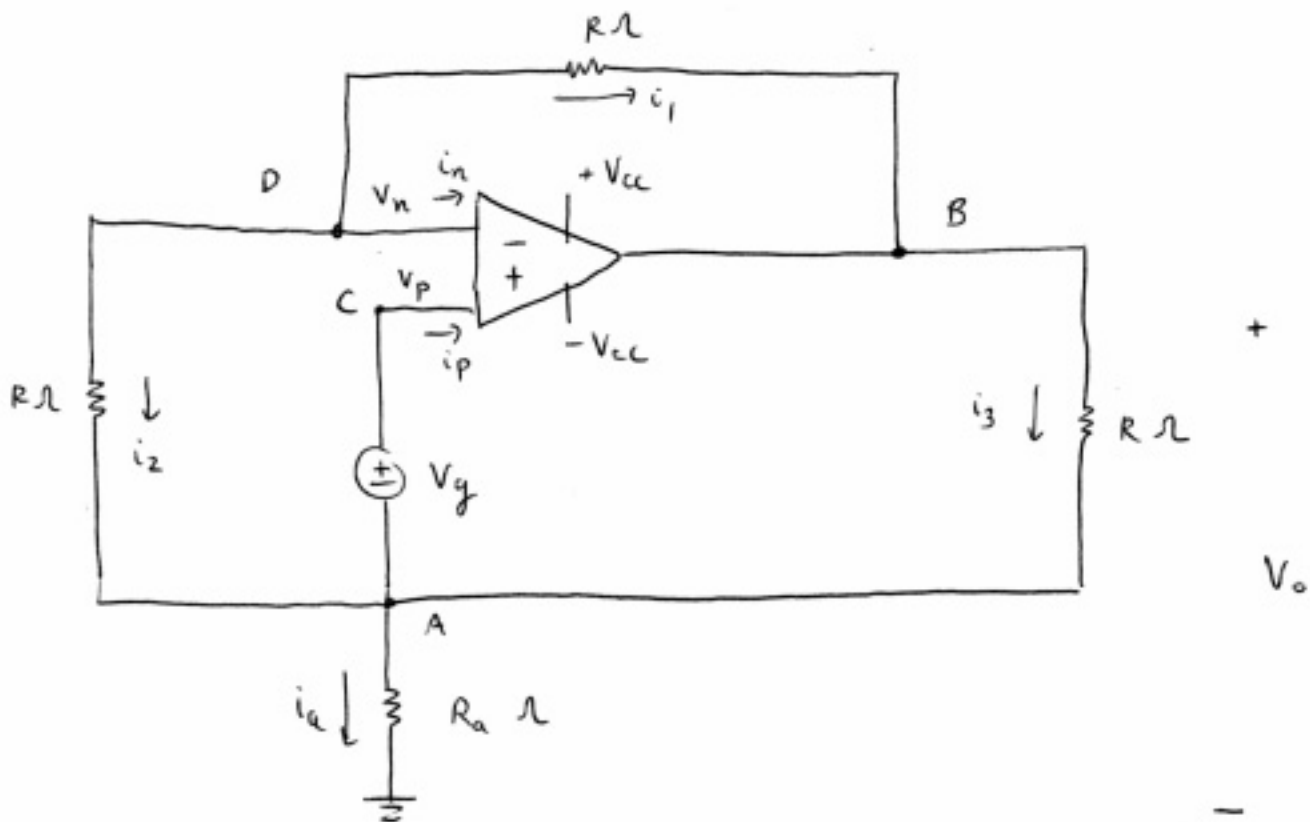5.15 (a) Show that $i_a = \frac{3V_g}{R}$ when op amp operates in linear region. 6



Node-voltage analysis at node D.:

$$i_n = 0$$

$$i_2 + i_1 = 0$$

$$\frac{V_n - V_A}{R} + \frac{V_n - V_B}{R} = 0 \quad \text{eqn (1).}$$

Note:

$$V_c = V_p$$

$$V_c = ?$$

$$V_c - V_A = V_g$$

$$V_c = V_A + V_g = V_p = V_n$$

$$\Rightarrow \text{eqn (1) becomes: } \frac{(V_A + V_g) - V_A}{R} + \frac{(V_A + V_g) - V_B}{R} = 0$$

$$\Rightarrow \frac{V_g}{R} + \frac{V_A - V_B + V_g}{R} = 0$$

$$2V_g = V_B - V_A$$

• Node-voltage analysis at node A:

$$-i_2 - i_3 + i_a = 0$$

$$i_a = i_2 + i_3$$

$$= \frac{V_h - V_A}{R} + \frac{V_B - V_A}{R}$$

$$= \frac{(V_A + V_g) - V_A}{R} + \frac{2V_g}{R}$$

$$i_a = \frac{3V_g}{R} \quad \checkmark$$

(b) Show saturation occurs when

$$R_a = \frac{R(\pm V_{cc} - 2V_g)}{3V_g}$$

Saturation does NOT occur when

$$-V_{cc} \leq V_o \leq V_{cc}$$

$$-V_{cc} \leq i_3 R + i_a R_a \leq V_{cc}$$

$$-V_{cc} - i_3 R \leq i_a R_a \leq V_{cc} - i_3 R$$

$$-V_{cc} - \left(\frac{2V_g}{R}\right)R \leq \left(\frac{3V_g}{R}\right)R_a \leq V_{cc} - \left(\frac{2V_g}{R}\right)R$$

$$\frac{R(-V_{cc} - 2V_g)}{3V_g} \leq R_a \leq \frac{R(V_{cc} - 2V_g)}{3V_g}$$

So, R_a is bounded by $\frac{R(\pm V_{cc} - 2V_g)}{3V_g}$ //

Solution

For an inverting amplifier the magnitude of gain is

$$|G| = (R_f) / (R_s)$$

For the nominal values of the resistors this ratio equals
 $100.0 / 2.4 = 41.67$

The lowest gain is

$$(R_{f, \text{lowest}}) / (R_{s, \text{highest}}) = (100.0 - 10.0) / (2.4 + 0.24) = 90.0 / 2.64 = 34.09$$

The highest gain is

$$(R_{f, \text{highest}}) / (R_{s, \text{lowest}}) = (100.0 + 10.0) / (2.4 - 0.24) = 110.0 / 2.16 = 50.93$$

For a non-inverting amplifier,

$$G = 1 + (R_f) / (R_s)$$

$$\text{Nominal value} = 1 + 100.0 / 2.4 = 1 + 41.67 = 42.67$$

The lowest gain is

$$1 + (R_{f, \text{lowest}}) / (R_{s, \text{highest}}) = 1 + (100.0 - 10.0) / (2.4 + 0.24) = 35.09$$

The highest gain is

$$1 + (R_{f, \text{highest}}) / (R_{s, \text{lowest}}) = 1 + (100.0 + 10.0) / (2.4 - 0.24) = 51.93$$

Comment.

Students familiar with propagation of errors may apply their knowledge and arrive at essentially the same values in a more elegant way.

The maximal amplitude of the output signal, which is not clipped, is 20 V peak-to-peak or 10 V peak. The AC waveform has the amplitude 100 mV peak.

After amplification, the peak value of the AC signal is

$$AC * |G|$$

Even for the maximal gain it equals

$$AC * |G| = 100 \text{ mV} * 50.93 = 5.093 \text{ V.}$$

This signal is not clipped.

The equation for maximal DC offset at which the output signal is not clipped is:

$$(AC + DC_{\max}) \cdot |G| = 10 \text{ V}$$

$$DC_{\max} = \{ 10 \text{ V} / |G| \} - AC$$

Substitution gives:

For nominal gain,
 $DC_{\max} = 140.0 \text{ mV}$

For minimal gain,
 $DC_{\max} = 193.3 \text{ mV}$

For maximal gain,
 $DC_{\max} = 96.3 \text{ mV}$

Since the clipping of waveforms occurs at +10 V and -10 V (same magnitude despite different signs), the largest negative DC offset at which the clipping does not occur equals to $-DC_{\max}$ found above, that is

For nominal gain,
 -140.0 mV

For minimal gain,
 -193.3 mV

For maximal gain,
 -96.3 mV