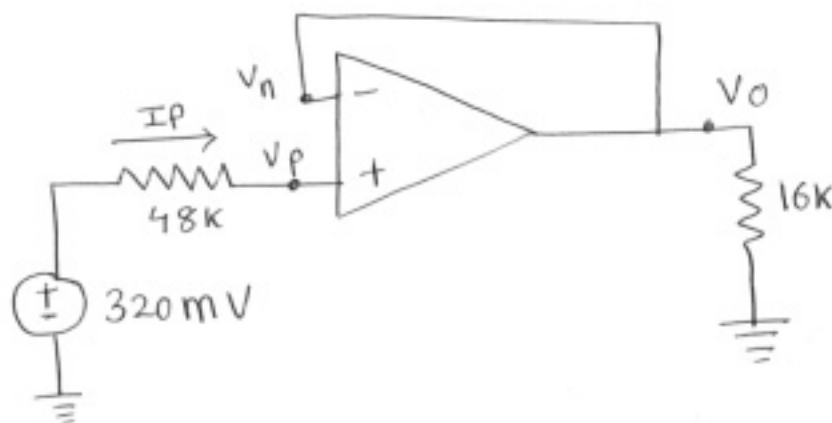


HOMEWORK #7 SOLUTIONS

1

5.20

(a)



By Golden Rules of Op-amps

$$(1) V_n = V_p \quad \& \quad (2) I_n = I_p = 0$$

∴ with reference to the above ckt,

$$I_p = 0 \quad \therefore V_p = 320 \text{ mV}$$

$$\text{But since } V_n = V_p, \quad V_n = 320 \text{ mV}$$

$$\text{But } V_o = V_n \quad (\text{from ckt diagram})$$

$$\therefore V_o = 320 \text{ mV}$$


$V_o \rightarrow$ voltage across the 16k resistor

∴ power delivered to the 16k resistor

$$\begin{aligned} = P_{16k} &= \frac{V_o^2}{R_L} \quad (\text{where } R_L = 16k) \\ &= \frac{(0.32)^2}{16k} \end{aligned}$$

$$\therefore P_{16k} = 6.44 \mu W$$

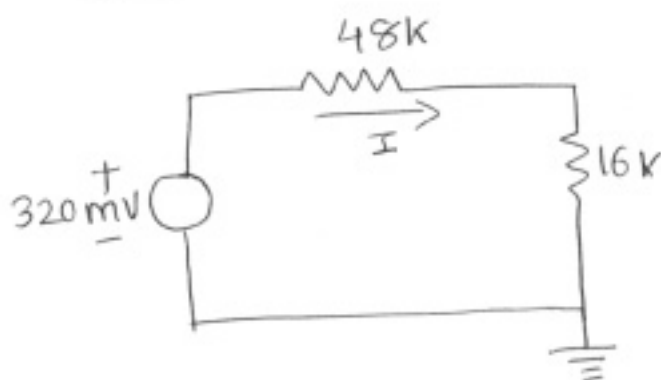- (b) ckt redrawn with op-amp removed from the ckt



In this case,

$$V_{16k} = \left(\frac{16k}{16k + 48k} \right) (0.32) = 0.08 V$$

(Voltage Divider)

$$\therefore P_{16k} = \frac{(0.08)^2}{16k}$$

$$\therefore P_{16k} = 0.4 \mu W$$

$$\begin{aligned} \text{(c) Ratio} &= \frac{(P_{16k})_{(a)}}{(P_{16k})_{(b)}} \\ &= \frac{6.4 \mu W}{0.4 \mu W} \end{aligned}$$



$$\text{Ratio} = 16$$

(d) Yes it does. Some of them are:

- 1) It enables the source to control 16 times as much power delivered to the load resistor — as found in part (c). Thus it aids in Power Amplification
- 2) Irrespective of the source resistance (in this case $48k +$ the internal resistance of $320mV$ source) the o/p voltage is always equal to the input. Thus, it's a VOLTAGE FOLLOWER (o/p voltage = i/p voltage) ckt.
- 3) It serves as a buffer amplifier between the i/p voltage ckt and the o/p ckt to which the voltage is delivered. Thus it prevents the loading of i/p ckt by the o/p ckt.
- 4) It also allows the load resistor voltage (and its current) to be set without drawing any current from i/p. This is called current amplification function of the ckt

2

Problem 5.29

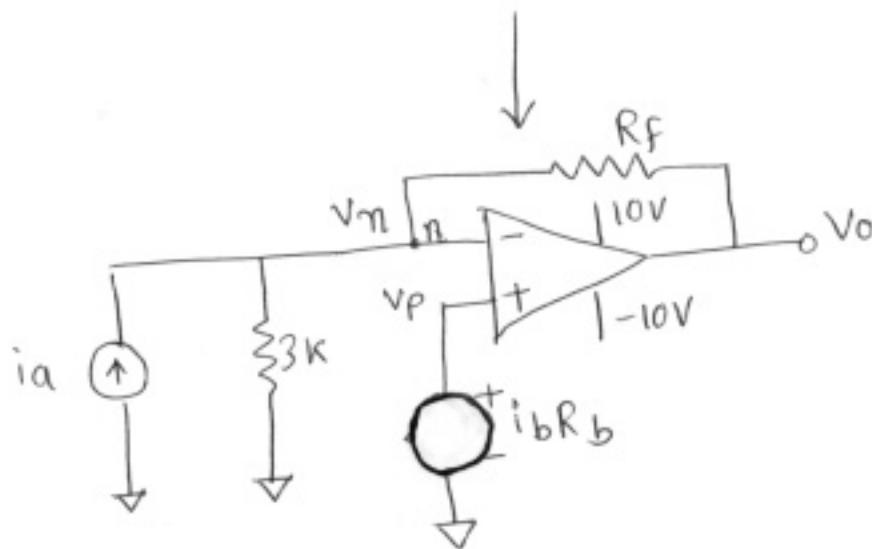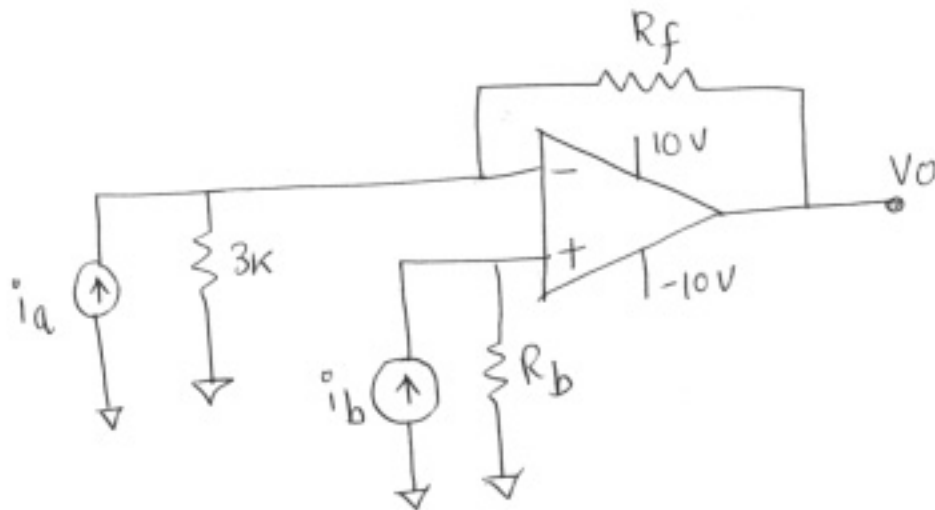

By Golden rules, $v_n = v_p$

$$\therefore v_n = i_b R_b$$

Applying KCL at node n ,

$$-i_a + \frac{v_n - 0}{3k} + \frac{v_n - V_o}{R_f} = 0$$

$$\therefore -i_a + \frac{i_b R_b}{3k} + \frac{i_b R_b - V_o}{R_f} = 0$$

$$\therefore (-i_a)(3k)(R_f) + (i_b R_b) R_f + (i_b R_b) 3k = (V_o) 3k \quad \text{--- (1)}$$

Since, $V_o = 2000 (i_b - i_a)$ (Given)

$$(V_o) 3k = 3k (2000) i_b - 3k (2000) i_a \quad \text{--- (2)}$$

Comparing eqns (1) & (2)


$$R_f = 2000 = 2k\Omega$$

and $(3k)(2000) = R_b R_f + R_b 3k$

$$\therefore R_b = \frac{(3k)(2000)}{5k}$$

$$\therefore R_b = 1200\Omega$$

3 Problem 5.30

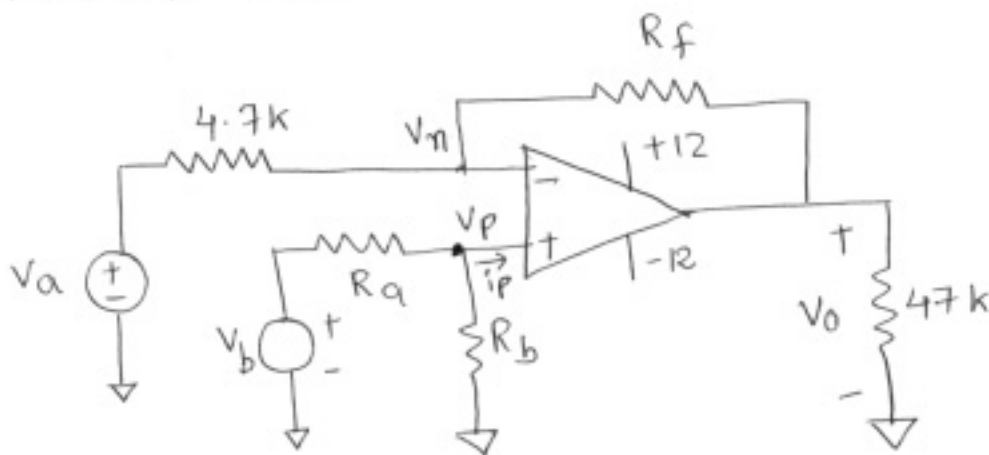

Using ideal model for op-amps,
resistance seen by voltage source V_b
 $= R_a + R_b$

$$\therefore \boxed{R_a + R_b = 220k} \quad (\text{from given})$$

Now by Golden rules,
 $i_p = 0$

$$\therefore V_p = \left(\frac{R_b}{R_a + R_b} \right) V_b \quad (\text{from ckt, using voltage divider})$$

Since $V_n = V_p$ (also by Golden Rules)

$$V_n = \left(\frac{R_b}{R_a + R_b} \right) V_b$$

Applying KCL at node n , using node-voltage method, we get

$$\frac{V_n - V_a}{4.7k} + \frac{V_n - V_o}{R_f} = 0$$

$$\therefore V_n \left(\frac{1}{4.7k} + \frac{1}{R_f} \right) - \frac{V_a}{4.7k} = \frac{V_o}{R_f}$$

$$\therefore V_o = \left(\frac{R_b}{R_a + R_b} \right) \cdot R_f \cdot \left(\frac{R_f + 4.7k}{(4.7k)R_f} \right) \cdot V_b - \frac{V_a}{4.7k} \cdot R_f$$

Now since $v_o = 10v_b - 10v_a$ is given,

$$\therefore \frac{R_f}{4.7k} = 10$$

$$\therefore \boxed{R_f = 47k}$$

$$\text{Also, } \left(\frac{R_b}{R_a + R_b} \right) R_f \left(\frac{R_f + 4.7k}{(4.7k)(R_f)} \right) = 10$$

putting $R_a + R_b = 220k$, and $R_f = 47k$ in there, we get

$$v_o = \left(\frac{R_b}{220k} \right) \cdot 47k \left(\frac{47k + 4.7k}{4.7k(47k)} \right)$$


$$\therefore \boxed{R_b = 200k}$$

$$\text{and } \boxed{R_a = 20k}$$

(Since $R_a + R_b = 220k$)

4

Problem 5.34

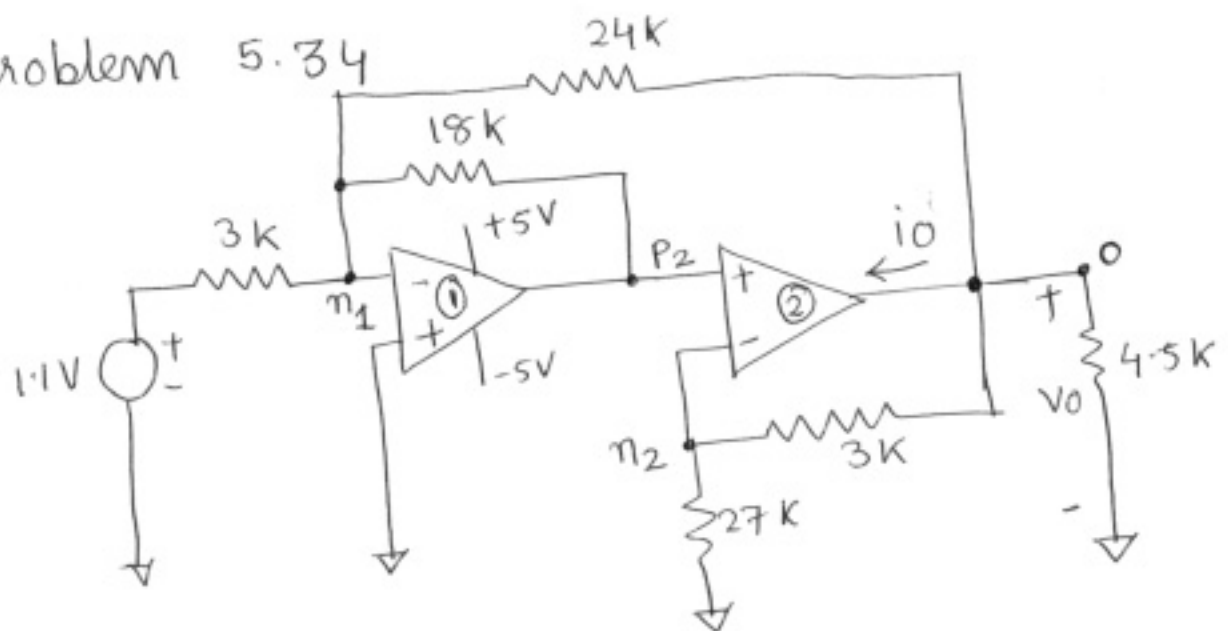

By Golden rules,

$$I_{n1} = I_{p1} = I_{n2} = I_{p2} = 0$$

(where the subscripts 1 & 2 refer to the respective opamps in the ckt)

Applying KCL at node n_2 ,

$$\frac{V_{n2}}{27k} + \frac{V_{n2} - V_0}{3k} = 0 \quad (\text{since } I_{n2} = 0)$$

$$\therefore \boxed{V_{n2} = \frac{9}{10} V_0}$$

Again by Golden rules,

$$V_{p2} = V_{n2} \quad \text{and} \quad V_{p1} = V_{n1}$$

$$\therefore \boxed{V_{p2} = \frac{9}{10} V_0} \quad \text{and} \quad \boxed{V_{n1} = 0} \quad (\text{since } V_{p1} = 0)$$

Now applying KCL at node n_1 ,

$$\frac{0 - 11}{3k} + \frac{0 - V_{p2}}{18k} + \frac{0 - V_0}{24k} = 0$$

$$\therefore -\frac{11}{3} - \left(\frac{9}{10}\right) \frac{V_0}{18} - \frac{V_0}{24} = 0$$

$$\therefore -\frac{11}{3} = V_0 \left(\frac{1}{20} + \frac{1}{24} \right) = \frac{(V_0) 11}{120}$$

$$\therefore V_0 = \left(-\frac{11}{3} \right) \left(\frac{120}{11} \right)$$

$$\therefore \boxed{V_0 = -4V}$$

Now applying KCL at node 0,

$$i_0 + \frac{V_0 - 0}{4.5k} + \frac{V_0 - V_{n1}}{24k} + \frac{V_0 - V_{n2}}{3k} = 0$$


$$\therefore i_0 + \frac{V_0}{4.5k} + \frac{V_0}{24k} + \frac{V_0}{30k} = 0$$

$$(\because V_{n2} = \frac{9}{10} V_0)$$


$$(i_0)(10^3) = +4 \left(\frac{1}{4.5} + \frac{1}{24} + \frac{1}{30} \right)$$

$$\therefore i_0 = 1.188 \text{ mA}$$

5 Problem 5.40

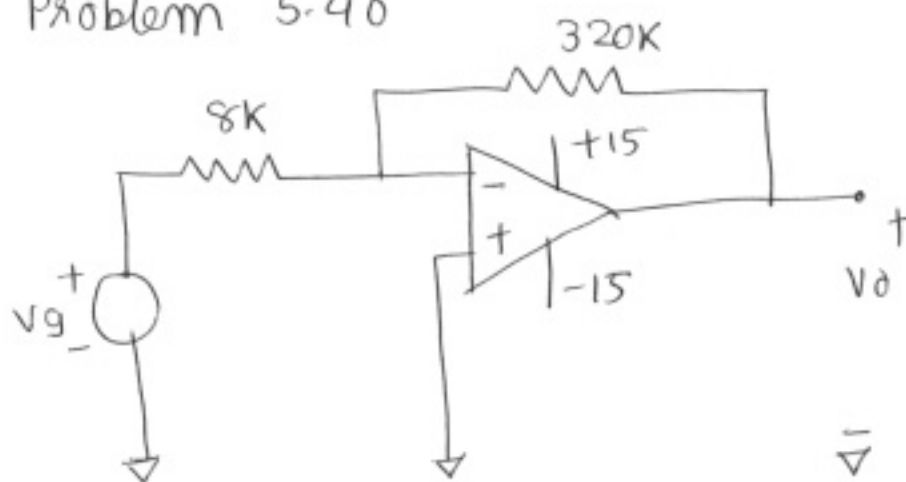

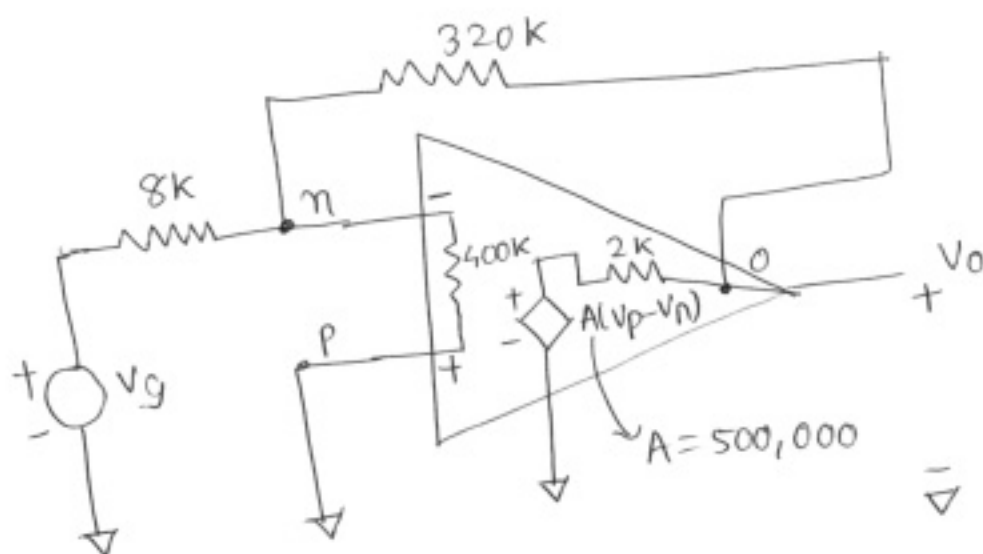We draw a new ckt equivalent to the one given, but one which takes into account the non-idealities of the op-amp



(a) Applying KCL at node n.

$$\frac{V_n - V_g}{8k} + \frac{V_n - V_p}{400k} + \frac{V_n - V_o}{320k} = 0$$

$$V_p = 0$$

$$\therefore V_n \left(\frac{1}{8k} + \frac{1}{400k} + \frac{1}{320k} \right) - \frac{V_o}{320k} = \frac{V_g}{8k}$$

$$\therefore 41.8V_n - V_o = 40V_g \quad - (1)$$

Applying KCL at node o, and putting $V_p = 0$;

$$\frac{V_o - 500,000(-V_n)}{2k} + \frac{V_o - V_n}{320k} = 0$$

$$\therefore 80 \times 10^6 V_n + 161 V_o = 0 \quad - (2)$$

Solving eqns (1) & (2) we get

$$v_o = -39.997 v_g$$

$$\therefore \boxed{\frac{v_o}{v_g} = -39.997}$$

(b) Again, from eqns ① & ② derived in part (a),

$$v_n = 8.05 \times 10^{-5} v_g$$

Since $v_g = 50 \text{ mV}$,

$$\boxed{v_n = 4.02 \mu\text{V}}$$

(c) Resistance seen by source v_g , is the ratio v_g/i_g , where i_g is the current drawn from that source v_g .

Now in our case, it's the current i_g flowing through 8K resistor.

$$\therefore i_g = \frac{v_g - v_n}{8\text{K}}$$

$$= \frac{v_g - 8.05 \times 10^{-5} v_g}{8\text{K}} \quad (\text{from (a) \& (b)})$$

$$R_g = \frac{v_g}{i_g} = \frac{v_g}{\frac{v_g - 8.05 \times 10^{-5} v_g}{8\text{K}}} \quad (8\text{K})$$

$$\boxed{R_g = 8000.644 \Omega}$$

(d) For an ideal inverting amplifier,

$$\text{Gain} = \frac{V_o}{V_g} = -\frac{R_F}{R_{in}}$$

$\therefore$ in this case,

$$\boxed{\text{Gain} = \frac{-320\text{k}}{8\text{k}} = -40}$$

By Golden rules, $V_n = V_p$

Since $V_p = 0$,

$$\boxed{V_n = 0}$$

$$\text{and } i_g = \frac{V_g - V_n}{8\text{k}} = \frac{V_g - 0}{8\text{k}} = \frac{V_g}{8\text{k}}$$

$$\therefore R_g = \frac{V_g}{i_g} = 8\text{k}$$

$$\boxed{R_g = 8\text{k}}$$

Comments:-

Comparing the results from part (d), with results from other parts, we find that they are very close. We conclude from this, that for very high i/p resistance, very low o/p resistance and very high openloop gain, the ideal op-amp model yields very accurate results. Thus we can safely assume our op-amp to be ideal under the above-mentioned conditions, and simplify our analysis, while still getting close to accurate results!

6 Lab-related problem - By A. Gango

(a) $R_L = 8 \Omega$

$V_{CC} = 10V$

for LM380, $\text{max } V_{oppk} = (V_{CC} - 4) = 10 - 4 = 6V$

$\text{max o/p short ckt current for LM380}$
 $= I_{sc}(380) = 1.3A$

$(I_{sc, \text{max}})(R_L) = (1.3)(8) = 10.4V$

Thus if $(V_o)_{ppk}$ exceeds $10.4V$, current clipping will occur.

But voltage clipping will occur when $(V_o)_{ppk}$ exceeds $6/2 = 3V$.

$$10.4 > 3$$

Thus current clipping will not occur.

* $\text{Max } (V_o)_{ppk} = 6/2 = 3V$

$\therefore$ Max power delivered to the load when o/p is not clipped, will be

$$(P_L)_{\text{max}} = \frac{(V_o)_{ppk}^2}{2R_L}$$
$$= \frac{(3)^2}{2(8)}$$

$(P_L)_{\text{max}} = 0.5625W$

 $R_L = 8\Omega, V_{CC} = 10V$

* Now for $V_{CC} = 22V$

$$\text{max } (V_o)_{ppk} = 22 - 4 = 18V$$

$$\therefore \text{max } (V_o)_{pk} = 9V$$

Since $9V < 10.4V$, current clipping will not occur.

* Also $(P_L)_{\text{max}} = (9)^2 / 2(8)$

$(P_L)_{\text{max}} = 5.0625W$

 $R_L = 8\Omega, V_{CC} = 22V$

* When two 8Ω speakers are connected in parallel,

$$R_L = 8 \parallel 8 = 4\Omega$$

for $V_{CC} = 10V$

$$(I_{sc, max}) \cdot R_L = (1.3)4 = 5.2V$$

Since $5.2V > 3V$ current clipping will not occur.

$$\text{and } (P_L)_{max} = \frac{(3)^2}{2(4)} = 1.125W$$

$R_L = 4\Omega, V_{CC} = 10V$

for $V_{CC} = 22V$,

since $5.2V < 9V$,
current clipping WILL occur.
and unlike the $R_L = 8\Omega$ case,

$$(V_{pk})_{max} = 5.2V$$

$$(P_L)_{max} = \frac{(5.2)^2}{2(4)} = 3.38W$$

$R_L = 4\Omega, V_{CC} = 22V$

$\Rightarrow$ The combination of $R_L = 8\Omega$ and $V_{CC} = 22V$, gives the max power to load, which is $5.0625W$

$\Rightarrow$ Since max power delivered = 5.0625 W and package dissipation limit (from specs) is 8.3 W , the power limits are not exceeded.

$\Rightarrow$ When $V_{CC} = 10 \text{ V}$, connecting two speakers, gives more power (1.125 W against 0.5625 W), but when $V_{CC} = 22 \text{ V}$, the power decreases with two speakers (3.38 W against 5.0625 W) because of current clipping.

(b)

for LM741

$$(I_{sc})_{\max} = 25 \text{ mA}$$

$$R_L = 8 \Omega$$

$$\therefore (I_{sc})_{\max} \cdot R_L = (25 \text{ mA})(8 \Omega) = 200 \text{ mV} = 0.2 \text{ V}$$

$$\text{Now } |V_{cd}| = 12 \text{ V} \therefore |V_{CC} - 2| = 10 \text{ V}.$$

Since $0.2 < 10 \text{ V}$, current clipping will occur. and

$$(V_{opk})_{\max} = 0.2 \text{ V}$$

New max power delivered to o/p

$$(P_L)_{\max} = \frac{(V_{opk})_{\max}^2}{2R_L}.$$

$$\therefore (P_L)_{\max} = \frac{(0.2)^2}{2(8)} = 0.0025 \text{ W}$$

$$(P_L)_{\max} = 2.5 \text{ mW}$$

$$V_{CC} = 12 \text{ V}, R_L = 8 \Omega$$

Compared to LM380, the power delivered to o/p is very small. Thus LM741 is not useful for audio power amplification purposes, as against LM380 //