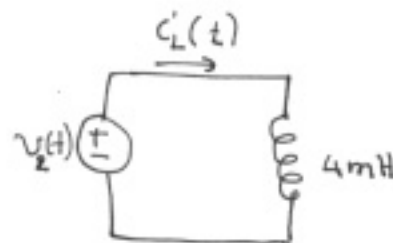


Homework # 82. Problem 6.2

$$L = 4 \text{ mH}$$

$$i = 2.5 \text{ A} \quad t \leq 0$$



$$v_L(t) = 30e^{-3t} \text{ mV}, \quad 0^+ \leq t < \infty$$



$$i_L = \frac{1}{L} \int_{t_0}^t v dt + i(t_0) \Rightarrow i_L(t) = \frac{1}{4 \times 10^{-3}} \int_0^t 30e^{-3t} \times 10^{-3} dt + 2.5$$

$$\Rightarrow i_L(t) = 7.5 \left(\frac{1}{-3} e^{-3t} \right) \Big|_0^t + 2.5 = 2.5 + 2.5(1 - e^{-3t})$$
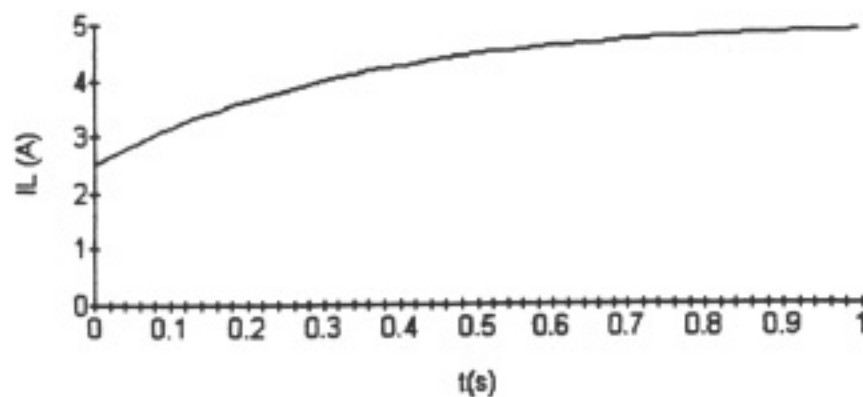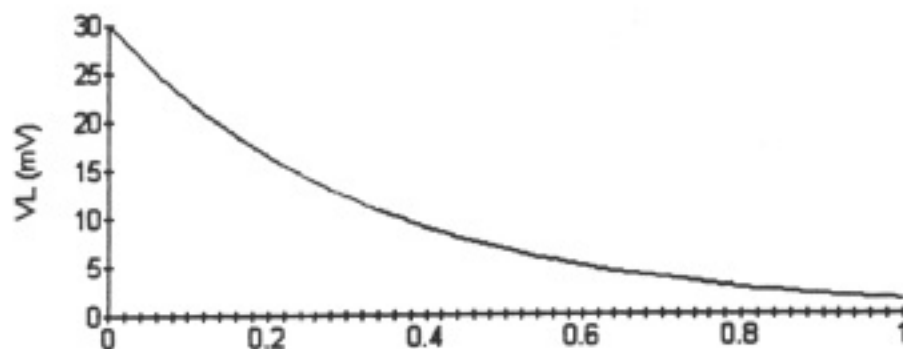
$$= \underline{\underline{5 - 2.5 \times e^{-3t} \text{ A}, \quad 0 < t < \infty}}$$



3. Problem 6.9

$$L = 25 \text{ mH}$$

$$i_L = -10 \text{ A}, \quad t \leq 0$$

$$i_L = -[10 \cos 400t + 5 \sin 400t] e^{-200t} \text{ A}, \quad t \geq 0$$

(a) At what instant of time is the voltage across the inductor maximum?

$$u_L = L \frac{di_L}{dt}$$

$$\begin{aligned} \frac{di_L}{dt} &= -\frac{d}{dt} [10 \cos 400t e^{-200t} + 5 \sin 400t e^{-200t}] \\ &= 10 \times 400 \times \sin 400t e^{-200t} - 10 \cos 400t \times (-200) e^{-200t} \\ &\quad - 5 \times 400 \cos 400t e^{-200t} + 5 \times 200 \sin 400t e^{-200t} \\ &= 5000 \sin 400t e^{-200t} \end{aligned}$$


$$\begin{aligned} u_L &= L \frac{di_L}{dt} = 25 \times 10^{-3} \times 5000 \sin 400t e^{-200t} \\ &= 125 \sin 400t e^{-200t} \text{ V} \end{aligned}$$

$$\begin{aligned} \frac{du_L}{dt} &= 125 \times 400 \cos 400t e^{-200t} - 125 \times \sin 400t e^{-200t} \times 200 = 0 \\ &\Rightarrow 2 \cos 400t - \sin 400t = 0 \Rightarrow \sin 400t = 2 \cos 400t \\ &\Rightarrow \tan 400t = 2 \quad (\text{when } \sin 400t \neq 0) \\ &\Rightarrow 400t = \arctan(2) \Rightarrow t = \frac{1}{400} \arctan 2 = \frac{1.107}{400} \text{ sec} \\ &\quad n=0, 1, \dots \end{aligned}$$

Notice that at $t=0$, $\frac{du_L}{dt} > 0 \Rightarrow$ curve has positive slope until it reaches a maximum at $t=0.0028 \text{ sec}$

$$(b) u_L(0.0028) = 125 \sin(400 \times \frac{1.107}{400}) e^{-200 \times 0.0028} = \underline{\underline{64.27 \text{ V}}}$$

Plot of $V(t)$, Problem 6.9

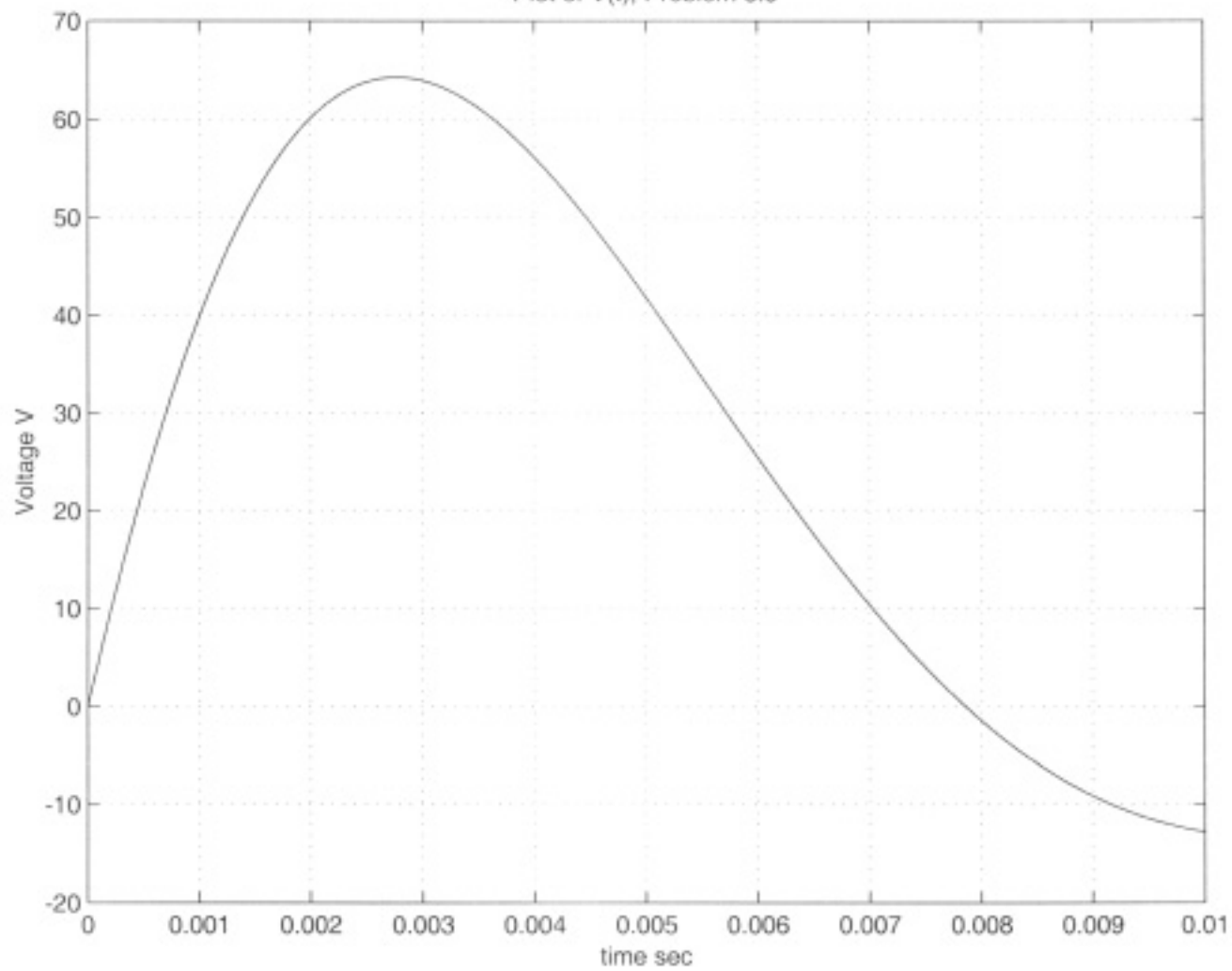

4. Problem 6.14

$$C = 0.5 \mu F \Rightarrow \frac{1}{C} = 2 \times 10^6$$

$$V = 20V \text{ at } t = 0$$

$$(a) \quad 0 \leq t \leq 50 \mu s$$

$$v(t) = \frac{1}{C} \int_0^t 20 \times 10^{-3} dt + v(0) = 2 \times 10^6 \int_0^t 20 \times 10^{-3} dt + 20$$

$$= \underline{40 \times 10^3 t + 20 V} \quad \Rightarrow \quad v(50) = 40 \times 10^3 \times 50 \times 10^{-6} + 20 = 22V$$

$$(b) \quad 50 \mu s \leq t \leq 200 \mu s$$

$$v(t) = \frac{1}{C} \int_{50 \times 10^{-6}}^t (-40 \times 10^{-3} dt) + v(50) = 2 \times 10^6 \int_{50 \times 10^{-6}}^t (-40 \times 10^{-3} dt) + 22$$

$$= -2 \times 10^6 \times 40 \times 10^{-3} (t - 50 \times 10^{-6}) + 22$$


$$= -8 \times 10^4 t + 4 + 22 = \underline{26 - 8 \times 10^4 t}$$

$$v(200) = 26 - 8 \times 10^4 \times 200 \times 10^{-6} = 26 - 16 = 10V$$

$$(c) \quad 200 \mu s \leq t < \infty$$

$$v(t) = \frac{1}{C} \int_{200 \mu sec}^t (0) dt + v(200) = \underline{10V}$$

(d)

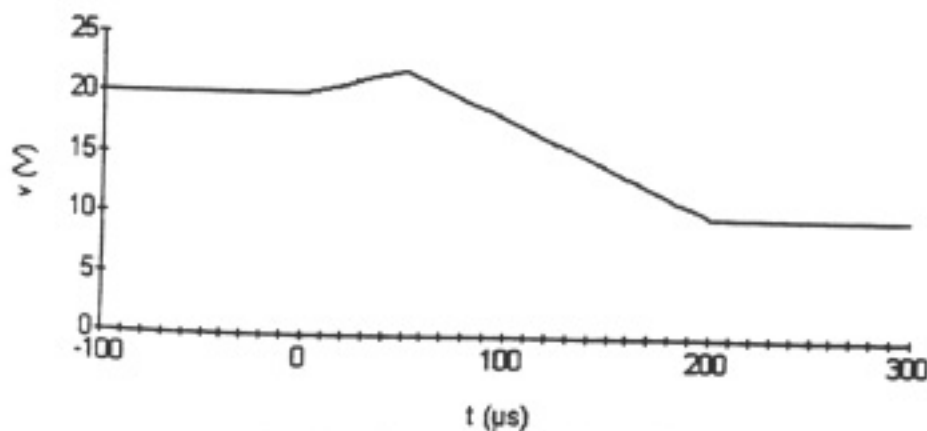

s. Problem 6.15

$$C = 0.8 \mu F$$


$$v_c(t) = \begin{cases} 20t^3 \text{ V} & 0 \leq t \leq 1 \text{ sec} \\ 2.5(3-t)^3 \text{ V} & 1 \leq t \leq 3 \text{ sec} \\ 0 & \text{elsewhere} \end{cases}$$

$$i_c = C \frac{dv}{dt}$$


$$\text{for } 0 \leq t \leq 1 \quad i_c = 0.8 \times 10^{-6} \frac{d}{dt} (20t^3) = 0.8 \times 10^{-6} \times 20 \times 3 t^2 \\ = \underline{48 t^2 \mu A}$$

$$\text{for } 1 \leq t \leq 3 \quad i_c = 0.8 \times 10^{-6} \frac{d}{dt} (2.5(3-t)^3)$$
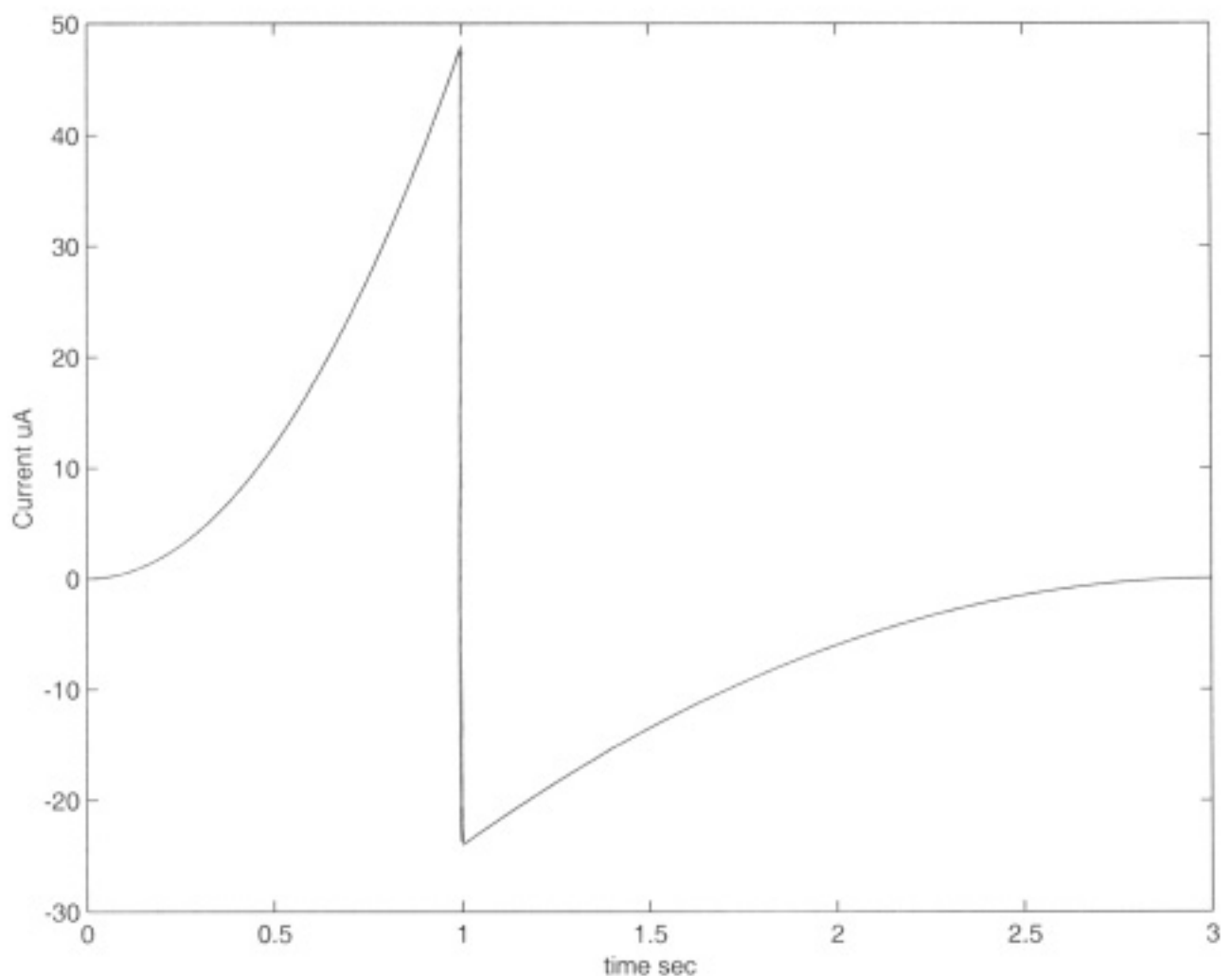
$$\Rightarrow i_c = 2 \times 10^{-6} \times 3 \times (-1) \times (3-t)^2 = -6 \times 10^{-6} (3-t)^2 \\ = -6 (3-t)^2 \mu A$$



6. Problem 6.19

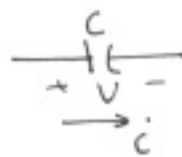

$$v = \begin{cases} -60 \text{ V} & t \leq 0 \\ 15 - 15 e^{-500t} (5 \cos 2000t + \sin 2000t) \text{ V} & t \geq 0 \end{cases}$$

$$C = 0.4 \mu\text{F}$$

(a) $i = 0$, $t \leq 0$ (capacitor acts as open circuit for DC)
 $i = C \frac{dv}{dt} = 0$, $t \leq 0$

$$\begin{aligned} \text{(b)} \quad \frac{dv}{dt} &= -15 [(5 \cos 2000t + \sin 2000t)(-500)e^{-500t} + \\ &\quad e^{-500t} (-10000 \sin 2000t + 2000 \cos 2000t)] \\ &= 15 e^{-500t} [500 \cos 2000t + 10500 \sin 2000t] \end{aligned}$$

$$\begin{aligned} i &= C \frac{dv}{dt} = 0.4 \times 10^{-6} \times 15 \times 500 \times e^{-500t} [\cos 2000t + 21 \sin 2000t] \\ &= 3 \times 10^{-3} (\cos 2000t + 21 \sin 2000t) \\ &= \underline{3 (\cos 2000t + 21 \sin 2000t) \text{ mA}} \end{aligned}$$

(c) No; The voltage cannot change instantaneously across the terminals of a capacitor. Also observe from $v(t)$ specified in this problem that $v(0^-) = -60 \text{ V}$ and $v(0^+) = -60 \text{ V}$.

(d) From (b), find i for $t = 0^+$:


$$i = 3(1 + 0) = 3 \text{ mA}$$

$\Rightarrow$ Instantaneous change from 0

$$\text{(e)} \quad v(\infty) = 15 - 15 e^{-\infty} = 15 - 0 = 15 \text{ V}$$


$$W = \frac{1}{2} C v^2 = \frac{1}{2} \times 0.4 \times 10^{-6} \times (15^2) = \underline{45 \mu\text{J}}$$

7. Problem 6.20

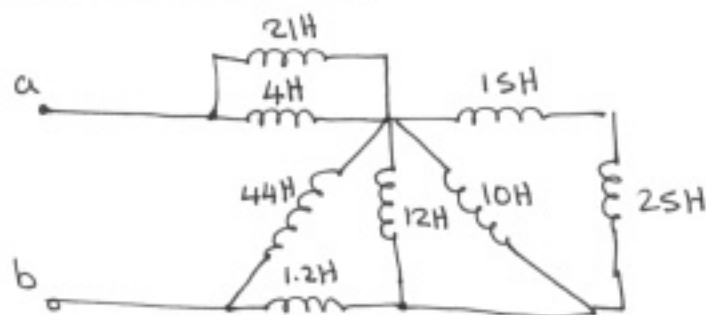


15H and 25H in series : $15 + 25 = 40H$

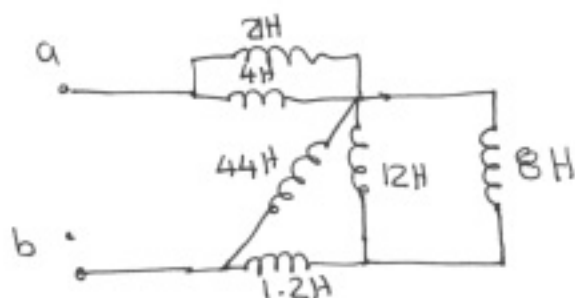40H in parallel with 10H : $40 // 10 = 8H$




8H in parallel with 12H : $8 // 12 = 4.8H$

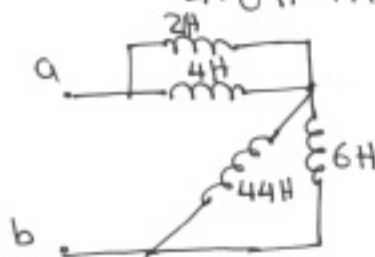4.8H in series with 1.2H : $4.8 + 1.2 = 6H$




6H in parallel with 44H $\Rightarrow 6 // 44 = 5.28H$

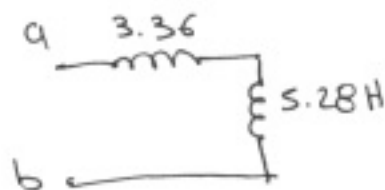2H in parallel with 4H : $2 // 4 = 3.36H$




in series
 $3.36 + 5.28$
 $= 8.64H$

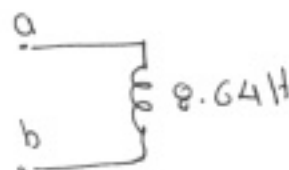


$$\Rightarrow \underline{\underline{L_{eq} = 8.64H}}$$

8. Problem 6.24

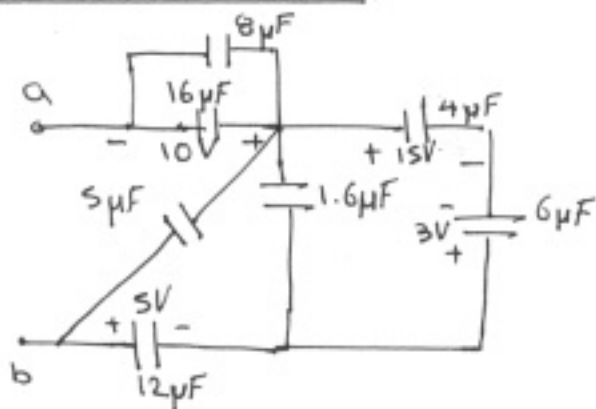

$$4 \text{ series } 6: \frac{1}{4} + \frac{1}{6} = \frac{1}{C} \Rightarrow C = 2.4 \mu F$$

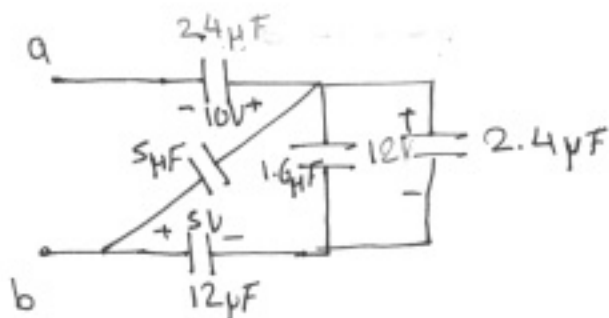
$$16 \text{ parallel } 8: 16 + 8 = 24 \mu F$$



$$2.4 \text{ parallel } 1.6: 2.4 + 1.6 = 4 \mu F$$


$$4 \mu F \text{ in series } 12 \mu F: \frac{1}{4} + \frac{1}{12} = \frac{1}{C}$$

$$\Rightarrow C = 3 \mu F$$

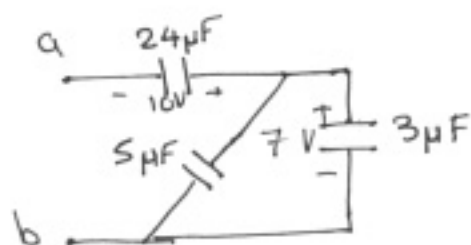


$$3 \mu F \text{ parallel } 5 \mu F: 3 + 5 = 8 \mu F$$
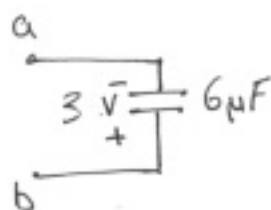
$$8 \mu F \text{ series } 24 \mu F: \frac{1}{C} = \frac{1}{8} + \frac{1}{24} \Rightarrow C = 6 \mu F$$



$$\Rightarrow \underline{\underline{C_{eq} = 6 \mu F}}$$

9. Problem 6.26

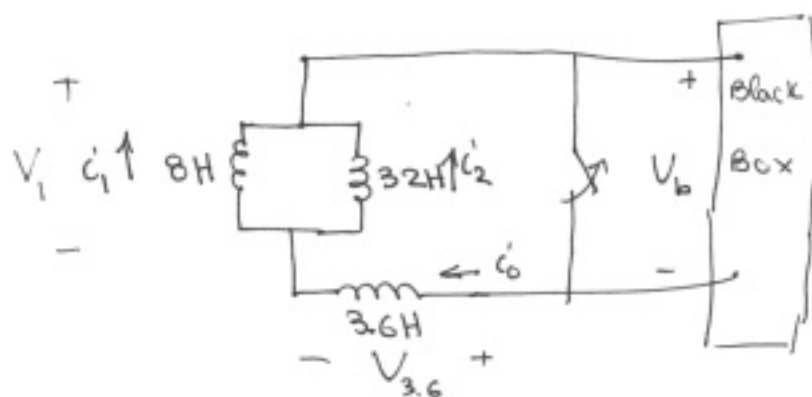


$$V_b = 1250e^{-2st} \text{ V}, \quad t \geq 0$$

$$i_1(0) = 10 \text{ A}$$

$$i_2(0) = -5 \text{ A}$$

(a) $i_0(0) = i_1(0) + i_2(0) = 10 - 5 = 5 \text{ A}$

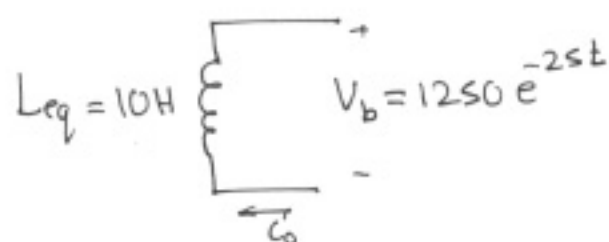(b) $L_{eq} = 3.6 \text{ H} + (8 \text{ H} // 32 \text{ H}) = 3.6 \text{ H} + 6.4 \text{ H} = 10 \text{ H}$



$$\Rightarrow i_0 = -\frac{1}{10} \int_0^t 1250e^{-2st} dt + 5 = 5 + \frac{(-125)}{(-2s)} e^{-2st} \Big|_0^t$$

$$= 5 + 5(e^{-2st} - 1) = \underline{\underline{5e^{-2st} \text{ A}, \quad t \geq 0}}$$

(c) $V_{3.6} = 3.6 \frac{d}{dt} (i_0(t)) = 3.6 \times 5 \times (-2s) e^{-2st} = \underline{\underline{-450e^{-2st} \text{ V}}}$

$$\Rightarrow V_i(t) = V_{3.6}(t) + V_b(t) = -450e^{-2st} + 1250e^{-2st}$$

$$= \underline{\underline{800e^{-2st} \text{ V}}}$$

$$i_1(t) = -\frac{1}{8} \int_0^t 800e^{-2st} dt + i_1(0)$$

$$= -\frac{1}{8} \cdot 800(-2s)(e^{-2st} - 1) + 10 = \underline{\underline{4e^{-2st} + 6 \text{ A}, \quad t \geq 0}}$$

$$(d) \quad i_2(t) = i_0(t) - i_1(t) \\ = 5e^{-25t} - 4e^{-25t} - 6 = \underline{\underline{e^{-25t} - 6 \text{ A}}}$$

$$(e) \quad W(0) = \frac{1}{2} L_1 (i_1(0))^2 + \frac{1}{2} L_2 (i_2(0))^2 + \frac{1}{2} L_0 (i_0(0))^2 \\ = \frac{1}{2} 8 (10)^2 + \frac{1}{2} (32) (5)^2 + \frac{1}{2} (3.6) (5)^2 = \underline{\underline{845 \text{ J}}}$$

$$(f) \quad i_0(\infty) = 0, \quad i_1(\infty) = 6 \text{ A}, \quad i_2(\infty) = -6 \text{ A} \\ \Rightarrow W_{\text{Final}} = \frac{1}{2} L_1 (i_1(\infty))^2 + \frac{1}{2} L_2 (i_2(\infty))^2 = \frac{1}{2} 8 (6)^2 + \frac{1}{2} (32) (6)^2 = 720 \text{ J}$$

$$W_{\text{del}} = W(0) - W(\infty) = 845 - 720 = \underline{\underline{125 \text{ J}}}$$

or (equivalent):

$$W_{\text{del}} = \int_0^{\infty} i_0(t) v_0(t) dt = \int_0^{\infty} 5e^{-25t} \cdot 1250e^{-25t} dt \\ = 5 \times 1250 \int_0^{\infty} e^{-50t} dt = -\frac{5 \times 1250}{50} e^{-50t} \Big|_0^{\infty} \\ = -125 (e^{-\infty} - e^0) = -125 (0 - 1) = \underline{\underline{125 \text{ J}}}$$

$$(g) \quad W_{\text{trapped}} = W_{\text{Final}} \quad \text{that was calculated in part (f)}$$

$$\Rightarrow W_{\text{trapped}} = \underline{\underline{720 \text{ J}}}$$