

EECS 210


Homework #9 Solutions

① d) $z_1 = 1 + 2j$

Modulus = $\sqrt{1^2 + 2^2} = \sqrt{5} = 2.236$

Phase = $\tan^{-1}\left(\frac{2}{1}\right) = 63.43^\circ$

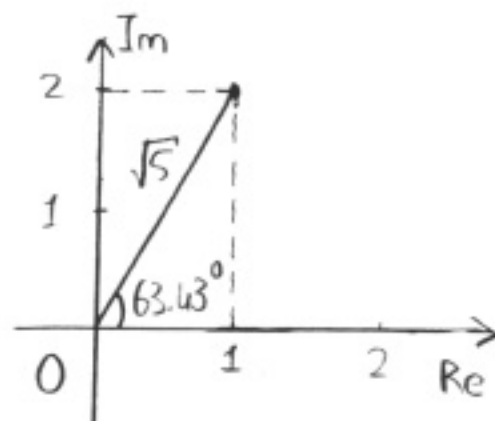$\Rightarrow z_1 = \sqrt{5} \angle 63.43^\circ$




b) $z_2 = 2 + 3j$

Modulus = $\sqrt{2^2 + 3^2} = \sqrt{13} = 3.605$

Phase = $\tan^{-1}\left(\frac{3}{2}\right) = 56.3^\circ$

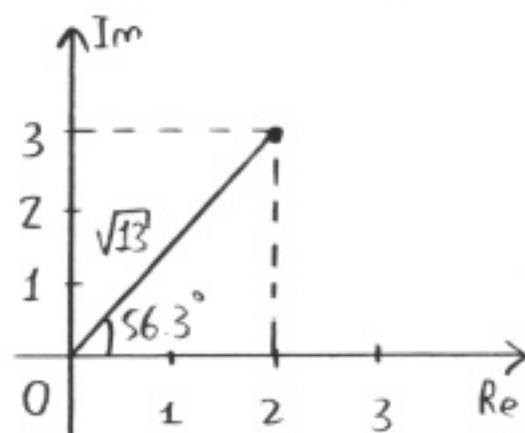$\Rightarrow z_2 = \sqrt{13} \angle 56.3^\circ$




c) $z_3 = 1 - j$

Modulus = $\sqrt{1^2 + 1^2} = \sqrt{2} = 1.414$

Phase = $\tan^{-1}\left(-\frac{1}{1}\right) = -45^\circ$

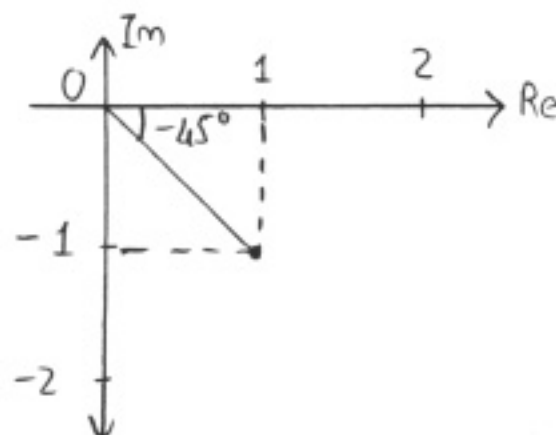$\Rightarrow z_3 = \sqrt{2} \angle -45^\circ$



①

$$\begin{aligned}
 \textcircled{2} \text{ a) } z_1 \cdot z_2 \cdot z_3 &= (z_1 \cdot z_2) \cdot z_3 = [(1+2j)(2+3j)](1-j) \\
 &= (2+3j+4j-6)(1-j) = (-4+7j)(1-j) \\
 &= -4+4j+7j+7 = 3+11j = \sqrt{130} \angle 74.74^\circ = 11.4 \angle 74.74^\circ //
 \end{aligned}$$

$$\begin{aligned}
 \text{b) } z_1 \cdot z_2 \cdot z_3 &= (\sqrt{5} \angle 63.43^\circ)(\sqrt{13} \angle 56.3^\circ)(\sqrt{2} \angle -45^\circ) \\
 &= \sqrt{5 \cdot 13 \cdot 2} \angle 63.43^\circ + 56.3^\circ - 45^\circ = \sqrt{130} \angle 74.74^\circ \\
 &= 11.4 \angle 74.74^\circ //
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{3} \text{ a) } \frac{z_1}{z_2} &= \frac{1+2j}{2+3j} = \frac{\sqrt{5} \angle 63.43^\circ}{\sqrt{13} \angle 56.3^\circ} = \left(\frac{\sqrt{5}}{\sqrt{13}} \right) \angle 63.43^\circ - 56.3^\circ \\
 &= 0.62 \angle 7.13^\circ = 0.615 + j0.0769
 \end{aligned}$$

$$\begin{aligned}
 \text{b) } \frac{z_1}{z_2} &= \frac{1+2j}{2+3j} = \frac{(1+2j)(2-3j)}{(2+3j)(2-3j)} = \frac{2-3j+4j+6}{13} \\
 &= \frac{8+j}{13} = 0.615 + j0.0769 = 0.62 \angle 7.13^\circ
 \end{aligned}$$


(4) a) $\frac{Z_1}{Z_2} = 0.62 \angle 7.13^\circ \Rightarrow \text{Modulus} = 0.62$ (from (3) part b)

b) $\left| \frac{Z_1}{Z_2} \right| = \frac{|Z_1|}{|Z_2|} = \frac{\sqrt{5}}{\sqrt{13}} = 0.62$

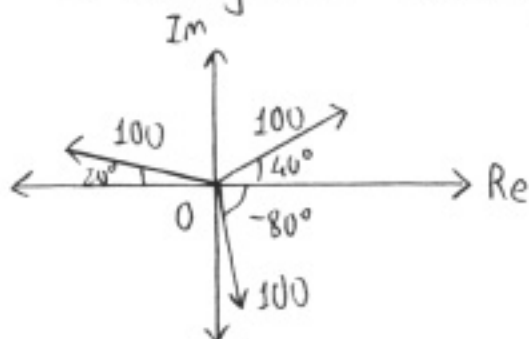
(5) Problem 9.6 (d): $y = 100 \cos(\omega t + 40^\circ) + 100 \cos(\omega t + 160^\circ) + 100 \cos(\omega t - 80^\circ)$

$\Rightarrow Y = 100 \angle 40^\circ + 100 \angle 160^\circ + 100 \angle -80^\circ$

$= 76.6 + j64.27 - 93.96 + j34.2 + 17.36 - j98.4 = 0 \Rightarrow y = 0$



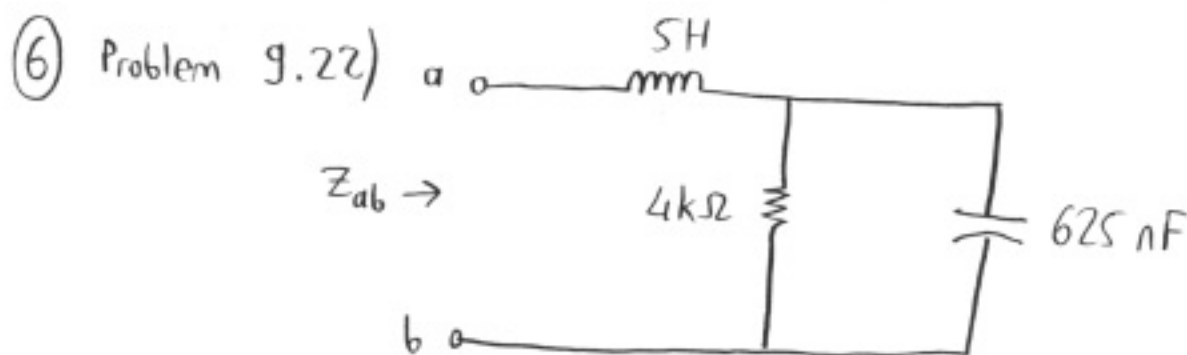The three phasors exactly cancel, because they have the same magnitude and they are 120° apart.




a) $Z_{ab} = j5\omega + \frac{4 \cdot 10^3 \cdot \frac{1}{j\omega 625 \cdot 10^{-9}}}{4 \cdot 10^3 + \frac{1}{j\omega 625 \cdot 10^{-9}}} = j5\omega + \frac{4 \cdot 10^3 (1 - j\omega 2500 \cdot 10^{-6})}{1 + (2500 \cdot 10^{-6} \omega)^2}$

$$\Rightarrow Z_{ab} = j5\omega + \frac{4 \cdot 10^3 - j10\omega}{1 + 6.25 \times 10^{-6} \omega^2} = \frac{4 \cdot 10^3}{1 + 6.25 \times 10^{-6} \omega^2} + j \left(5\omega - \frac{10\omega}{1 + 6.25 \times 10^{-6} \omega^2} \right)$$

Purely resistive $\Rightarrow \text{Im}(Z_{ab}) = 0$

$$\Rightarrow 5\cancel{\omega} = \frac{10\cancel{\omega}}{1 + 6.25 \times 10^{-6} \omega^2} \Rightarrow \boxed{\omega = 400 \text{ rad/sec}}$$

$$b) Z_{ab}(\omega = 400) = \text{Re}(Z_{ab}) = \left. \frac{4 \cdot 10^3}{1 + 6.25 \times 10^{-6} \omega^2} \right|_{\omega = 400} = \frac{4000}{2} = 2 \text{ k}\Omega$$

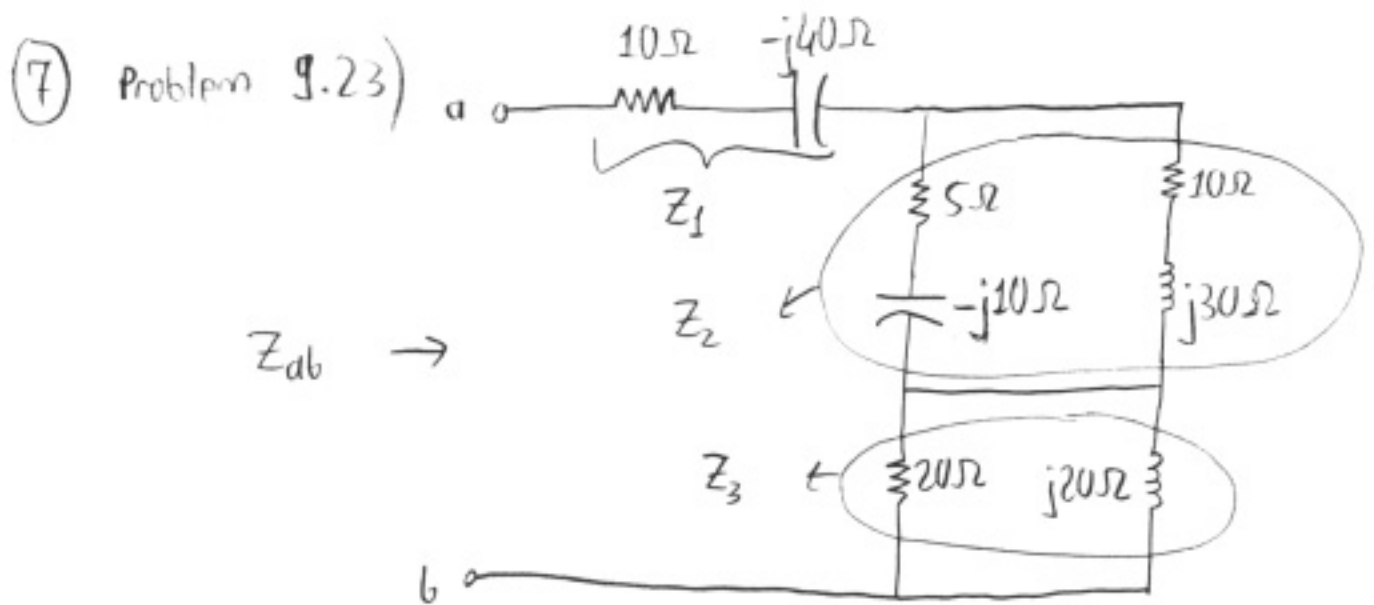

$$Z_1 = 10 - j40\Omega$$

$$Z_2 = \frac{(5 - j10)(10 + j30)}{15 + j20} = \frac{50 + j150 - j100 + 300}{15 + j20}$$

$$= \frac{350 + j50}{15 + j20} = \frac{70 + j10}{3 + j4} = \frac{(70 + j10)(3 - j4)}{3^2 + 4^2}$$

$$= \frac{210 - j280 + j30 + 40}{25} = \frac{250 - j250}{25} = 10 - j10\Omega$$

$$Z_3 = \frac{20 \cdot (j20)}{20 + j20} = \frac{20j}{1 + j} = \frac{20j(1 - j)}{1 + 1} = \frac{20j + 20}{2} = 10 + j10\Omega$$

⑤

$$Z_{ab} = Z_1 + Z_2 + Z_3 = 10 - j40 + 10 - j10 + 10 + j10 = 30 - j40 \Omega$$

$$= 50 \angle -53.15^\circ //$$

(8) Problem 9.29) $V_g = 150 \cos(8000\pi t + 20^\circ) \text{ V}$
 $i_g = 30 \sin(8000\pi t + 38^\circ) \text{ A}$
 $= 30 \cos(8000\pi t - 52^\circ) \text{ A}$

a) $Z = \frac{V_g}{I_g} = \frac{150 \angle 20^\circ}{30 \angle -52^\circ} = 5 \angle 20^\circ + 52^\circ = 5 \angle 72^\circ$
 $= 1.545 + j 4.75 \Omega$



b) $V_g = 150 \cos(8000\pi t + 20^\circ) \text{ V} = 150 \cos(8000\pi(t - t_{vg})) \text{ V}$
 $i_g = 30 \cos(8000\pi t - 52^\circ) \text{ A} = 30 \cos(8000\pi(t - t_{ig})) \text{ A}$

where $-8000\pi(t_{vg}) = 20^\circ \cdot \left(\frac{2\pi}{360^\circ}\right) \text{ radians} \Rightarrow t_{vg} = -13.88 \mu\text{sec}$
 $-8000\pi(t_{ig}) = 52^\circ \cdot \left(\frac{2\pi}{360^\circ}\right) \text{ radians} \Rightarrow t_{ig} = 36.11 \mu\text{sec}$

$\Rightarrow \Delta t = t_{ig} - t_{vg} = 50 \mu\text{sec}$ (i_g lags V_g by $50 \mu\text{sec}$)

(6)

g) Problem 9.25)

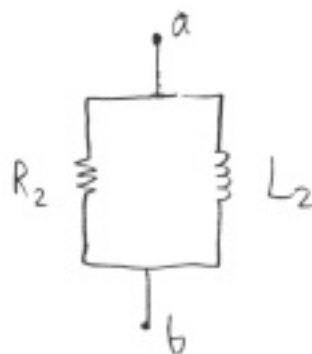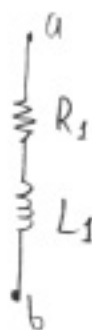

$$Z_1 = R_1 + j\omega L_1$$

$$Z_2 = \frac{R_2 (j\omega L_2)}{R_2 + j\omega L_2} = \frac{j\omega R_2 L_2 (R_2 - j\omega L_2)}{R_2^2 + (\omega L_2)^2}$$

$$= \frac{\omega^2 L_2^2 R_2 + j\omega L_2 R_2^2}{R_2^2 + \omega^2 L_2^2}$$

$$Z_1 = Z_2 \Rightarrow R_1 = \frac{\omega^2 L_2^2 R_2}{R_2^2 + \omega^2 L_2^2}$$

$$L_1 = \frac{R_2^2 L_2}{R_2^2 + \omega^2 L_2^2}$$

b) $R_2 = 50 \text{ k}\Omega$ $L_2 = 2.5 \text{ H}$ $\omega = 20 \text{ krad/sec}$


$$\begin{aligned} \Rightarrow R_1 &= \frac{(2 \cdot 10^4)^2 (2.5)^2 5 \cdot 10^4}{(5 \cdot 10^4)^2 + (2 \cdot 10^4)^2 (2.5)^2} = \frac{4 \cdot 6.25 \cdot 5 \cdot 10^4}{(5 \cdot 10^4)^2 + (2 \cdot 10^4)^2 (2.5)^2} \\ &= \frac{125 \cdot 10^4}{25 + 25} = 25 \text{ k}\Omega \end{aligned}$$

(7)

$$L_1 = \frac{(5 \cdot 10^4)^2 \cdot 2.5}{(5 \cdot 10^4)^2 + (2 \cdot 10^4)^2 (2.5)^2} = \frac{25 \cdot 2.5 \cdot 10^5}{25 \cdot 10^8 + 4 \cdot 6.25 \cdot 10^8}$$

$$= \frac{62.5}{50} = 1.25 \text{ H} //$$

(10) Problem 9.14)

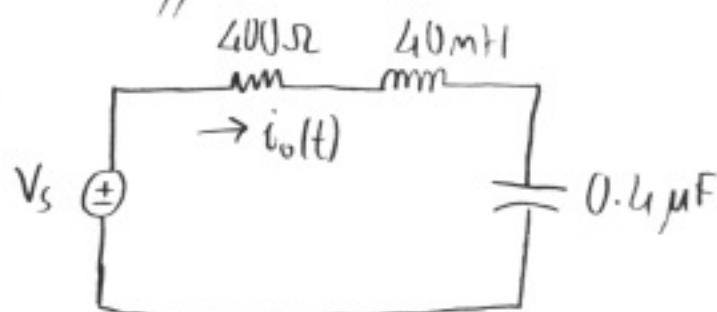

$$V_s = 750 \cos 5000t \text{ mV}$$

Equivalent resistance of R, L, C:


$$Z = 400 + j(5 \cdot 10^3)(4 \cdot 10^{-2}) + \frac{1}{j(5 \cdot 10^3)(0.4 \cdot 10^{-6})}$$

$$= 400 + j200 - j\frac{1000}{2} = 400 - j300 = 500 \angle -36.86^\circ \Omega$$

$$I_o = \frac{V_s}{Z} = \frac{0.75 \angle 0^\circ}{500 \angle -36.86^\circ} = 1.5 \angle 36.86^\circ \text{ mA}$$

$$\Rightarrow i_o(t) = 1.5 \cos(5000t + 36.86^\circ) \text{ mA}$$

① Problem 9.21)

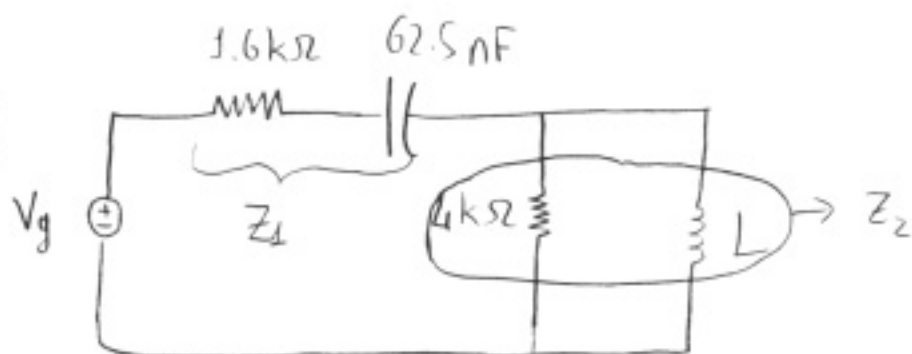

$$V_g = 96 \cos 10000t \text{ V}$$

$$a) Z_1 = 1600 + \frac{1}{j(10^4)(62.5 \cdot 10^{-9})} = 1600 - j1600 \Omega$$

$$Z_2 = \frac{4000(j10^4 L)}{4000 + j10^4 L} = \frac{j16 \cdot 10^4 L + 4 \cdot 10^5 L^2}{16 + 100 L^2}$$

$$Z_T = Z_1 + Z_2 = 1600 + \frac{4 \cdot 10^5 L^2}{16 + 100 L^2} - j1600 + j \frac{16 \cdot 10^4 L}{16 + 100 L^2}$$

For i_g and V_g to be in phase require Z_T to be purely resistive $\Rightarrow \text{Im}(Z_T) = 0$

$$\Rightarrow 1600 = \frac{16 \cdot 10^4 L}{16 + 100 L^2} \Rightarrow 16 \cdot 10^4 L = 25600 + 160000 L^2$$

$$\Rightarrow 1600 L^2 - 1600 L + 256 = 0 \Rightarrow 25 L^2 - 25 L + 4 = 0$$

$$\Delta = 625 - 400 = 225 \Rightarrow L_{1,2} = \frac{25 \pm 15}{50} = 0.8, 0.2 \text{ H}$$

⑨

$$b) L = 0.8 \text{ H} \Rightarrow Z_T = 1600 + \frac{4 \cdot 10^5 \cdot 0.64}{16 + 64} = 4800 \Omega$$

$$I_g = \frac{V_g}{Z} = \frac{96 \angle 0^\circ}{4800} = 20 \angle 0^\circ \text{ mA}$$

$$\Rightarrow i_g = 20 \cos 10000t \text{ mA}$$

$$L = 0.2 \text{ H} \Rightarrow Z_T = 1600 + \frac{4 \cdot 10^5 (0.04)}{16 + 4} = 2400 \Omega$$

$$I_g = \frac{V_g}{Z} = \frac{96 \angle 0^\circ}{2400} = 40 \angle 0^\circ \text{ mA}$$

$$\Rightarrow i_g = 40 \cos 10000t \text{ mA}$$