


## EECS 210 Sec 2 - W'01 Midterm 1 - 2/9/01

50 minutes, closed book, one 8.5"x11" crib sheet, calculator, no scratch sheets

I have neither given nor received aid on this exam, nor have I concealed any violation of the Honor Code.

Name: Solution Set

$v(t)_{in}$  is periodic in time  $T_{in}$ , exhibits odd symmetry, and is comprised of a fundamental frequency and two harmonics whose Fourier coefficients are positive and have amplitudes shown in the frequency domain representation:

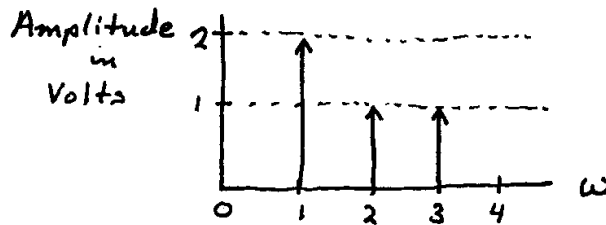1.a (5%) What is the period,  $T_{in}$ , of  $v(t)_{in}$  (in seconds)?

$$\omega_0 = \frac{2\pi}{T_{in}} = 1 \Rightarrow \underline{T_{in} = 2\pi = 6.28 \text{ s}}$$

$F(\omega)$  is a high pass filter with a cutoff at  $f_{co} = 0.25$  Hz so that all frequencies below 0.25 Hz are blocked. Frequencies above 0.25 Hz are passed without a delay in phase but with a transfer function that looks like  $F(\omega) = 1 - e^{-\omega}$

1.b (15%) If  $v(t)_{in}$  is passed through filter  $F(\omega)$  and  $v(t)_{out}$  is the output, write  $v(t)_{out}$  as a sinusoidal series (in Volts).

$$\begin{aligned} \omega = 1 &\Rightarrow f = \frac{1}{2\pi} = 0.16 \text{ Hz} \\ \omega = 2 &\Rightarrow f = \frac{2}{2\pi} = 0.32 \text{ Hz} \end{aligned} \left. \begin{array}{l} \text{fundamental is blocked} \\ \text{2nd harmonic is passed} \end{array} \right\}$$


$$F(2) = 1 - e^{-2} = 0.86; \quad F(3) = 1 - e^{-3} = 0.95$$

$$\therefore \underline{v(t)_{out} = 0.86 \sin 2t + 0.95 \sin 3t \text{ V}}$$

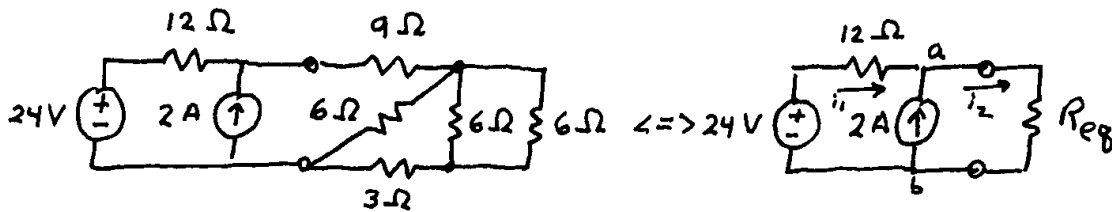1.c (5%) Considering  $v(t)_{out}$  as a new signal, what is its fundamental frequency (in Hz)?

My error here. I had meant to show the 3<sup>rd</sup> component at  $\omega = 4$  rather than at  $\omega = 2$ . Then, for the new signal, the fundamental would have been  $\omega = 2$  and the 2<sup>nd</sup> harmonic would have been  $\omega = 4$ . For this case the fundamental frequency would have been  $f_0 = \frac{2}{2\pi} = 0.32 \text{ Hz}$

The way I drew the problem, the fundamental is  $f_0 = 0.16 \text{ Hz}$ , but it is absent in the signal. I will accept either answer.



2.a (10%) Find  $R_{eq}$  in the equivalent circuit (in ohms).

$$R_{eq} = ((6 \parallel 6) + 3) \parallel 6 + 9 = (3 + 3) \parallel 6 + 9 = 6 \parallel 6 + 9$$

$$= 3 + 9 = 12 \Omega$$

2.b (10%) What is the power dissipated/produced (+/-) by the current source (in Watts)?

We need  $v_{ab}$  → nodal analysis at a

$$i_1 + 2 - i_2 = 0$$

$$\frac{24 - v_2}{12} + 2 - \frac{v_2}{12} = 0$$


$$\Rightarrow 24 - 2v_2 + 24 = 0$$

$$v_2 = 24V$$

$$i_1 P_{2A} = (\text{voltage drop in direction of current}) \times \text{current}$$

$$= -24 \times 2 = -48 W$$

For the circuit:

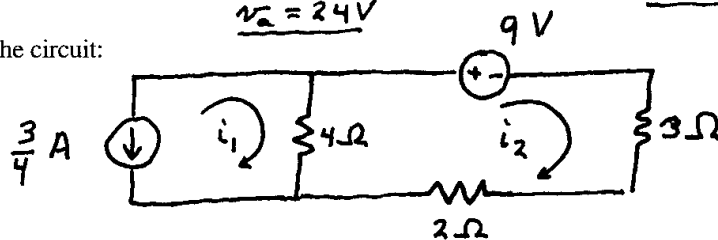


3 (15%) Use mesh-current for loop  $i_2$  to find  $i_2$  (in Amps).

$$-4(i_2 - i_1) - 9 - 5i_2 = 0 \quad \text{but } i_1 = -\frac{3}{4}$$

$$\therefore -4(i_2 + \frac{3}{4}) - 9 - 5i_2 = 0$$

$$-9i_2 - 12 = 0$$

$$i_2 = -\frac{4}{3} A$$

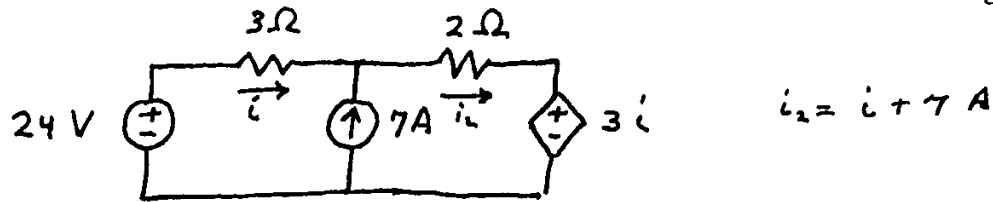

- 4 (15%) Use KVL around the outer loop to find current  $i$  (in Amps)?


$$+24 - 3i - 2(i_2) - 3i = 0$$

$$24 - 3i - 2(i+7) - 3i = 0$$

$$8i = 24 - 14$$

$$i = \frac{5}{4} \text{ A}$$

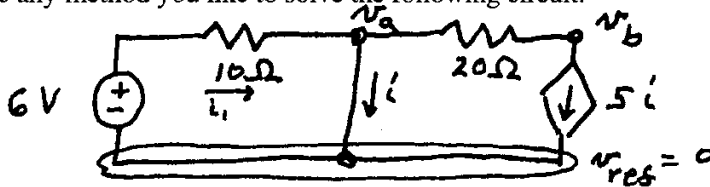Use any method you like to solve the following circuit:



- 5.a (10%) What is the voltage  $v_a$  (in Volts)?

$$\text{By observation, } \underline{v_a = v_{ref} = 0 \text{ V}}$$

- 5.b (15%) What is the voltage  $v_b$  (in Volts)?

$$\text{Try nodal analysis: at a) } i_1 - i - 5i = 0$$

$$\text{but } i_1 = \frac{6 - v_a}{10} = \frac{6 - 0}{10} = \frac{3}{5} \text{ A}$$

$$i \quad \frac{3}{5} - i - 5i = 0$$

$$\text{or } i = \frac{1}{10} \text{ A}$$

$$\text{Also } 5i = \frac{v_a - v_b}{20} = \frac{0 - v_b}{20}$$

$$\Rightarrow v_b = -100i = -100 \left(\frac{1}{10}\right)$$

$$\underline{v_b = -10 \text{ V}}$$