

# Solution Set



## EECS 210 Sec 2 - W'01 Midterm 2 - 3/16/01

50 minutes, closed book, 2-sides 8.5x11 crib sheet, calculator, no scratch sheets


Honor Code Pledge: "I have neither given nor received aid on this exam, nor have I concealed any violation of the Honor Code."

Signature: \_\_\_\_\_ Print Name: \_\_\_\_\_

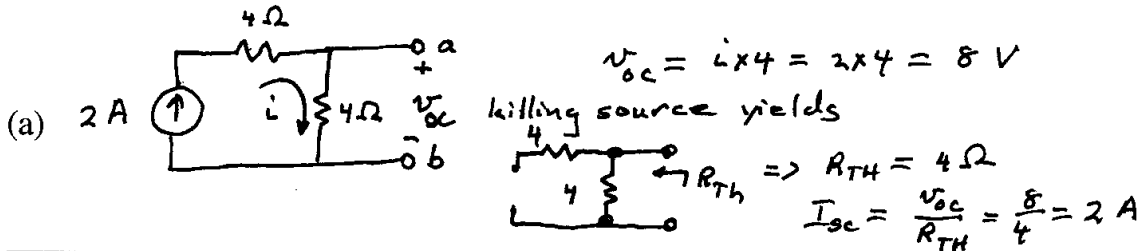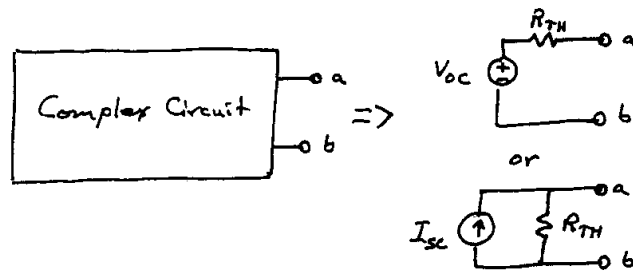- 1 Find Thevenin and Norton components. Include units. Hint with (c), believe your math. Follow the sign conventions shown in this sketch.



	$V_{OC}$	$I_{SC}$	$R_{TH}$
(a) (10%)	8 V	2 A	4 $\Omega$

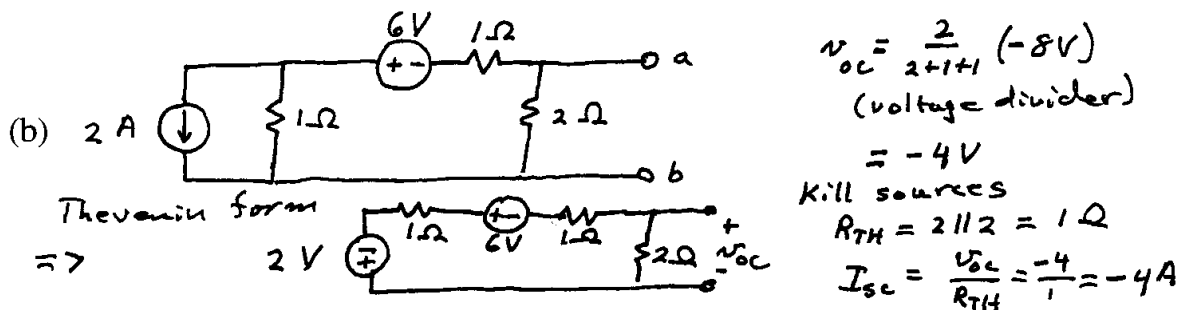

	$V_{OC}$	$I_{SC}$	$R_{TH}$
(b) (15%)	-4 V	-4 A	1 $\Omega$


For  $I_{sc}$

Nodal KCL at a

$$i_1 + 2 - i_x = 0$$

$$\frac{3i_x - v_a}{1} + 2 - i_x = 0 \text{ but } i_x = \frac{v_a}{1}$$

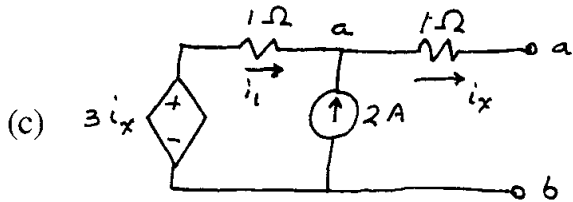
$$\therefore 3i_x - i_x + 2 - i_x = 0 \Rightarrow i_x = I_{sc} = -2 \text{ A}$$



For  $V_{oc}$ ,  $i_x = 0 \Rightarrow$  kill dependent source  $\Rightarrow v_a = 1\Omega \times 2\text{A} = 2\text{V}$   $\left| R_{TH} = -\frac{2}{-2} = -1\Omega \right.$   
 with  $i_x = 0$ ,  $V_{oc} = v_o = 2\text{V}$

	$V_{oc}$	$I_{sc}$	$R_{TH}$
(c) (15%)	2 V	-2 A	-1 $\Omega$

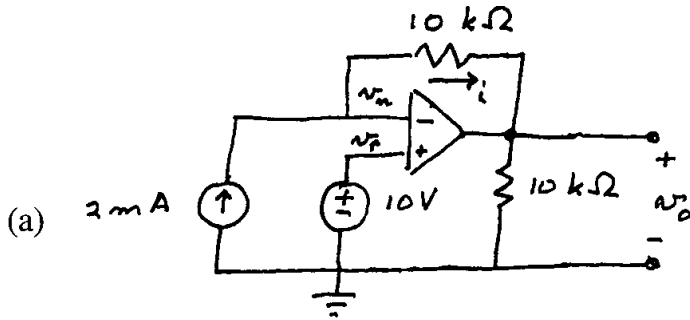2 Find the output voltages,  $v_o$ , for each of the following Op Amp circuits. Assume that you can use the "Golden Rules".




$$v_n = 10 \text{ V}$$

$$i = \frac{v_n - v_o}{10^4} = 2 \times 10^{-3}$$

$$10 - v_o = 20$$

$$v_o = -10 \text{ V}$$

(a) (15%)  $v_o = -10 \text{ V}$

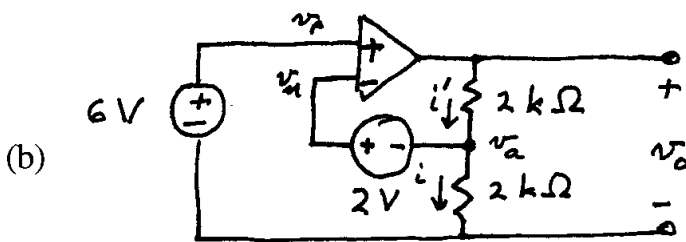

$$v_p = v_n = 6 \text{ V}$$

$$v_a = v_n - 2 = 4 \text{ V}$$

$$i = \frac{v_a}{2 \times 10^3} = i'$$


$$v_o = v_a + i' \times 2 \times 10^3$$

$$= v_a + \frac{v_a}{2 \times 10^3} \times 2 \times 10^3$$

$$= 2 v_a = 2 \times 4$$

$$= 8 \text{ V}$$

(b) (15%)  $v_o = 8 \text{ V}$

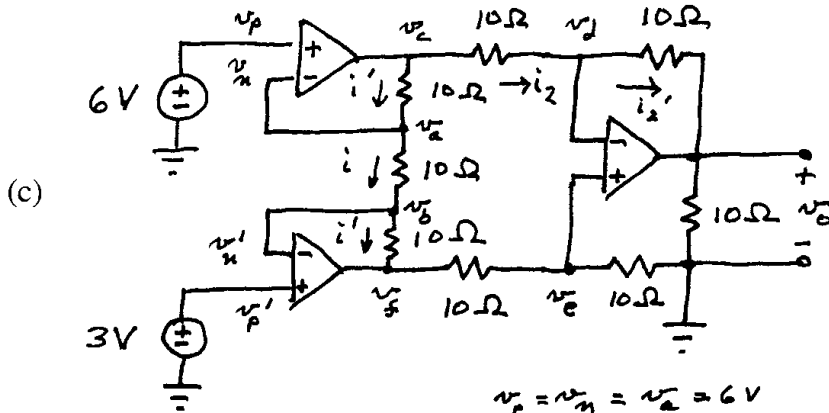

(c) (15%)  $v_0 = -9V$

$$v_p = v_n = v_2 = 6V$$

$$v_p' = v_n' = v_0 = 3V$$

$$i = i' = \frac{v_a - v_b}{10} = \frac{3V}{10}$$


$$v_e = v_a + i' \times 10 = 6 + 3 = 9V$$

$$v_5 = v_b - i' \times 10 = 3 - 3 = 0V$$

$$\Rightarrow v_e = 0 \Rightarrow v_2 = 0 \Rightarrow i_2 = \frac{v_e - v_2}{10} = \frac{9}{10}$$

$$i_2 = i_2' \Rightarrow i_2' = \frac{v_2 - v_0}{10} = \frac{-v_0}{10} = \frac{9}{10} \Rightarrow v_0 = -9V$$

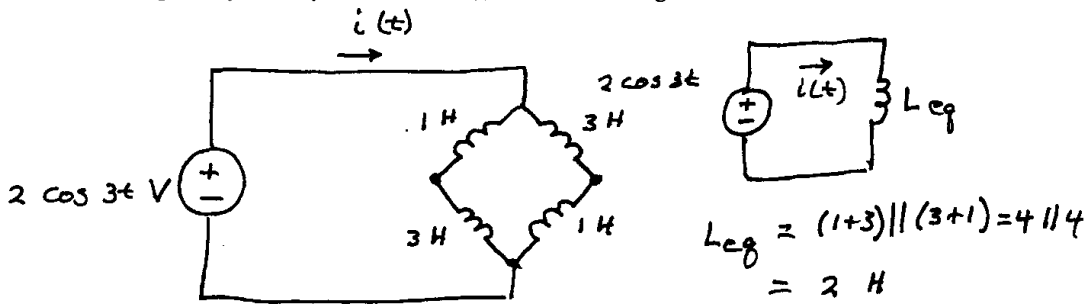In the following steady-state system, what is  $i(t)$  if its time average is zero?



(15%)  $i(t) = \frac{1}{3} \sin 3t \text{ A}$

$$\int_{i(t_0)}^{i(t)} di = \frac{1}{L_{eq}} \int_{t_0}^t v(t) dt$$

$$i(t) - i(t_0) = \frac{1}{2} \int_{t_0}^t 2 \cos 3t dt$$

$$= \frac{1}{3} \sin 3t \Big|_{t_0}^t$$

$$= \frac{1}{3} \sin 3t - \frac{1}{3} \sin 3t_0$$

$\therefore i(t) = \text{constant} + \frac{1}{3} \sin 3t$   
 Average over all time of sinusoid is zero,  $\therefore$  for average over all time of  $i(t)$  to be zero, constant = 0