

-
1. This is the *differential amplifier* (page 200 of text).

$$V_O = \frac{18k(30k+20k)}{30k(6k+18k)}(12V) - \frac{20k}{30k}(24V) = -1V \rightarrow i_L = \frac{-1V}{5k} = -0.2mA.$$

2. $i_n = 0 \rightarrow V_o = V_n + (1mA)(9k) = 9V$ since $V_n = V_p = 0$.

$$-i_O = \frac{9V}{15k \parallel 6k} + 1mA = 3.1mA \rightarrow i_O = -3.1mA.$$

3. Thevenin equivalent of input is $V_T = v_g \left(\frac{4.8}{3.2+4.8} \right) = 0.3V$, $R_T = 4.8k \parallel 3.2k = 1.92k\Omega$.

$$\text{Inverting amplifier (text p.196)} \rightarrow V_O = -\frac{30k + \sigma 170k}{1.92k}(0.3V) = -(26.5625\sigma + 4.6875).$$

This reaches -10 when $\sigma = 0.20$. Hence no saturation for $0 < \sigma < 0.20$.

4. Inverting summer: $v_o = -\left(\frac{72k}{R_a}v_a + \frac{72k}{R_b}v_b + \frac{72k}{R_c}v_c + \frac{72k}{R_d}v_d \right) = -(6v_a + 9v_b + 4v_c + 3v_d)$.

$$\rightarrow R_a = 12k\Omega; \quad R_b = 8k\Omega; \quad R_c = 18k\Omega; \quad R_d = 24k\Omega.$$

5a. $P_{16k\Omega} = \frac{(0.32V)^2}{16k\Omega} = 6.4\mu W$. (b) $(0.32V) \left(\frac{16k}{48k+16k} \right) = 0.08V$. $P_{16k\Omega} = \frac{(0.08V)^2}{16k\Omega} = 0.4\mu W$.

- 5c. Ratio = $\frac{6.4\mu W}{0.4\mu W} = 16$. (d) This circuit isolates the weak 320 mV source from the load. The op-amp supplies current and voltage so that its output *follows* the input.
-

6. Noninverting amp with input $v_g \frac{5.6k}{2.4k+5.6k} = 0.7v_g$ and gain $1 + \frac{75k}{15k} = 6$.

Without saturation, $v_o(t) = 6(0.7)10 \sin(\pi/3)t = 42 \sin(\pi/3)t$ for $t > 0$.

With saturation at $\pm 21V$, the sine wave *clips* at $\pm 21V$.

7a. $i_n = 0 \rightarrow v = v_p = v_n = v_o \left(\frac{R}{R+R} \right) = \frac{v_o}{2} \rightarrow v_o = 2v$.

$$i_p = 0 \rightarrow v_o = v - iR. \text{ Combining these } \rightarrow 2v = v - iR \rightarrow v = -iR. \text{ QED.}$$

- 7b. But this relation only holds as long as the op-amp doesn't saturate, i.e., $|v_o| < 15V$. So the circuit acts like a negative resistor only over a limited range of v and i .

EECS 210

PROBLEM SET #7

Winter 2001

ASSIGNED: March 2, 2001. **Read:** Sects. 9.1-9.5 (skip Chaps. 7 & 8) and Appendix B of the text.
DUE DATE: March 9, 2001. **In Lab Book:** Read Unit #4, Lab Lecture #4 and Lab Experiment #4.

THIS WEEK: Inductors and capacitors and complex numbers.

1. Text #6.4. Just apply the integral counterpart to $v=L(di/dt)$, but watch units! Use Matlab for (b). Note that inductor current must be continuous at $t=0.001$ and $t=0.002$ seconds--a useful check.
 2. Text #6.7. Compute **numerical values** for A_1 and A_2 . Let $x=e^{5000t}$ in (b)
 3. Text #6.19. Requires a nasty derivative; otherwise easy. You should already know answer to (c).
 4. Text #6.21. Combining inductors in series and parallel. All integers after the beginning.
 5. Text #6.26a-e. Careful on (c) and (d)--the initial currents must match the given values.
-
6. For each of the following pairs of complex numbers, do the following:
 - o Multiply them directly in rectangular form, getting an answer in rectangular form;
 - o Convert to polar form, multiply in polar form, convert product back to rectangular form.
 o $\{4+j3, 5+j12\}$; $\{4+j3, (5+j12)^*\}$; $\{4+j3, 1/(5+j12)\}$; $\{1/(4+j3), 1/(5+j12)\}$; $\{(4+j3)^*, (5+j12)\}$
-
7. Show complex number $[5(8+j)(8+j6)(5+j12)(5+j10)]/[26(7+j4)(7+j24)(2+j11)]$ has magnitude=1.
-
8. Use trig identity from Problem Set #1 to show $5\cos(3t+30^\circ)+5\sin(3t)+5\cos(3t-210^\circ)=0$ exactly! Now use phasor representations of the sinusoids to show it. Plot the phasors in the complex plane.
-
9. **Ungraded:** We are given two unmarked boxes, each with a pair of wires sticking out of it. One contains the Thevenin equivalent of a circuit; the other contains its Norton equivalent. Explain how to **distinguish** the Thevenin equivalent box from the Norton equivalent box. **HINT:** This *cannot* be done using i-v characteristics of the two boxes; need something else.

"An optimist is an accordion player with a beeper"--Ted Koppel.