

**EECS 210 Section 2 – Lecture Summaries**  
**Lecture 11, Wednesday, January 31, 2001**

- Reviewed Mesh Current analysis
- Introduced Superposition
  - ✓ Can be used if all circuit elements are linear
  - ✓ Voltage or current at any point in a circuit is the sum of voltages or currents contributed by each independent source with all other sources killed