

**EECS 210 Section 2 – Lecture Summaries**  
**Lecture 12, Friday, February 2, 2001**

- Review of Superposition
  - Introduction to the Thevenin Equivalent Circuit
    - For two-terminal circuits that contain only linear elements, e.g.,
      - ✓ Independent sources
      - ✓ Linear dependent sources
      - ✓ Linear resistors
    - Examples
- 

Review Sessions for Exam 1 – BYOP (Bring Your Own Problems)

Wednesday, February 7, 6:00-7:30, Room 1301 EECS

Thursday, February 8, 2:00-4:00, Room 3433 EECS