

EECS 210 Section 2 – Lecture Summaries
Lecture 13, Monday, February 5, 2001

- Review of Thevenin Equivalent circuits
- Introduction to the Norton Equivalent Circuit
 - For two-terminal circuits that contain only linear elements, e.g.,
 - ✓ Independent sources
 - ✓ Linear dependent sources
 - ✓ Linear resistors
 - Examples

Review Sessions for Exam 1 – BYOP (Bring Your Own Problems)

Wednesday, February 7, 6:00-7:30, Room 1301 EECS

Thursday, February 8, 2:00-4:00, Room 3433 EECS