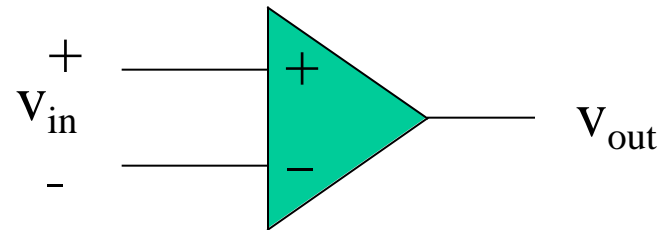


EECS 210 Section 2 – Lecture Summaries

Lecture 16, Monday, February 12, 2001

- Review of Norton Equivalent circuits
- Introduced the Operational Amplifier
 - Used often for signal conditioning
 - Circuit representation assumes “proper environment”



- 2 models
 - ✓ Ideal Op Amp
 - ✓ Infinite input resistance
 - ✓ Zero output resistance
 - ✓ More Realistic Op Amp
 - ✓ $\sim 1\text{ M}$ input resistance
 - ✓ ~ 30 output resistance