

EECS 210 Section 2 – Lecture Summaries
Lecture 17, Wednesday, February 14, 2001

- Reviewed Ideal and More Realistic Op Amp models
- Showed $R_1 = R_o$ for maximum power transfer
- Showed half of power dissipation for maximum power transfer occurs in amplifier
- Developed the voltage follower (memorize)