

EECS 210 Section 2 – Lecture Summaries
Lecture 18, Friday, February 16, 2001

- Developed the non-inverting amplifier (memorize)
- Developed inverting amplifier (memorize)
- Developed inverting summer
- Mentioned difference amplifier (your task)
- Introduced “Virtual Short Principle”
- Applies only when there is negative feedback
- Input of Op Amp is a short for voltage
- Input of Op Amp is an open for current