

EECS 210 Section 2 – Lecture Summaries
Lecture 19, Monday, February 19, 2001

- Introduced cascaded Op Amps
- Practiced virtual short principle
 - Valid only when there is negative feedback
 - Applies to input side of Op Amp
 - Virtual short for voltage
 - Effective open for current
- Example of a current amplifier