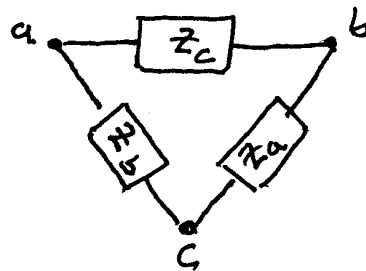


## EECS 210 Section 2 – Lecture Summaries


### Lecture 28, Monday, March 19, 2001

- To convert 3-terminal  $\Delta$  (or  $\pi$ ) to 3-terminal Y (or T)

$\Delta$  (or  $\pi$ )



Y (or T)

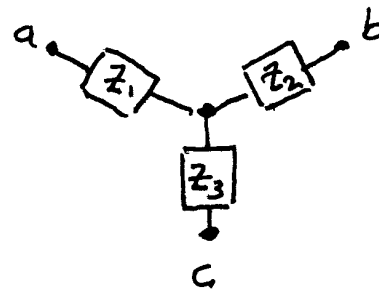

➤ Remember symmetry

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

- Series LC circuit is a short at resonance
- Parallel LC circuit is an open at resonance