

EECS 210 Section 2 – Lecture Summaries
Lecture 31, Monday, March 26, 2001

- Calculating power is an inherently non-linear process
 - Superposition requires a linear system
 - Superposition cannot be used to compute power
 - Except where source signals are independent within circuit – this occurs when source frequencies differ
- Ratio of output to input signals of a linear system is called the Transfer Function, $H(\omega)$
 - $H(\omega)$ is used to characterize performance of filters
 - Bode diagram is a convenient way to view frequency response of a filter
 - Bode diagram has two parts:
 - ✓ $|H(\omega)|$ in dB vs $\log_{10}(\omega)$, and
 - ✓ $\angle H(\omega)$ vs $\log_{10}(\omega)$