

EECS 210 Section 2 – Lecture Summaries

Lecture 8, Wednesday, January 24, 2001

- Adjust nodes to better visualize circuit
- Parallel conductances add, concept of current divider
- Power conservation (Tellegen's Thm)
- Analysis of more complicated circuits – simplify and think before jumping in