

Review

## 25% Signals

Given  $f(t) = 5 + \cos t + 3 \sin 3t$

What is the fundamental frequency,  $f_0$  (Hz)?

$$\omega_0 t = 2\pi f_0 t \Rightarrow \underline{f_0 = \frac{1}{2\pi} = 0.16 \text{ Hz}}$$

What is the fundamental angular frequency,  $\omega_0$  (rad/s)?

$$\omega_0 t = t \Rightarrow \underline{\omega_0 = 1 \text{ rad/s}}$$

What is the peak-to-peak amplitude of the 2nd harmonic?

0, there is no 2nd harmonic

What is the rms amplitude in dBV of

the fundamental  $V_{\text{rms}} = \frac{1}{\sqrt{2}} = 0.707$

$$= 20 \log_{10} 0.707 = \underline{-3 \text{ dBV}}$$


For Signal in  $\rightarrow$   $F(\omega)$   $\rightarrow$  signal out

What is signal out in time domain if


$$\left. \begin{array}{l} F(\omega) = 0 \quad 0 < \omega < \frac{\pi}{2} \\ F(\omega) = 1 \angle -90^\circ, \frac{\pi}{2} \leq \omega \end{array} \right\} \text{high pass filter}$$

$$f_{\text{out}}(t) = 3 \sin(3t - 90^\circ)$$

$$= \underline{-3 \cos(3t)}$$

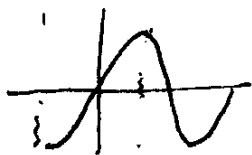

## 75% Circuits

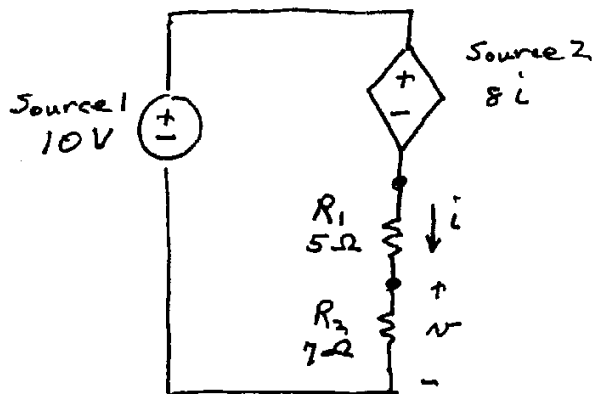

find  $v$   
find power  
 generated (-) or  
 dissipated (+)  
 in each element.

Simplify  $\rightarrow$  not obvious

Superposition  $\rightarrow$  doesn't help with only 1 independent source

nodal-voltage analysis -  $m = 4 - 1 - 1 = 2$  equations

mesh-current analysis -  $m = 1$  equation

Try mesh:

Label  $i_1$  with  $i = i_1$

Write mesh equation  $10 - 8i - 5i - 7i = 0$

$$20i = 10; i = 0.5A$$

$$\therefore v = R_2 i = 7 \times 0.5 = 3.5A$$


$$P_{S1} = (-10)(0.5) = -5W$$

$$P_{S2} = (8 \times 0.5)(0.5) = 2W$$


$$P_{R1} = i^2 R_1 = (0.5)^2 \times 5 = 1.25$$

$$P_{R2} = i^2 R_2 = (0.5)^2 \times 7 = 1.75$$

note:  $\sum P_x = 0$  as required

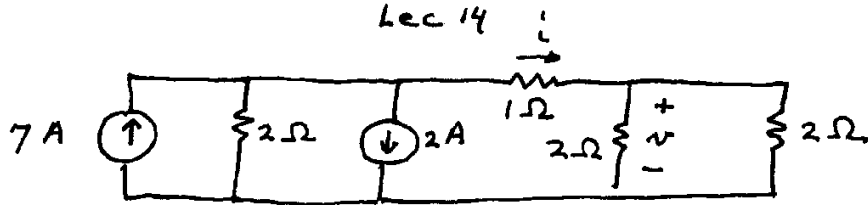


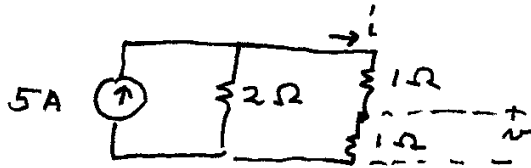find  $v$  and  $i$  using simplification  
 Combine  $2\Omega$  resistors + 2 current sources




find  $i$ ? current divider  $i = 5 \frac{1/2}{1/2 + 1/2} = 2.5A$

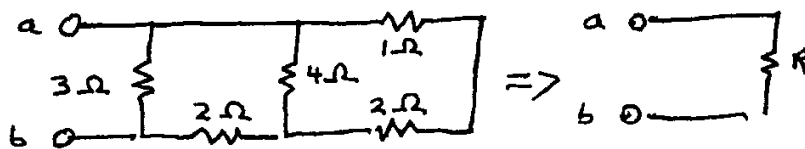$v$ ?  $v = 1\Omega \times i = 1 \times 2.5 = 2.5V$




find  $R$

Patience

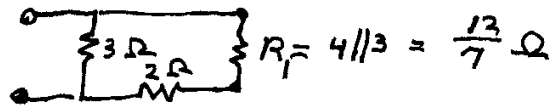

⇓

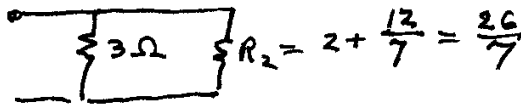


⇓

$$R_3 = 3 \parallel \frac{26}{7} = \frac{3 \times \frac{26}{7}}{3 + \frac{26}{7}} = \frac{3 \times 26}{21 + 26} = \frac{78}{47} \Omega$$

leave as ratio

don't insist upon "nice" numbers

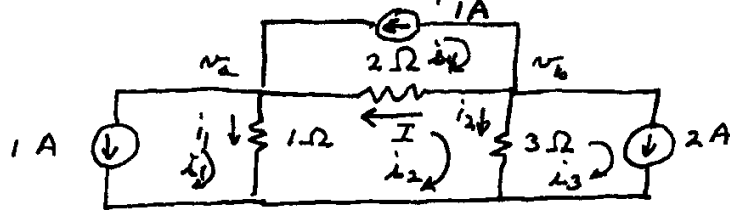

a) Write necessary node-voltage equations;  $m = 3 - 1 = 2$

$$a) -1 - i_1 + 1 + I = 0 \Rightarrow -1 = \frac{v_a}{1} + 1 + \frac{v_b - v_a}{2} = 0$$

$$b) -I - 1 - i_2 - 2 = 0 \Rightarrow -\left(\frac{v_b - v_a}{2}\right) - 1 - \frac{v_b}{3} - 2 = 0$$

Simplify  $3v_a - v_b = 0$

$$-3v_a + 5v_b = -18$$

b) Find  $I$  by solving node-voltage equations

need both  $v_a$  and  $v_b \Rightarrow$

$$v_a = \frac{\begin{vmatrix} 1 & -1 \\ -18 & 5 \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -3 & 5 \end{vmatrix}} = \frac{-18}{15-3} = -\frac{18}{12} = -\frac{3}{2} \text{ V}$$

$$v_b = \frac{\begin{vmatrix} 1 & -1 \\ -3 & 5 \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -3 & 5 \end{vmatrix}} = \frac{-54}{12} = -\frac{9}{2} \text{ V}$$

$$I = \frac{v_b - v_a}{2} = \frac{-\frac{9}{2} + \frac{3}{2}}{2} = -\frac{3}{2} \text{ A}$$

c) Write necessary mesh-current equations  $m = 4 - 3 = 1$

Label, equation  $-1(i_2 - i_1) - 2(i_2 - i_4) - 3(i_2 - i_3) = 0$

but  $i_1 = -1, i_4 = -1, i_3 = 2$


$$\therefore -1(i_2 + 1) - 2(i_2 + 1) - 3(i_2 - 2) = 0$$

$$\text{or } -6i_2 = 3 \text{ or } i_2 = 0.5 \text{ A}$$


$$I = -i_2 + i_4 = 0.5 + i_4 = 0.5 - 1.0$$

$$= -\frac{3}{2} \text{ A}$$

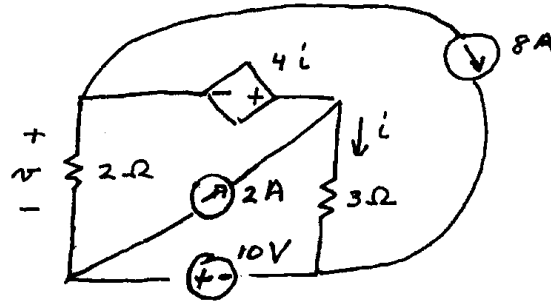d) Find  $I$  by solving mesh-current equations



Find  $v$  using superposition

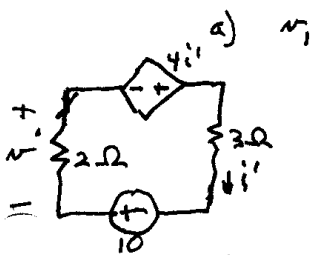


if we know  $i'$ , we have it, KVL

$$-2i' + 4i' - 3i' + 10 = 0$$

$$i' = 10 \text{ A}$$
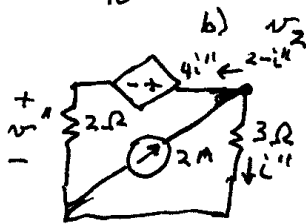
$$\Rightarrow v' = 2(-i') = -2 \times 10 = \underline{-20 \text{ V}}$$




KVL around outer loop

$$-2(-2-i'') + 4i'' - 3i'' = 0$$

$$4 - 2i'' + 4i'' - 3i'' = 0$$

$$i'' = 4 \text{ A}$$
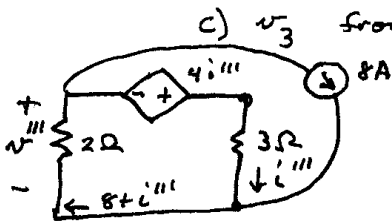
$$v'' = 2(2-i'') = 2(2-4) = \underline{-4 \text{ V}}$$



KVL around loop

$$-2(8+i''') + 4i''' - 3i''' = 0$$


$$-16 - 2i''' + 4i''' - 3i''' = 0$$

$$i''' = -16 \text{ A}$$

$$d) v = \quad \therefore v''' = 2(-8+i''') = 2(-8-16)$$

$$= \underline{16 \text{ V}}$$
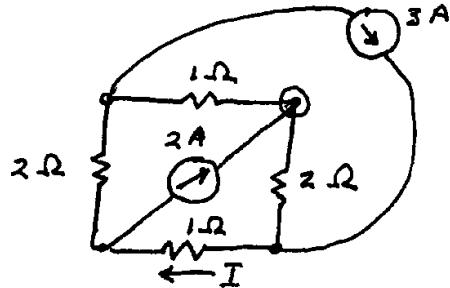
$$\therefore v = \underline{-20 \text{ V} + 4 \text{ V} + 16 \text{ V} = -8 \text{ V}}$$




Find  $I$  any  
way you want

node-voltage  $m = 4 - 1 - 0 = 3$  equations


mesh-current  $m = 3 - 2 = 1$  but 2A source is shared

I would use superposition

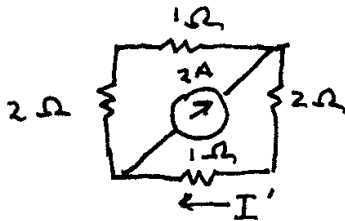

what do we have  $\Rightarrow$  current divider
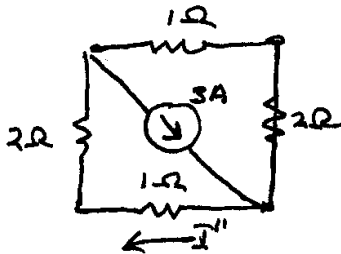
$$I' = 2 \frac{\frac{1}{3}}{\frac{1}{3} + \frac{1}{3}} = 1 \text{ A}$$




again current divider

$$I'' = 3 \times \frac{1}{2} = 1.5 \text{ A}$$

$$\Rightarrow \underline{I = I' + I'' = 2.5 \text{ A}}$$

(over)

Node-voltage method

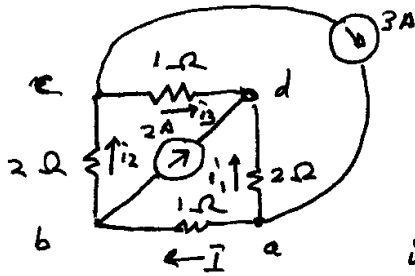

set das reference  
(arbitrary)

Label

$$i_1 = \frac{v_a}{2} ; I = \frac{v_a - v_b}{1} ; i_2 = \frac{v_b - v_e}{2}$$

$$i_3 = \frac{v_c}{1}$$

a)  $-I - i_1 + 3 = 0$

$$-\left(\frac{v_a - v_b}{1}\right) - \frac{v_a}{2} + 3 = 0 \Rightarrow 3v_a - 2v_b + 0v_c = 6$$

b)  $-i_2 - 2 + I = 0$

$$-\left(\frac{v_b - v_e}{2}\right) - 2 + \frac{v_a - v_b}{1} \Rightarrow -2v_a + 3v_b - v_c = -4$$

c)  $i_2 - i_3 - 3 = 0$

$$+\left(\frac{v_b - v_e}{2}\right) - \frac{v_c}{1} - 3 = 0 \Rightarrow 0v_a - v_b + 3v_c = -6$$

or 
$$\begin{bmatrix} 3 & -2 & 0 \\ -2 & 3 & -1 \\ 0 & -1 & 3 \end{bmatrix} \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix} = \begin{bmatrix} 6 \\ -4 \\ -6 \end{bmatrix}$$

need  $v_a$  and  $v_b$