

Problem Set #4

- 3.11 a) Find the voltage v_x in the circuit in Fig. P3.11.
 b) Replace the 30 V source with a general voltage source equal to V_s . Assume V_s is positive at the upper terminal. Find v_x as a function of V_s .

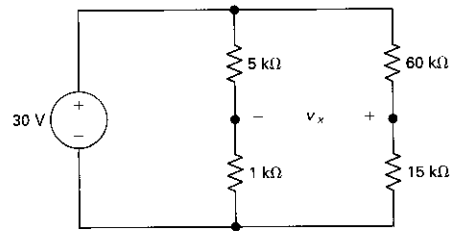


Figure P3.11

- 3.16 In the voltage-divider circuit shown in Fig. P3.16, the no-load value of v_o is 6 V. When the load resistance R_L is attached across the terminals a and b, v_o drops to 4 V. Find R_L .

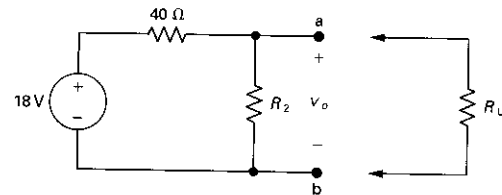


Figure P3.16

- 3.18 The no-load voltage in the voltage-divider circuit shown in Fig. P3.18 is 150 V. The smallest load resistor that is ever connected to the divider is 60 kΩ. When the divider is loaded, v_o is not to drop below 100 V.
 a) Design the divider circuit to meet the specifications just mentioned. Specify the numerical value of R_1 and R_2 .

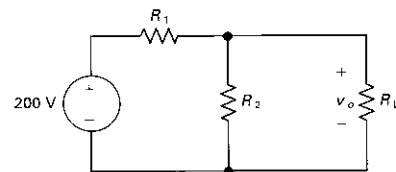


Figure P3.18

3.37 Design a d'Arsonval voltmeter that will have the three voltage ranges shown in Fig. P3.37.

a) Specify the values of R_1 , R_2 , and R_3 .

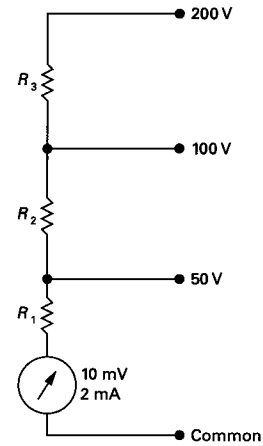


Figure P3.37

4.3 Use the node-voltage method to find v_1 and the power delivered by the 60 V voltage source in the circuit in Fig. P4.3.

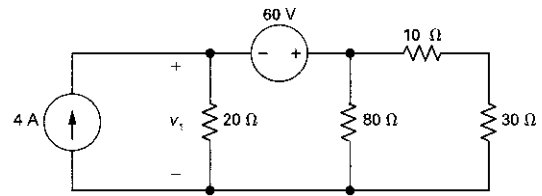


Figure P4.3

4.7 Use the node-voltage method to find v_1 and v_2 in the circuit shown in Fig. P4.7.

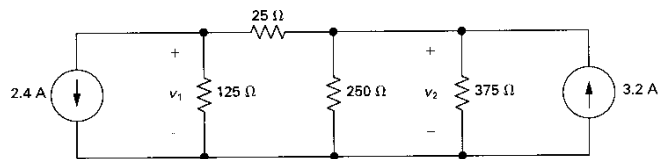


Figure P4.7

4.20 Use the node-voltage method to find v_o in the circuit in Fig. P4.20.

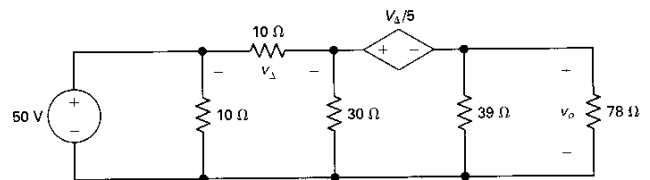


Figure P4.20

- 4.30 a) Use the mesh-current method to find the branch currents i_a , i_b , and i_c in the circuit in Fig. P4.30.

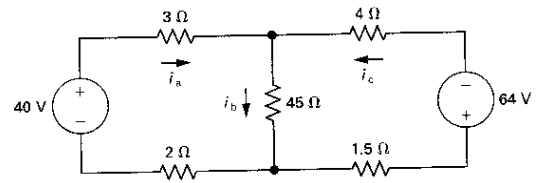


Figure P4.30

- 4.45 The circuit in Fig. P4.45 is a direct-current version of a typical three-wire distribution system. The resistors R_a , R_b , and R_c represent the resistances of the three conductors that connect the three loads R_1 , R_2 , and R_3 to the 125/250 V voltage supply. The resistors R_1 and R_2 represent loads connected to the 125 V circuits, and R_3 represents a load connected to the 250 V circuit.

- a) Calculate v_1 , v_2 , and v_3 .

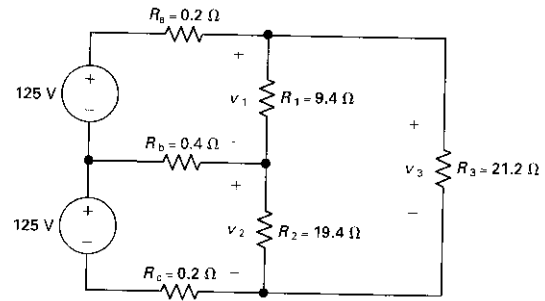


Figure P4.45