

Introduction to Combinational Verilog


EECS270 rev 9/25/12

What is Verilog?

- An HDL: Hardware Description Language
- Another way to express logical function.
- Fundamental form is an algebraic equation.
For example:

$$C = A \& B$$

Schematic equivalent:

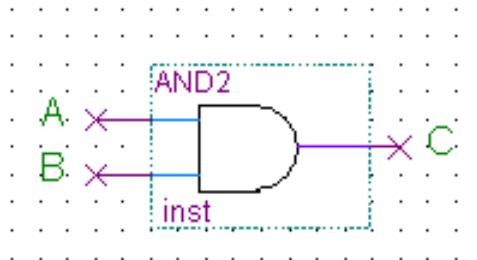


Anatomy of a Verilog Module

- Used to organize logical functions
 - Top-Level-Module (just one)
 - Sub-Level-Module 1 (multiple sub modules)
 - Sub-Level-Module 2
 - Sub-Level-Module 3
- Consists of:
 - Module Declarations
 - Input Output Declarations
 - Logic Function
 - output variables = fnc(input variables)

Lets Make a Verilog Half Adder Module


Schematic Half Adder

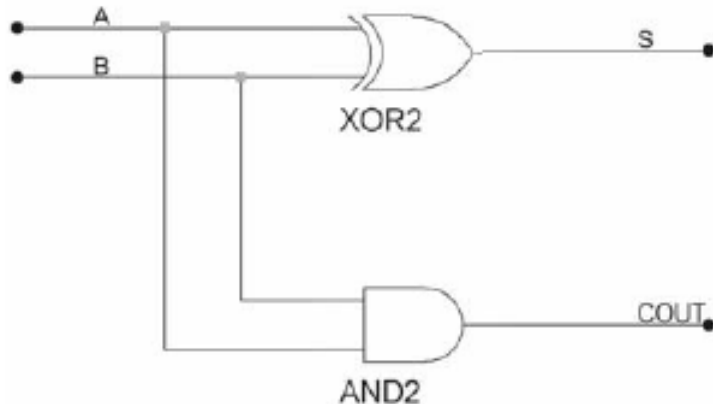


Verilog Half Adder

```
module add_half (a, b, s, cout);  
  
    input a, b;  
    output s, cout;  
    wire s, cout;  
  
    assign s = a ^ b;  
    assign cout = a & b;  
  
endmodule // end of half adder module
```

Module Declaration

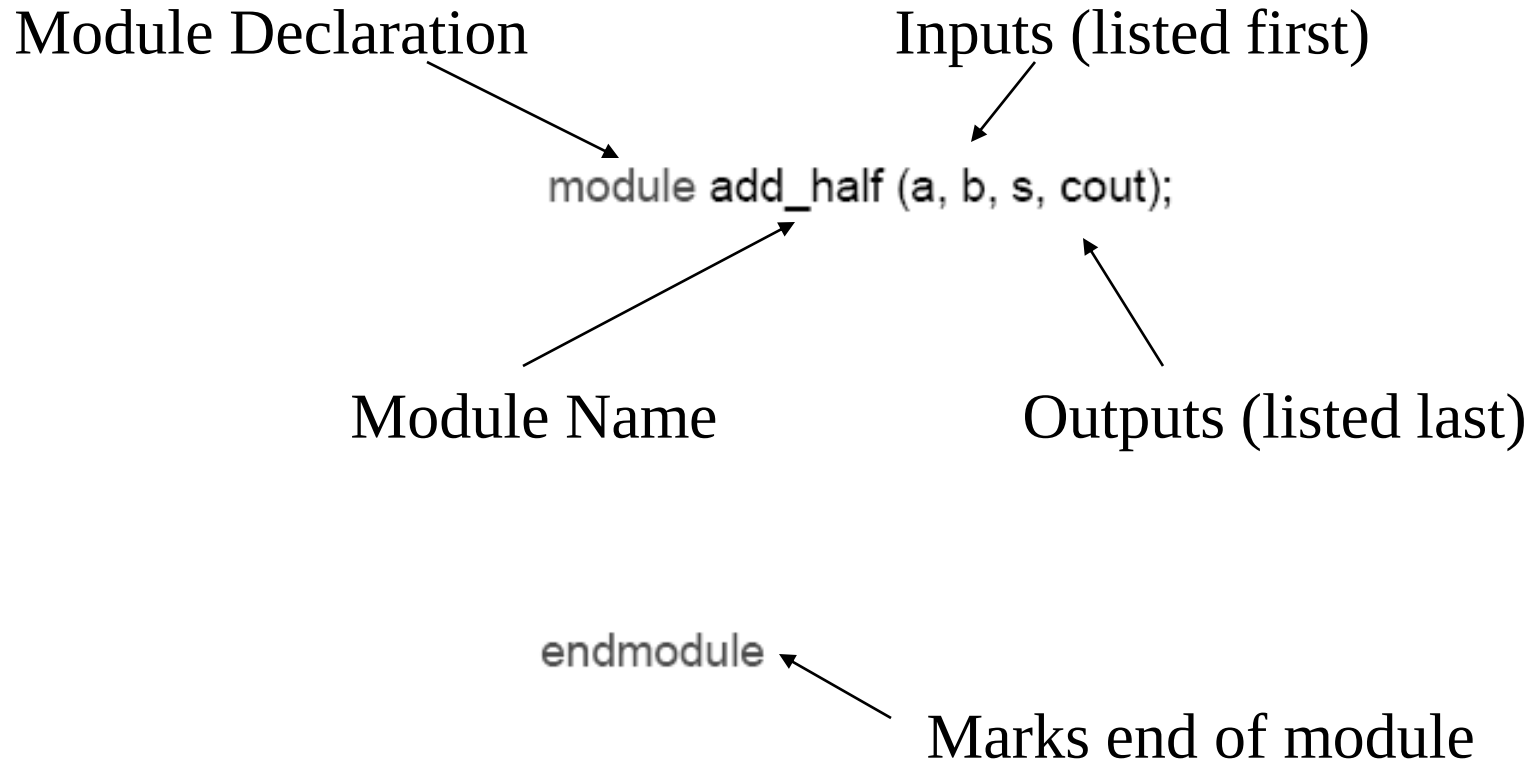

Input and Output Declarations

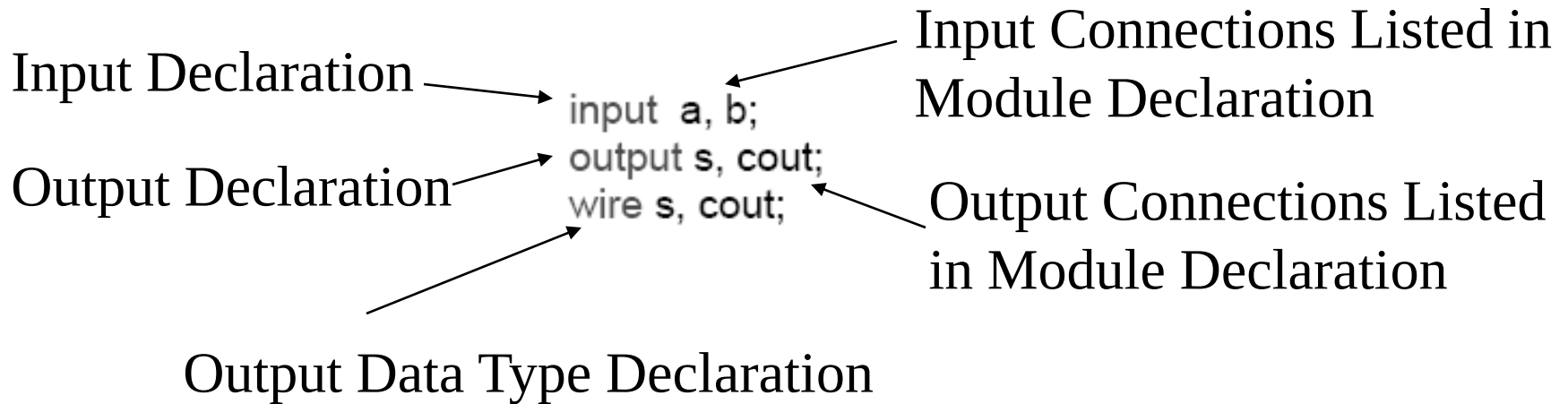

- Must be declared as either “wire” or “reg”
- **wire**: Does not hold state and depends continuously on input values.
- **reg**: (Register) dependent on previous values or state. This type will be used later in sequential logic labs.

Assignments

- Assignments associate output variables to input variables via a logical function.

```
assign s = a ^ b;  
assign cout = a & b;
```

- Although the assignment for cout follows s, s and cout respond **simultaneously (in parallel)** to changes in a and b.
- Unlike programming languages such as C, these logical statements **are not** processed in sequential order.

Verilog Operators Available for Lab 3

Verilog is a very powerful language with high level constructs such as: If Then Else, Case Statements, Arithmetic operators, Etc

For Lab 3 you are only allowed to use:

1. Bitwise AND &
2. Bitwise OR |
3. Bitwise negation ~ Can be combined with other logical functions ie NOR of A, B is $\sim(A | B)$.
4. Bitwise XOR ^

Literals

Literals are constants. The syntax for a constant is:

<size><base format><number>

size: size of number in bits, optional

base: numeric base, b (binary), d (decimal, default), h (hex)

number: Constant to be specified

For example:

549 decimal number, no size specified

'h8FF hex number, no size specified

4'b11 4-bit binary number (0011)

5'd3 5-bit decimal number (00011)

Literals, continued

Defining constant references can be very helpful and makes your HDL readable.

For example,

```
`define CONST3 3'b011
```

```
a = b & `CONST3;
```

Sets

- Sets are a way to express a collection of signals
- For example, lets say we want to set the seven segment HEX0 display to the pattern 7.
- 1st, declare the seven segments as a set:

Output [6:0] H0;

- 2nd, set each element to the appropriate level to give the pattern 7.

Sets, continued

Member Assignment

```
assign H0[0] = 0;  
assign H0[1] = 0;  
assign H0[2] = 0;  
assign H0[3] = 1;  
assign H0[4] = 1;  
assign H0[5] = 1;  
assign H0[6] = 1;
```

Group Assignment


```
assign H0 = 7'b1111000
```

or

```
assign H0 = 7'h78
```

or
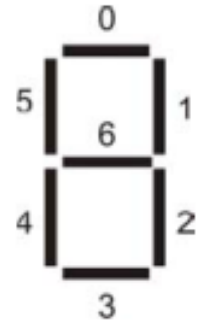
```
`define N7 7'b1111000  
assign H0 = `N7;
```



Clearest and easiest

Module Hierarchy

- HDL project are typically organized into one top level module and several supporting sub modules.
- Sub modules generally represent the various functions needed to support your design.
- The top level module defines the inputs and outputs of your application and the organization of the supporting functions or sub modules.

Module Hierarchy Example

Consider a two-bit adder built with a half adder and full adder.

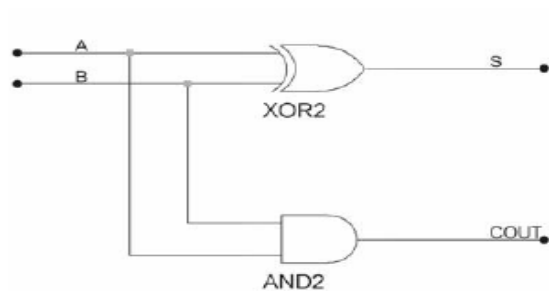


Figure 1a: Half adder

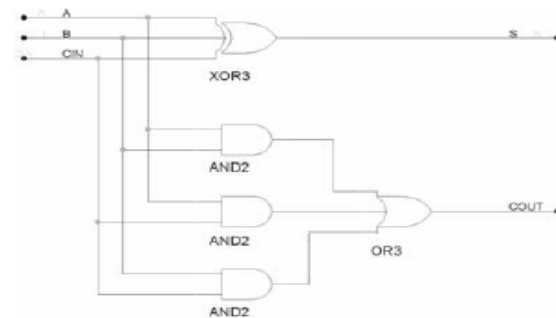


Figure 1b: Full adder

add_2bit module (top)

add_half module (sub)

add_full module (sub)


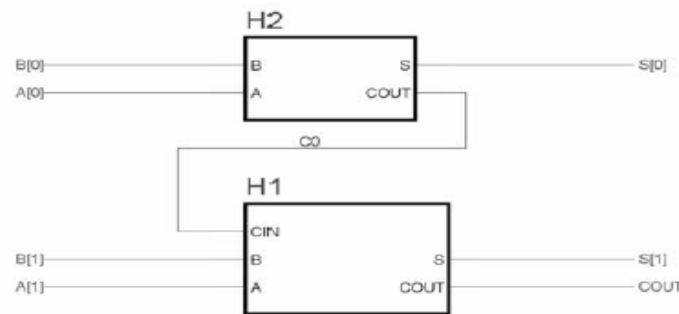


Figure 2c: Two-bit adder built from half adder and full adder

Half Adder Module

Sub Module

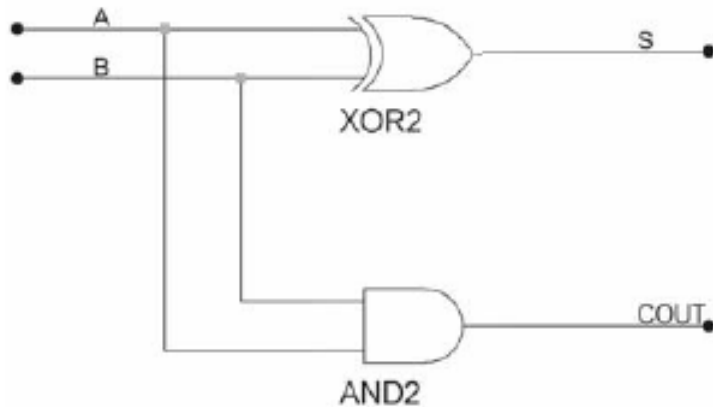

```
module add_half (a, b, s, cout);
```

```
    input a, b;
```

```
    output s, cout;
```

```
    wire s, cout;
```


```
    assign s = a ^ b;
```

```
    assign cout = a & b;
```

```
endmodule // end of half adder module
```

Full Adder Module

Sub Module

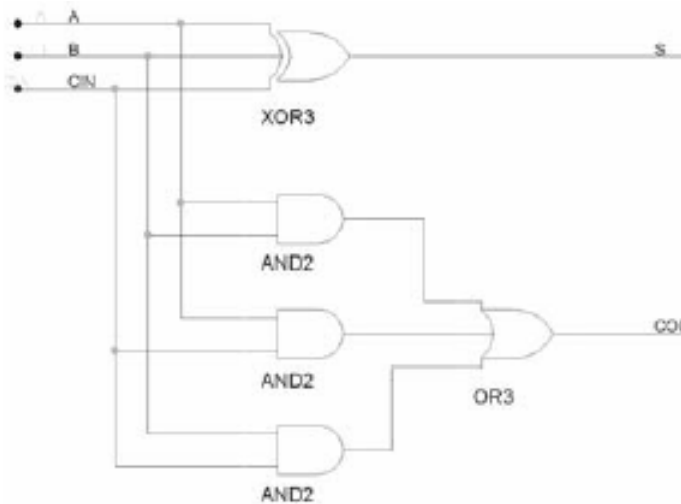

```
module add_full (a, b, cin, s, cout);
```

```
    input a, b, cin;
```

```
    output s, cout;
```

```
    wire s, cout;
```

```
    assign s = a ^ b ^ cin;
```


```
    assign cout = (a & b) | (a & cin) | (b & cin);
```

```
endmodule // end of full adder module
```


Two Bit Adder Module

Top Level Module

Application IO on top level

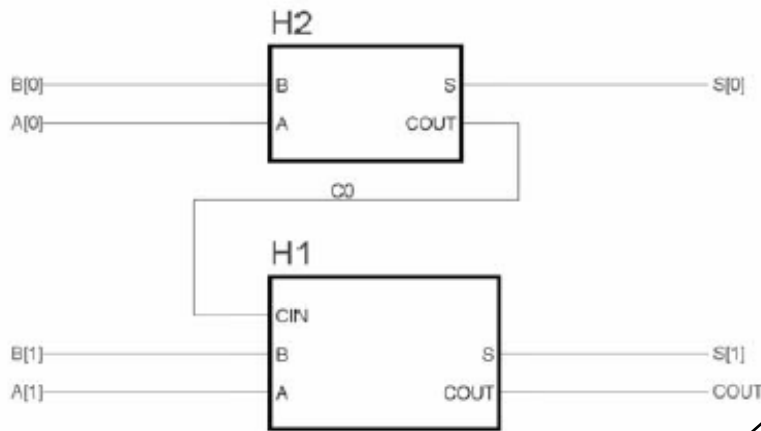

```
module add_2bit (a, b, s, cout);
```

```
    input [1:0] a, b; // Both a and b are 2 bit inputs
    output [1:0] s;   // s[1] = MSB of s, s[0] = LSB of s
    output cout;
    wire [1:0] s;
    wire cout;
    wire c0;          // intermediate carry between adders
```

```
    add_half a1(a[0], b[0], s[0], c0);
    add_full a2(a[1], b[1], c0, s[1], cout);
```

```
endmodule
```

module “call” syntax

<module name> <instance name> (<parameter list>);

- Module name is the name declared in module
- Instance name is one you make up. Each must be unique.
- Inputs and Outputs must follow order set in module declaration.

Pass values between modules with
“wire” types

Final Verilog File

add_2bit module (top)

add_half module (sub)

add_full module (sub)

```
module add_half (a, b, s, cout);
```

```
    input a, b;  
    output s, cout;  
    wire s, cout;
```

```
    assign s = a ^ b;  
    assign cout = a & b;
```

```
endmodule // end of half adder module
```

```
module add_full (a, b, cin, s, cout);
```

```
    input a, b, cin;  
    output s, cout;  
    wire s, cout;
```

```
    assign s = a ^ b ^ cin;  
    assign cout = (a & b) | (a & cin) | (b & cin);
```

```
endmodule // end of full adder module
```

```
module add_2bit (a, b, s, cout);
```

```
    input [1:0] a, b; // Both a and b are 2 bit inputs  
    output [1:0] s; // s[1] = MSB of s, s[0] = LSB of s  
    output cout;  
    wire [1:0] s;  
    wire cout;  
    wire c0; // intermediate carry between adders
```

```
    add_half a1(a[0], b[0], s[0], c0);  
    add_full a2(a[1], b[1], c0, s[1], cout);
```

```
endmodule
```

sub module

sub module

top module

Quartus Particulars

- As with schematic projects, the top-level-module and project name must be the same.
- Top-level-module and file (.v) should be the same name.
- Although it is acceptable to place modules in separate files, it is recommended to put the top-level-module and sub modules in the same file.
- FPGA pin assignments are made to IO names established in the top-level-module with either pin assignment editor or editing the qsf file.