

2.15 Show the conduction paths and output value of the AND gate transistor circuit in Figure 2.13 when: (a) $x = 1$ and $y = 0$, (b) $x = 1$ and $y = 1$.

