

2.30 Convert the following Boolean equations to a digital circuit:

a. $F(a, b, c) = a'bc + ab$

b. $F(a, b, c) = a'b$

c. $F(a, b, c) = abc + ab + a + b + c$

d. $F(a, b, c) = c'$

