

2.35 Fill in Table 2.1's columns for the equation: $F = ab + b'$

Table 2.1: Truth table.

Inputs					Outputs
a	b	ab	b'	ab+b'	F
0	0	0	1	1	1
0	1	0	0	0	0
1	0	0	1	1	1
1	1	1	0	1	1