

2.45 Convert the function F shown in the truth table in Table 2.3 to a digital circuit.

