

2.60 Show the conduction paths and output value of the NAND gate transistor circuit in Figure 2.45 when: (a) $x = 1$ and $y = 0$, (b) $x = 1$ and $y = 1$.

