

2.65 Use XOR to create a circuit that outputs a 1 when the number of 1s on inputs a, b, c, d is odd.

