

2.70 Design a 4x16 decoder using AND, OR and NOT gates.

