

2.75 Create a circuit that rings a bell whenever motion is detected from one of two motion sensors. A switch S determines which sensor to pay attention to: $S=0$ means ring the bell when there's motion at motion sensor 1, $S=1$ means motion sensor 2.

