

3.20 Using four registers, design a circuit that stores the previous four values seen at an 8-bit input D. The circuit should have a single 8-bit output that can be configured using two inputs s1 and s0 to output any one the four registers. (Hint: use an 8-bit 4x1 mux).

