

3.35 \*Assuming one input and one output, how many possible four-state FSMs exist?