

4.10 Design a 10-bit carry-ripple adder using 4-bit carry-ripple adders. (*Component use problem*).

