

4.25 Design a comparator that determines if three 4-bit numbers are equal, by connecting 4-bit magnitude comparators together and using additional components if necessary. (*Component use problem*).

