

4.30 Use magnitude comparators and logic to design a circuit that computes the maximum of two 16-bit numbers. (*Component use problem*).

