

4.60 Design a 4x4 three port (2 read, 1 write) register file. (*Component design problem*).

