

5.40 Draw a complete logic internal structure for a 4x2 SRAM (four words, two bits each), clearly labelling all internal components and connections.

