

5.45 Create an FSM describing the queue controller of Figure 5.78. Pay careful attention to correctly setting the `full` and `empty` outputs.

*The answer can be derived from the solution to Exercise 5.47.*